



AHEAD OF WHAT'S POSSIBLE™

Fundamentals of Data Converters


DAVID KRESS

Director of Technical Marketing


9/14/2016



Analog to Electronic Signal Processing

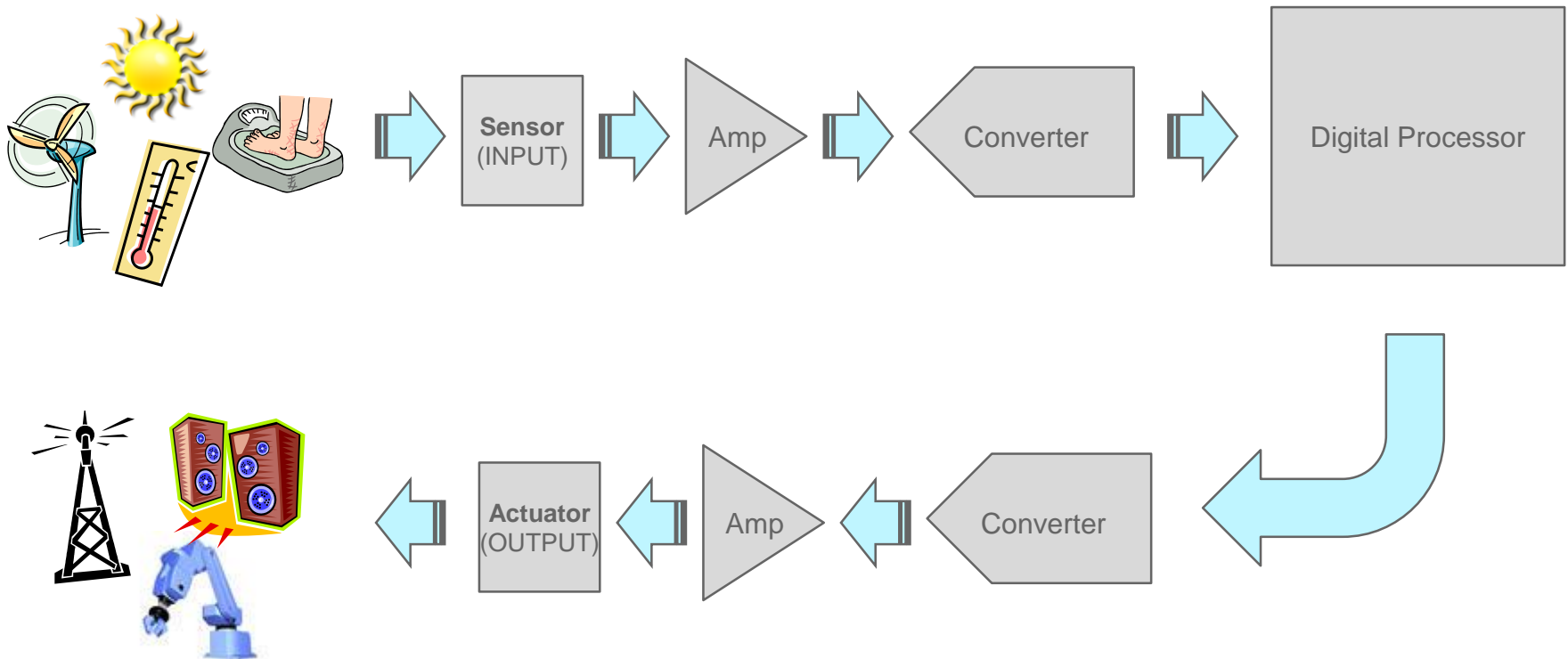

Analog to Electronic Signal Processing

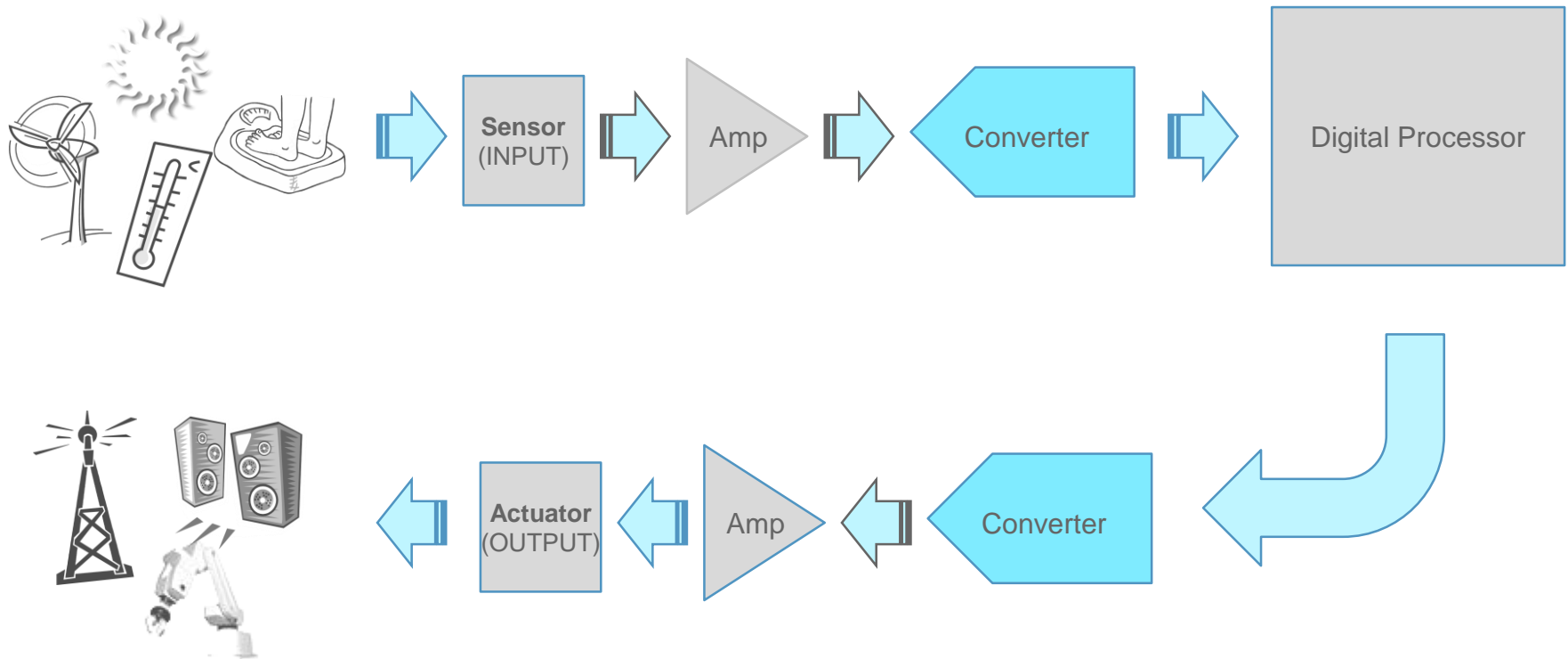

Outline

- ▶ Sampled data system types
- ▶ Digitizing processes
- ▶ Data converters for measurement systems and errors
- ▶ Data converters for dynamic systems and errors
- ▶ Sampling system problems
- ▶ Structure and use of digital-analog converters
- ▶ Structure and use of analog-digital converters

Many Types of Sampled Data Systems



- ▶ Analog to digital converters
- ▶ Digital to analog converters
- ▶ Sample and hold amplifiers
- ▶ Peak detectors
- ▶ Comparators
- ▶ Switched cap filters
- ▶ Samples a continuous signal
- ▶ Domain conversion
 - Analog to digital
 - Digital to analog
 - Continuous time to discrete time
 - Continuous frequency to discrete frequency
- ▶ Sampling rate
 - Continuous, discontinuous

Analog and Digital Domains



Why Convert to Digital?

- ▶ Analog signals are continuous and provide the entire signal
- ▶ Digital signals capture only a portion of the signal
- ▶ Why digitize?
 - Improved signal analysis potential
 - More robust storage
 - More accurate transmission
- ▶ Development objective of sampled data systems is to minimize effect of the sampling process

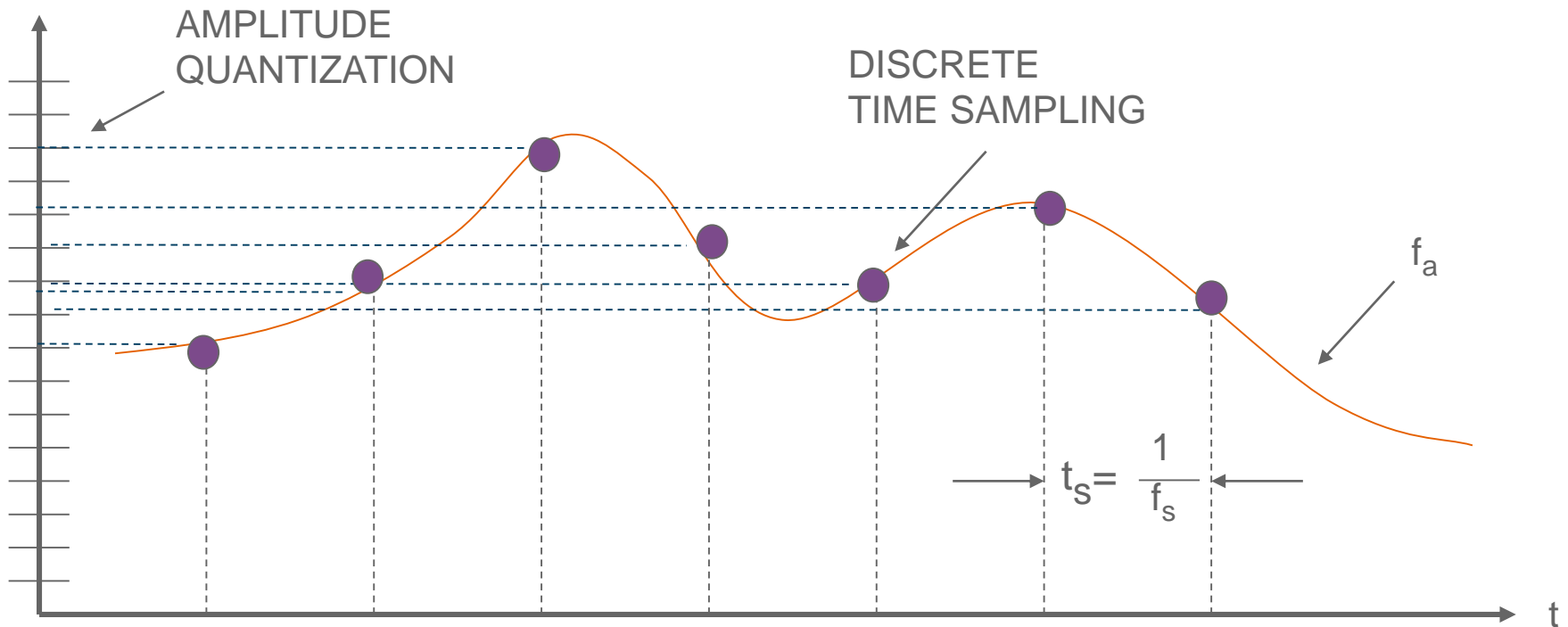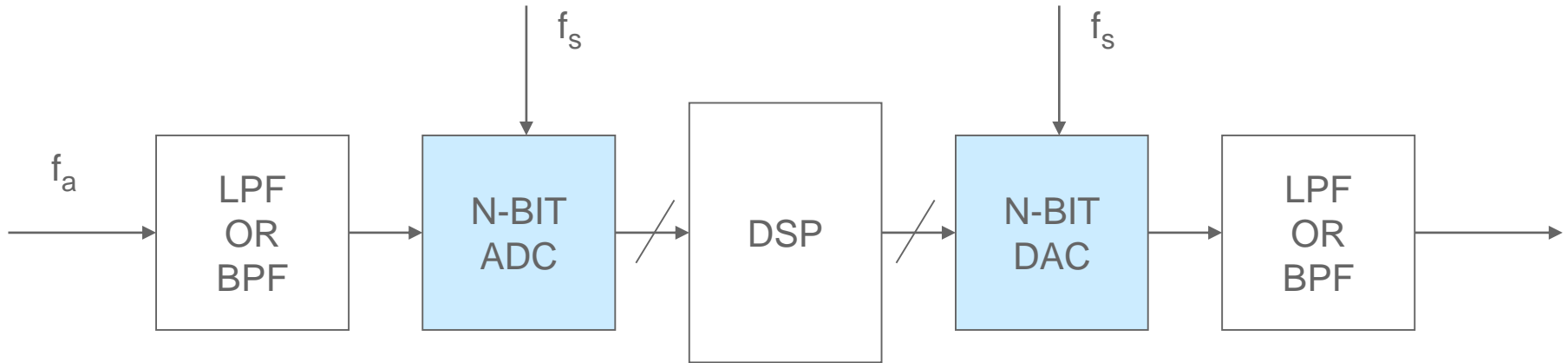Sampled Data System: Sampling and Quantization



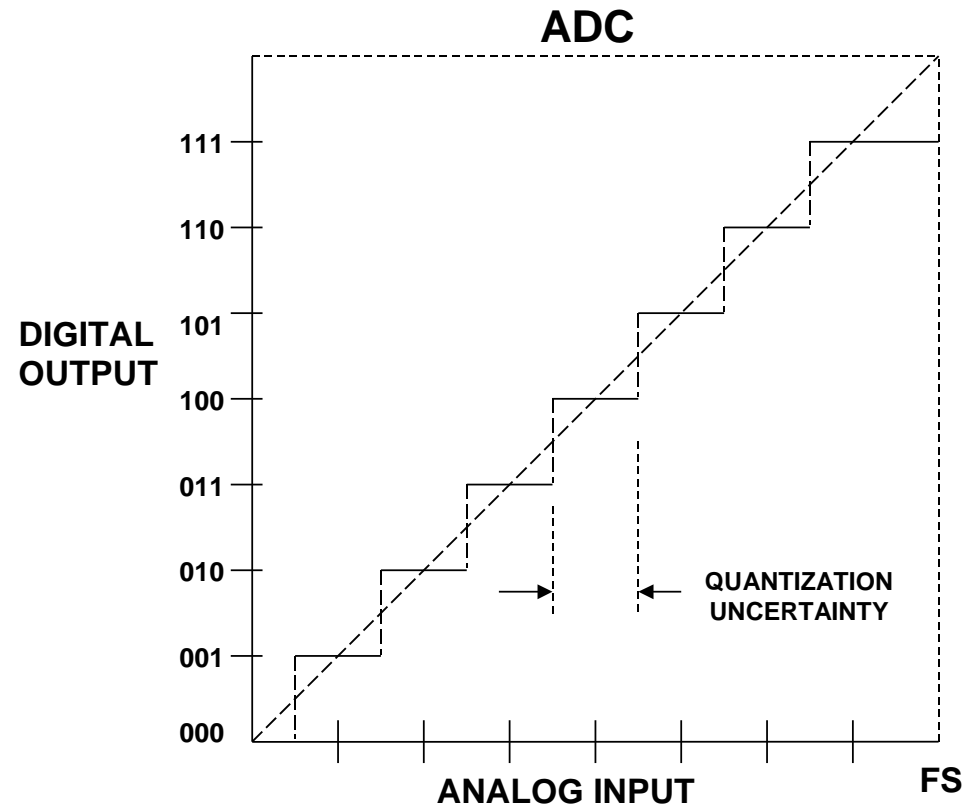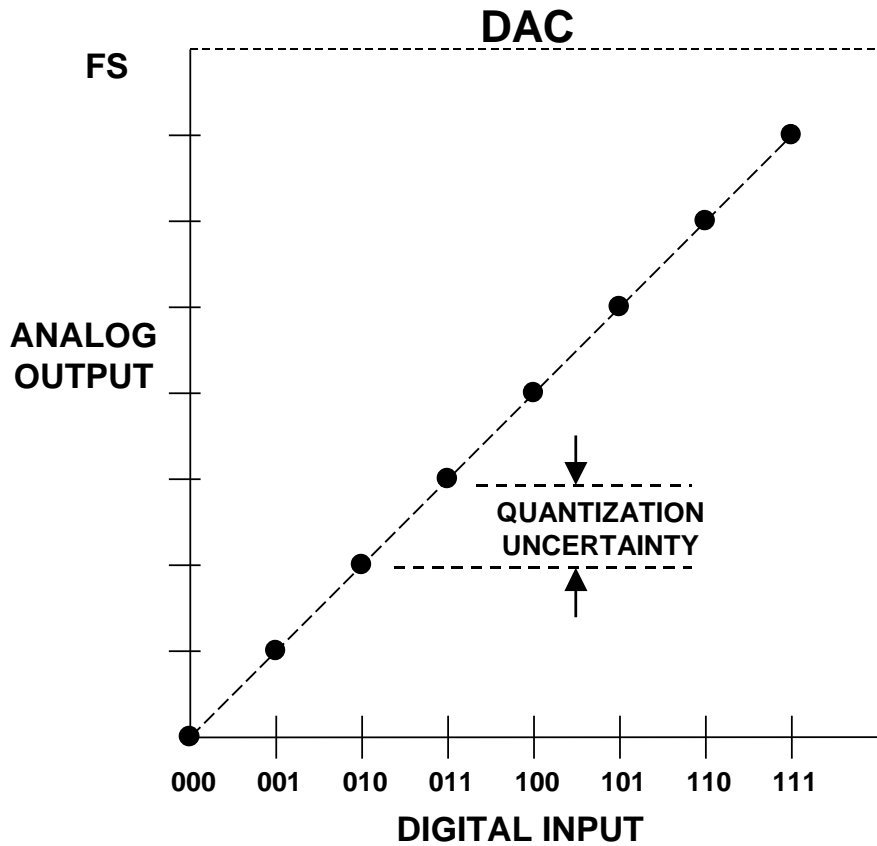Transfer Functions for Ideal 3-Bit DAC and ADC



Unipolar Binary Code, 4-bit Converter

BASE 10 NUMBER	SCALE	+10 V FS	BINARY
+15	$+FS - 1 \text{ LSB} = 15/16 \text{ FS}$	9.375	1111
+14	$+7/8 \text{ FS}$	8.750	1110
+13	$+13/16 \text{ FS}$	8.125	1101
+12	$+3/4 \text{ FS}$	7.500	1100
+11	$+11/16 \text{ FS}$	6.875	1011
+10	$+5/16 \text{ FS}$	6.250	1010
+9	$+9/16 \text{ FS}$	5.625	1001
+8	$+1/2 \text{ FS}$	5.000	1000
+7	$+7/16 \text{ FS}$	4.375	0111
+6	$+3/8 \text{ FS}$	3.750	0110
+5	$+5/16 \text{ FS}$	3.125	0101
+4	$+1/4 \text{ FS}$	2.500	0100
+3	$+3/16 \text{ FS}$	1.875	0011
+2	$+1/8 \text{ FS}$	1.250	0010
+1	$1 \text{ LSB} = +1/16 \text{ FS}$	0.625	0001
0	0	0.000	0000

Bipolar Codes, 4-bit Converter

BASE 10 NUMBER	SCALE	±5V FS	OFFSET BINARY	TWOS COMP.	ONES COMP.	SIGN MAG.
+7	+FS - 1LSB = +7/8 FS	+4.375	1 1 1 1	0 1 1 1	0 1 1 1	0 1 1 1
+6	+3/4 FS	+3.750	1 1 1 0	0 1 1 0	0 1 1 0	0 1 1 0
+5	+5/8 FS	+3.125	1 1 0 1	0 1 0 1	0 1 0 1	0 1 0 1
+4	+1/2 FS	+2.500	1 1 0 0	0 1 0 0	0 1 0 0	0 1 0 0
+3	+3/8 FS	+1.875	1 0 1 1	0 0 1 1	0 0 1 1	0 0 1 1
+2	+1/4 FS	+1.250	1 0 1 0	0 0 1 0	0 0 1 0	0 0 1 0
+1	+1/8 FS	+0.625	1 0 0 1	0 0 0 1	0 0 0 1	0 0 0 1
0	0	0.000	1 0 0 0	0 0 0 0	*0 0 0 0	*1 0 0 0
-1	- 1/8 FS	-0.625	0 1 1 1	1 1 1 1	1 1 1 0	1 0 0 1
-2	- 1/4 FS	-1.250	0 1 1 0	1 1 1 0	1 1 0 1	1 0 1 0
-3	- 3/8 FS	-1.875	0 1 0 1	1 1 0 1	1 1 0 0	1 0 1 1
-4	-1/2 FS	-2.500	0 1 0 0	1 1 0 0	1 0 1 1	1 1 0 0
-5	-5/8 FS	-3.125	0 0 1 1	1 0 1 1	1 0 1 0	1 1 0 1
-6	-3/4 FS	-3.750	0 0 1 0	1 0 1 0	1 0 0 1	1 1 1 0
-7	- FS + 1LSB = -7/8 FS	-4.375	0 0 0 1	1 0 0 1	1 0 0 0	1 1 1 1
-8	- FS	-5.000	0 0 0 0	1 0 0 0		

CODES NOT NORMALLY USED
IN COMPUTATIONS (SEE TEXT)

	ONES COMP.	SIGN MAG.
* 0+	0 0 0 0	0 0 0 0
* 0-	1 1 1 1	1 0 0 0

Quantization: The Size of a Least Significant Bit (LSB)

RESOLUTION N	2^N	VOLTAGE (10V FS)	ppm FS	% FS	dB FS
2-bit	4	2.5 V	250,000	25	- 12
4-bit	16	625 mV	62,500	6.25	- 24
6-bit	64	156 mV	15,625	1.56	- 36
8-bit	256	39.1 mV	3,906	0.39	- 48
10-bit	1,024	9.77 mV (10 mV)	977	0.098	- 60
12-bit	4,096	2.44 mV	244	0.024	- 72
14-bit	16,384	610 μ V	61	0.0061	- 84
16-bit	65,536	153 μ V	15	0.0015	- 96
18-bit	262,144	38 μ V	4	0.0004	- 108
20-bit	1,048,576	9.54 μ V (10 μ V)	1	0.0001	- 120
22-bit	4,194,304	2.38 μ V	0.24	0.000024	- 132
24-bit	16,777,216	596 nV*	0.06	0.000006	- 144

*600nV is the Johnson Noise in a 10kHz BW of a 2.2k Ω Resistor @ 25°C

Remember: 10-bits and 10V FS yields an LSB of 10mV, 1000ppm, or 0.1%.
All other values may be calculated by powers of 2.

Practical Resolution Needs for Data Converters

▶ Instrumentation measurements

- Sensor resolution/accuracy of 0.5% = 1/200
- 8 bits equivalent to 1/256 -- digitizing will lose information
- 10x sensor resolution = 1/2000 -- 12 bits is 1/4096
- Allows discrimination of small changes
- Can also be driven by display requirements



▶ Dynamic signal measurements

- Audio systems need better than 0.1% distortion at 5% of full scale
- Equivalent to 1/20,000 -- 16 bits is 1/65,536

Primary Errors in Data Converters


- ▶ Instrumentation and measurement
 - Described in LSBs(least-significant-bit), % of FS, ppm of FS
 - Offset error – the input level needed to change the first code
 - Gain/full-scale error – the input level need to change the last code
 - Nonlinearity – deviation of codes from the line from zero to FS
 - Differential nonlinearity – code-to-code deviation from 1 LSB
 - Transition noise – ADC uncertainty in code center point

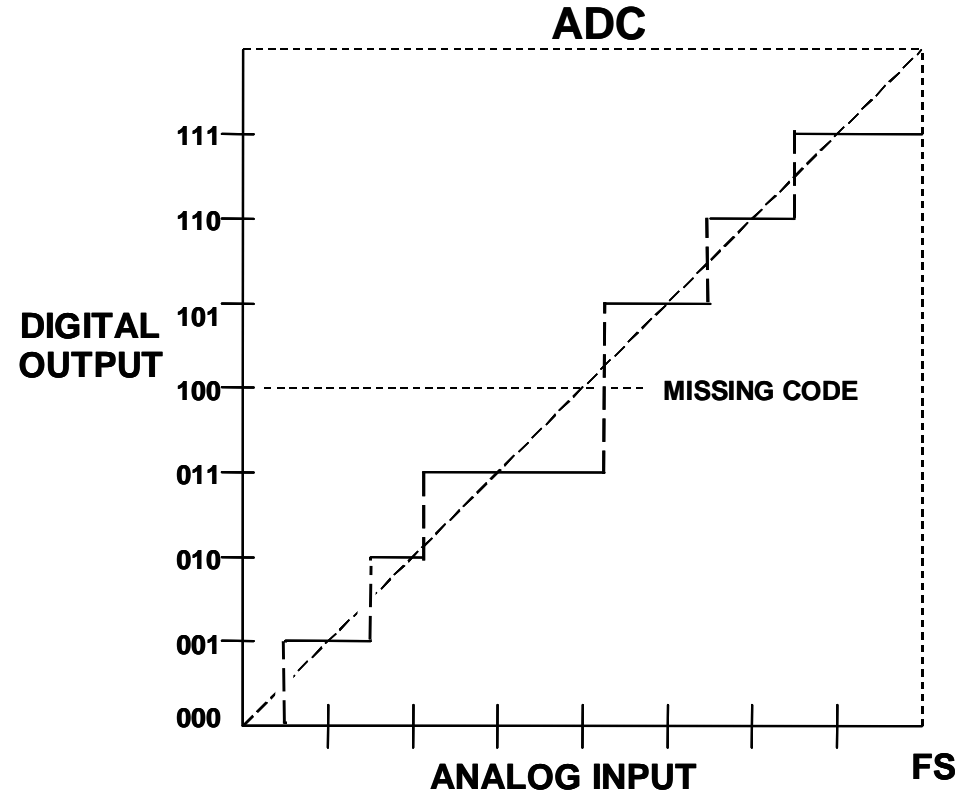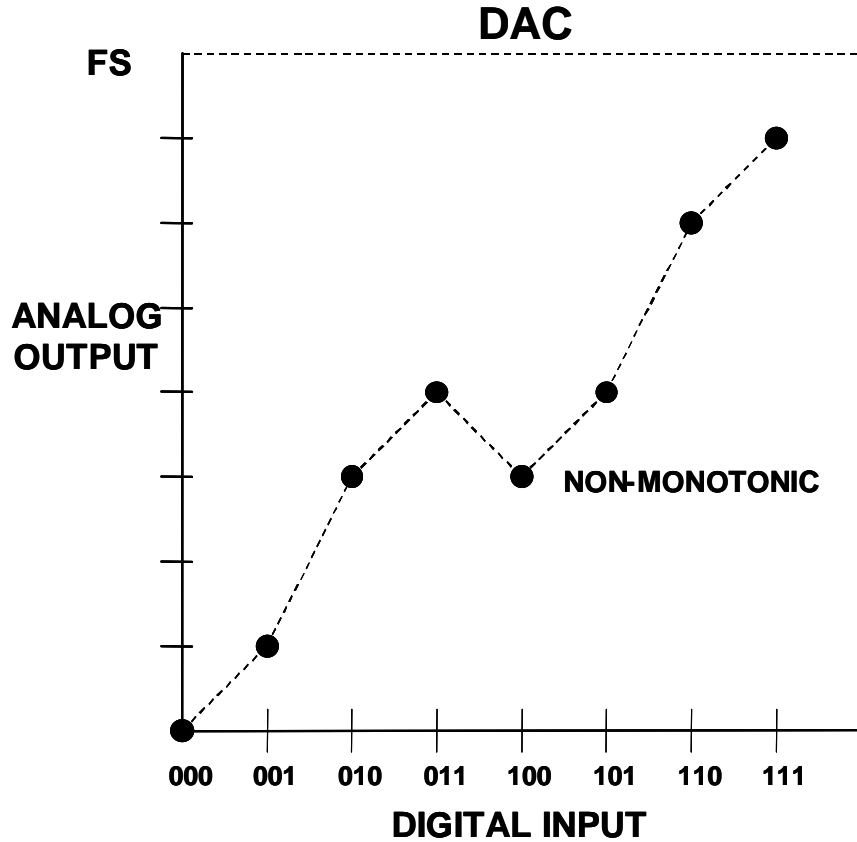Transfer Functions for Non-Ideal 3-Bit DAC and ADC




Combined Effects of Code Transition Noise and DNL


CODE TRANSITION NOISE

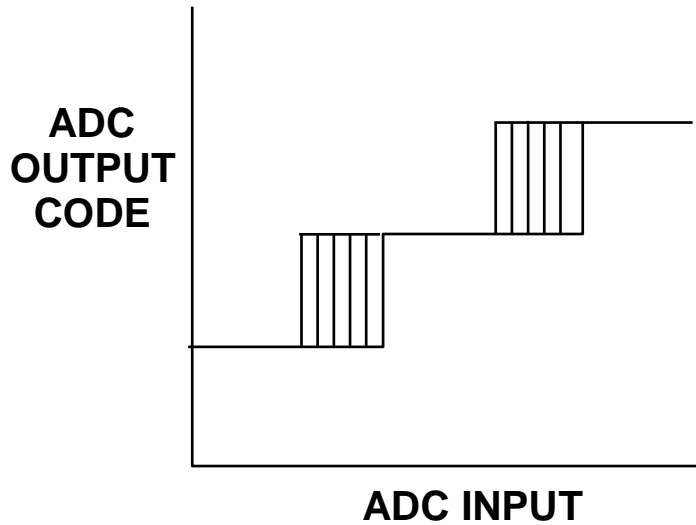

DNL

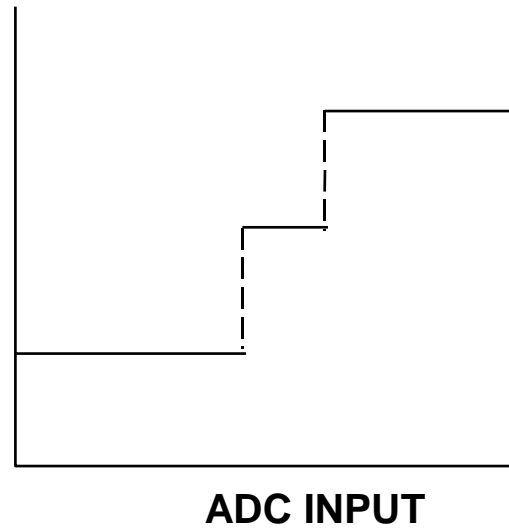

TRANSITION NOISE AND DNL

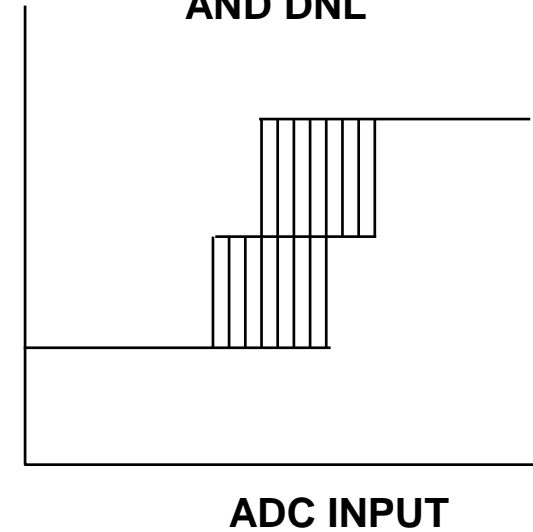

Primary Errors in Data Converters


- ▶ Dynamic systems
- ▶ SINAD (Signal-to-Noise-and-Distortion Ratio):
 - The ratio of the rms signal amplitude to the mean value of the root-sum-squares (RSS) of all other spectral components, including harmonics, but excluding DC.

- ▶ ENOB (Effective Number of Bits):

$$\text{ENOB} = \frac{\text{SINAD} - 1.76\text{dB}}{6.02\text{dB}}$$

- ▶ SNR (Signal-to-Noise Ratio, or Signal-to-Noise Ratio Without Harmonics):
 - The ratio of the rms signal amplitude to the mean value of the root-sum-squares (RSS) of all other spectral components, excluding the first 5 harmonics and DC
- ▶ SFDR (Spurious-Free-Dynamic-Range) Signal dynamic range in the bandwidth of interest containing no frequency noise spurs

Quantization & Quantization Noise

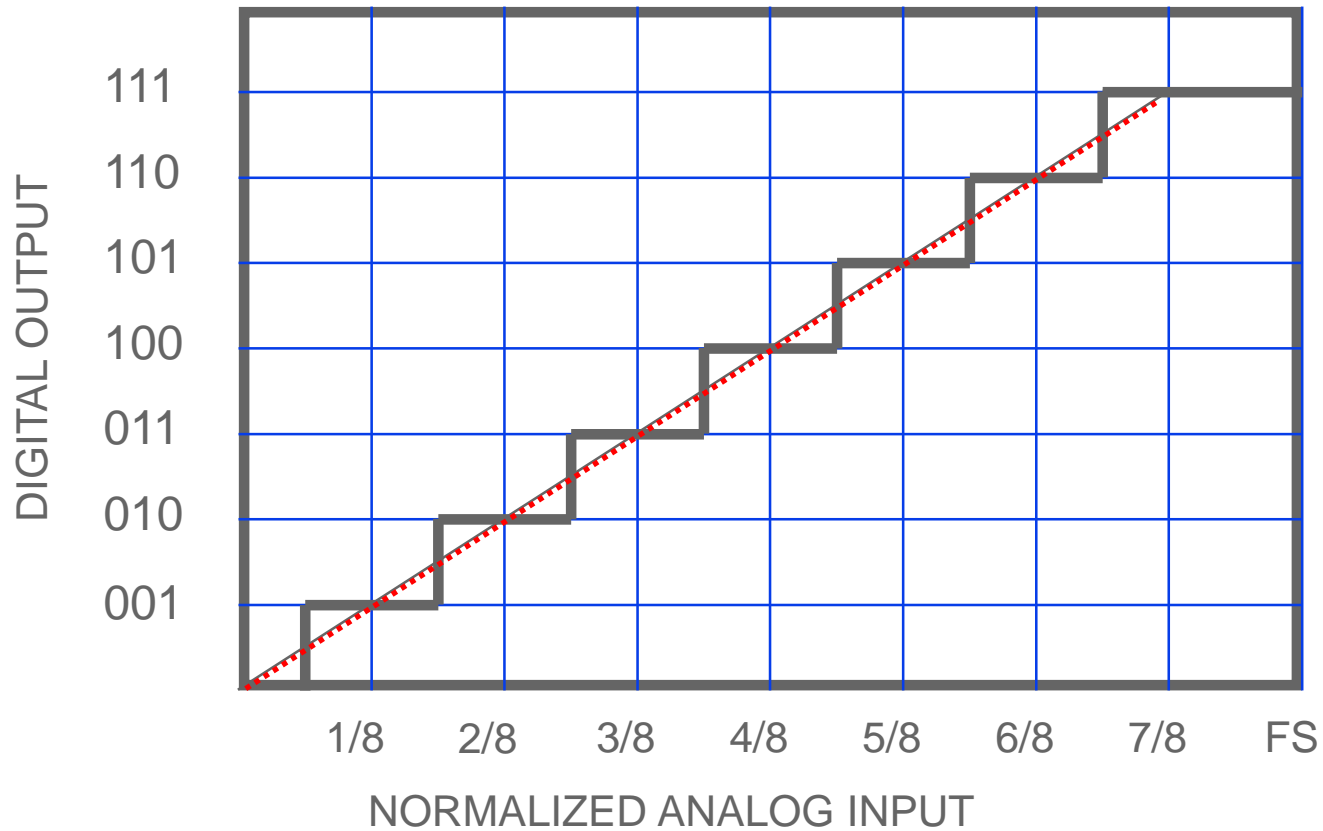


Quantization Error
Function



quantization noise error: RMS value is $\text{LSB}/3.464$

Quantization Noise as a Function of Time

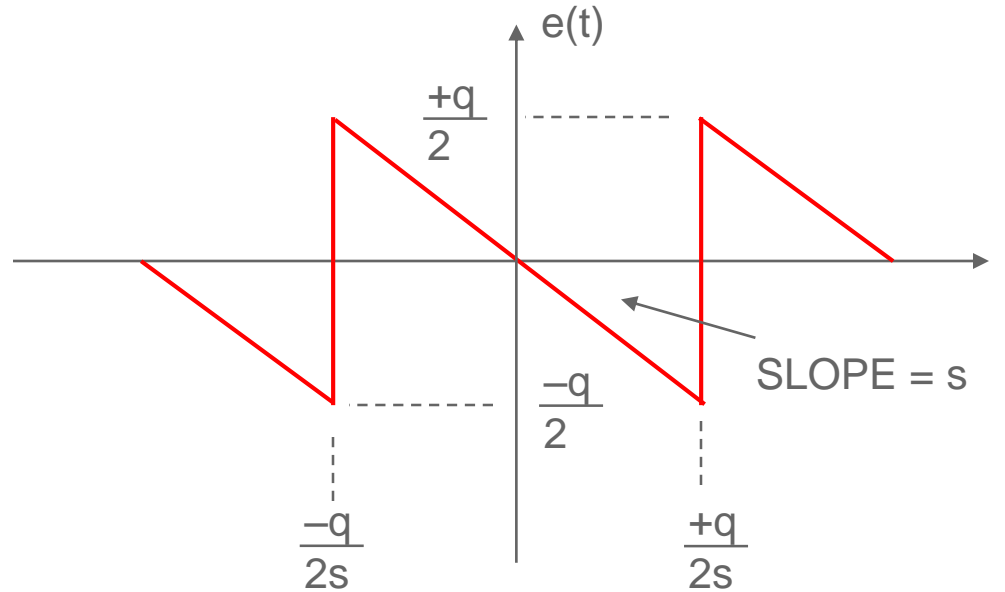


◆ ERROR = $e(t) = st, \quad \frac{-q}{2s} < t < \frac{+q}{2s}$

◆ MEAN-SQUARE ERROR = $\overline{e^2(t)} = \frac{s}{q} \int_{-q/2s}^{+q/2s} (st)^2 dt = \frac{q^2}{12}$

◆ ROOT-MEAN-SQUARE ERROR = $\sqrt{\overline{e^2(t)}} = \frac{q}{\sqrt{12}}$


Ideal ADC Sampling

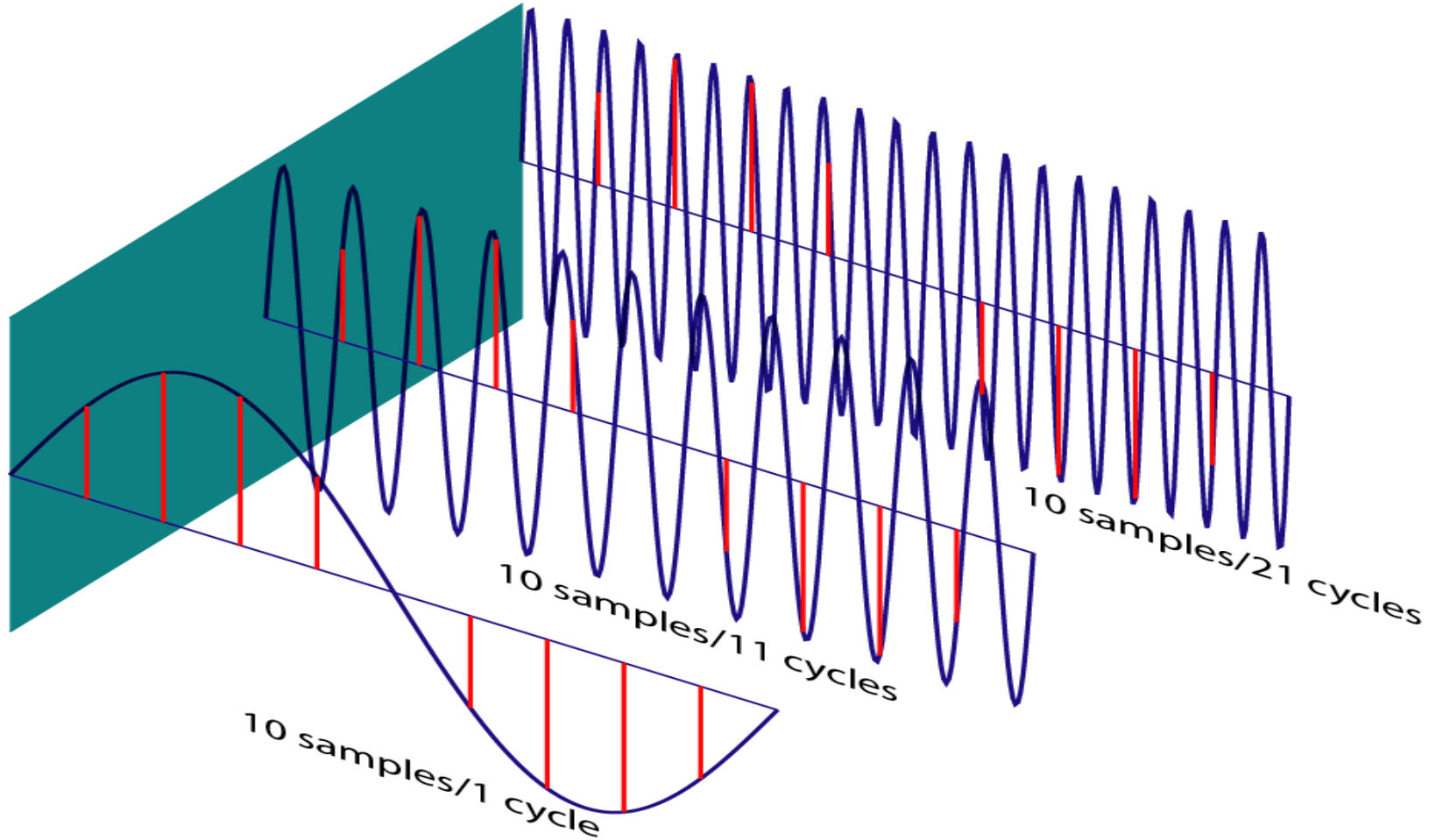3 Different Frequencies, Sampled the Same



Ideal ADC Sampling


Once Sampled, Information is Lost

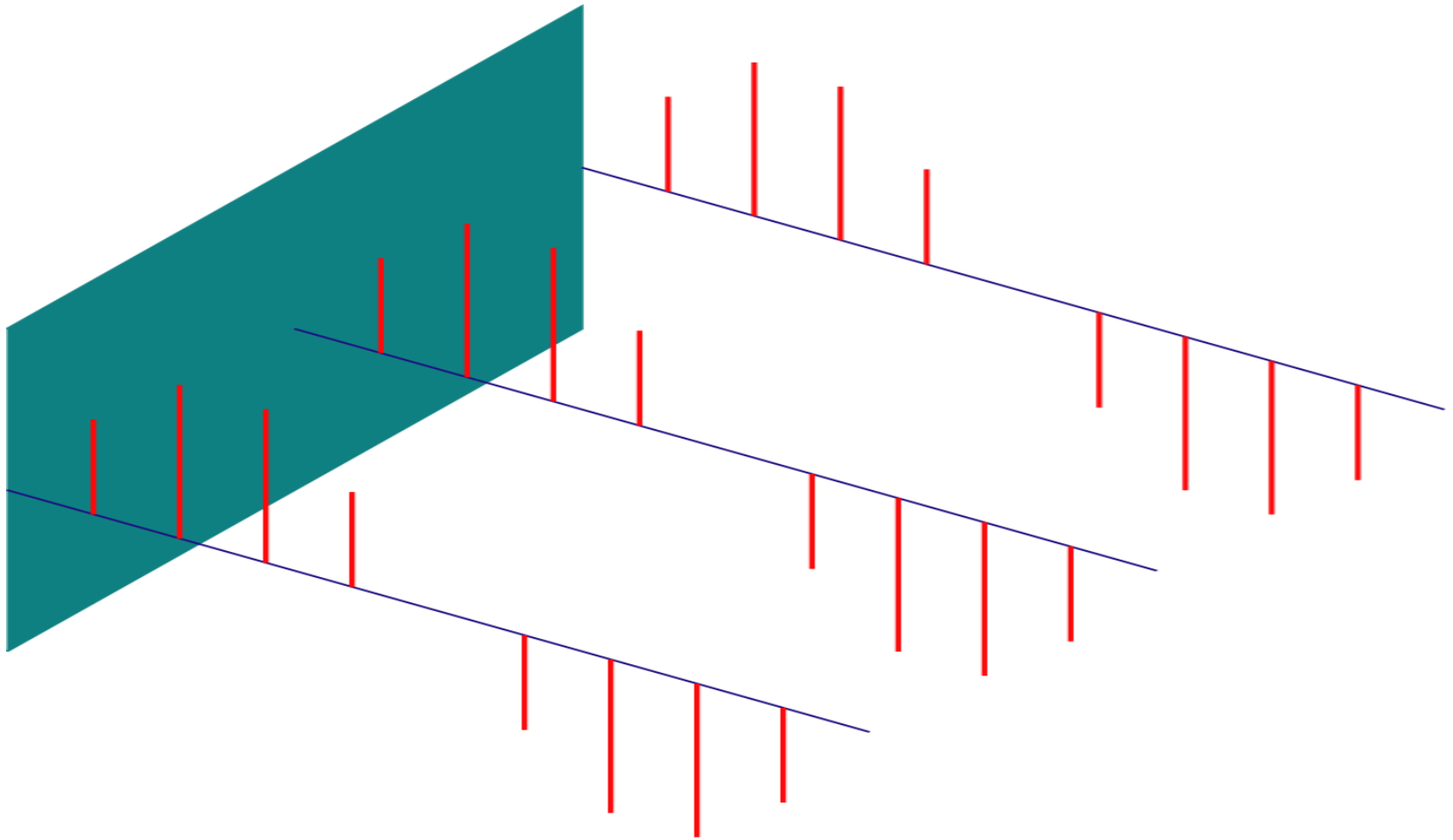


Nyquist's Criteria

- ▶ A signal with a maximum frequency f_a must be sampled at a rate $f_s > 2f_a$ or information about the signal will be lost because of aliasing.
- ▶ Aliasing occurs whenever $f_s < 2f_a$
- ▶ A signal which has frequency components between f_a and f_b must be sampled at a rate $f_s > 2(f_b - f_a)$ in order to prevent alias components from overlapping the signal frequencies
- ▶ The concept of aliasing is widely used in communications applications such as direct IF-to-digital conversion.

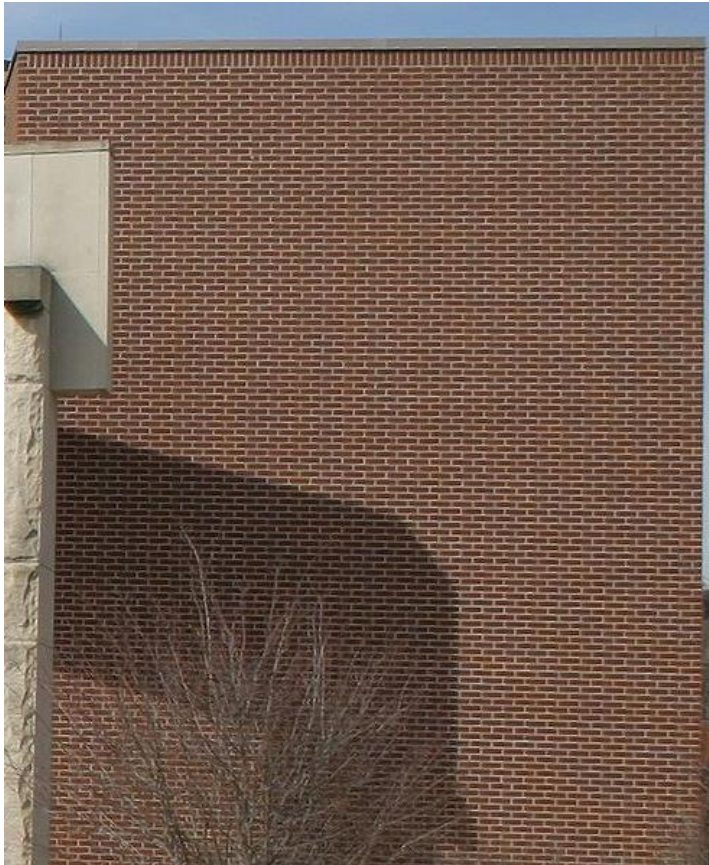Aliasing occurs in Many Domains Spatial, Temporal, etc.




Sampling & Aliasing in the Time Domain

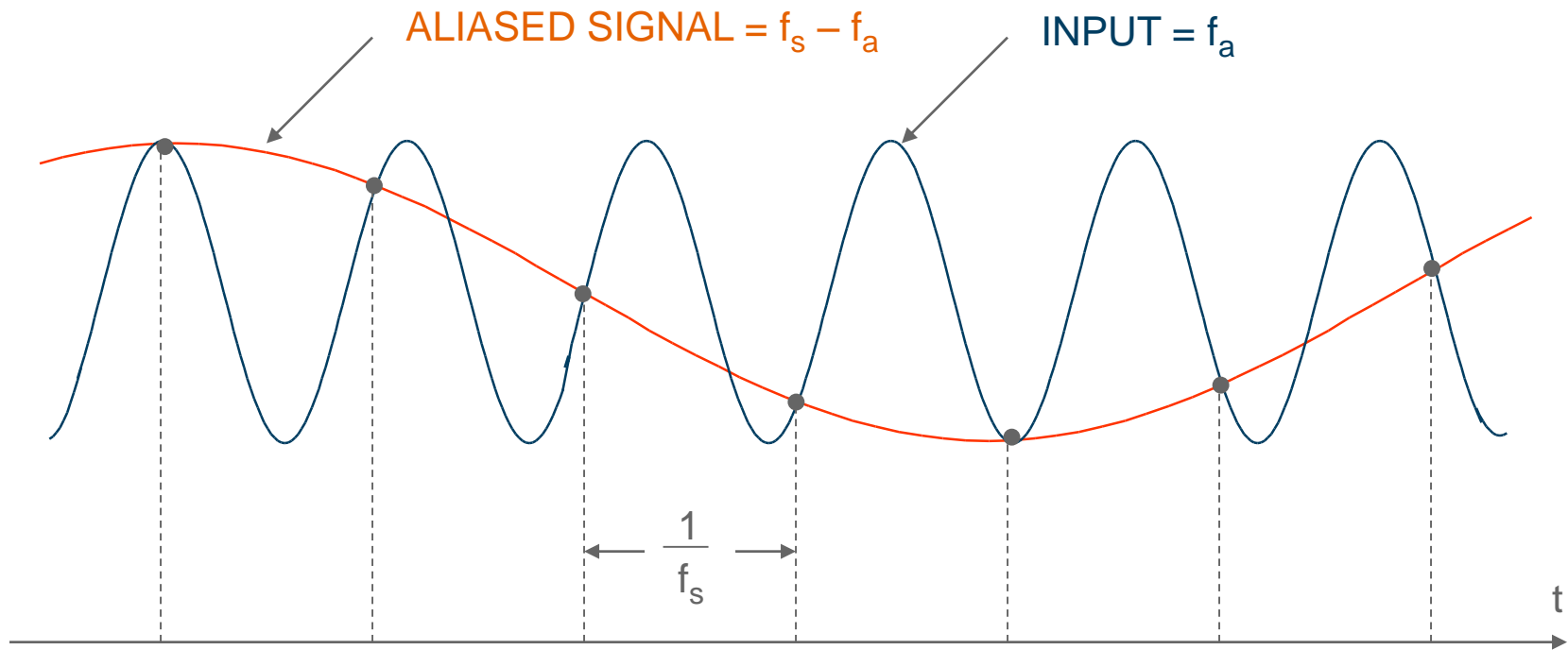

NOTE: f_a IS SLIGHTLY LESS THAN f_s

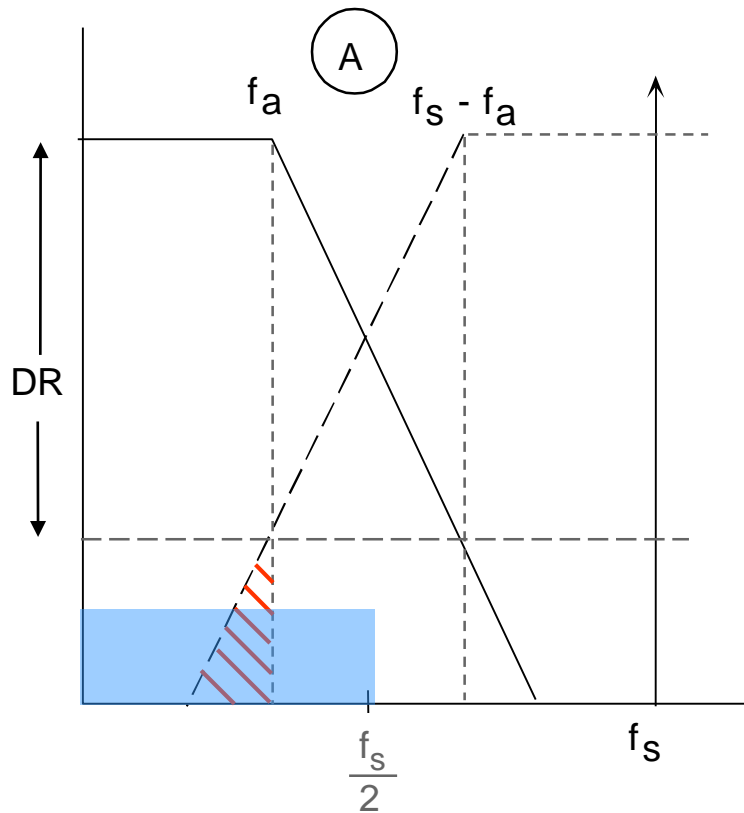Baseband Antialiasing Filter Requirements



STOPBAND ATTENUATION = DR

TRANSITION BAND: f_a to $f_s - f_a$


CORNER FREQUENCY: f_a

Anti-Alias Filter Prevents Aliasing
Contributes to Dynamic Range


Anti-Alias Filter Objectives

- Brick Wall (Steep/Deep Rolloff)
- Linear Passband
- Linear Phase

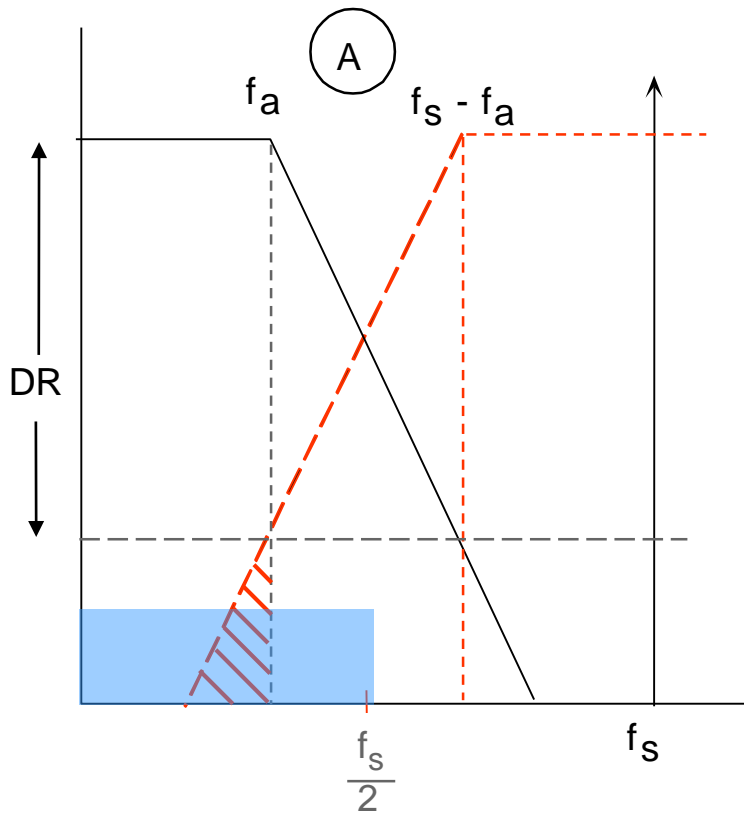Oversampling Relaxes Requirements on Baseband Antialiasing Filter




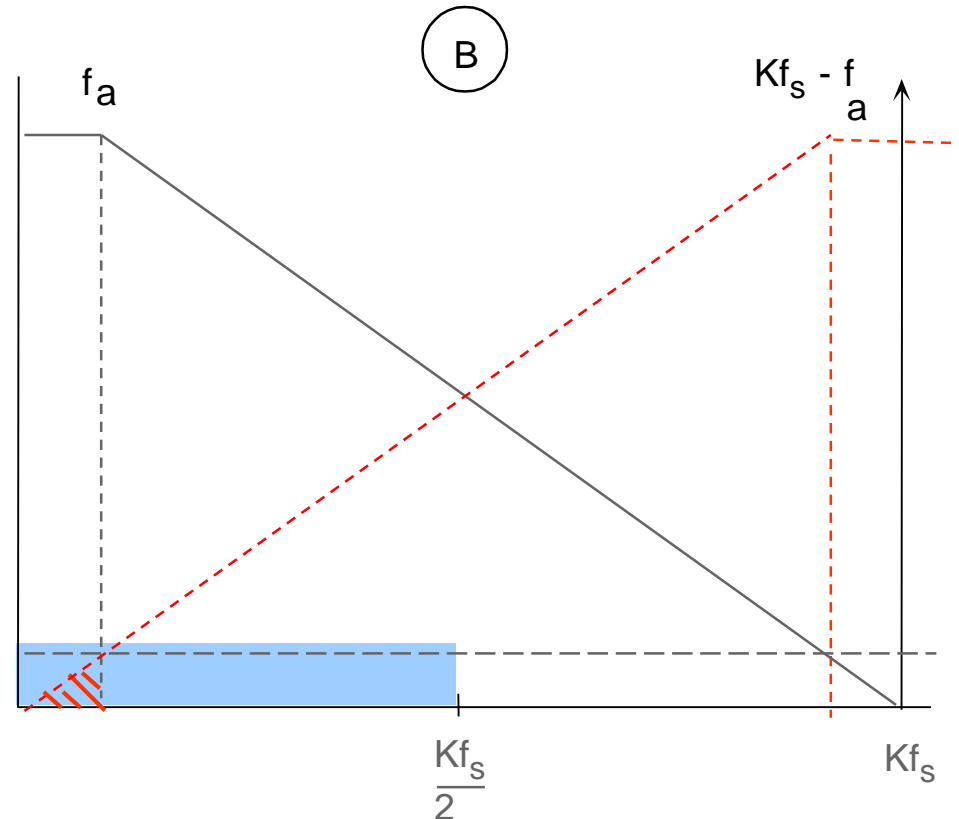STOPBAND ATTENUATION = DR
TRANSITION BAND: f_a to $f_s - f_a$
CORNER FREQUENCY: f_a




STOPBAND ATTENUATION = DR
TRANSITION BAND: f_a to $Kf_s - f_a$
CORNER FREQUENCY: f_a

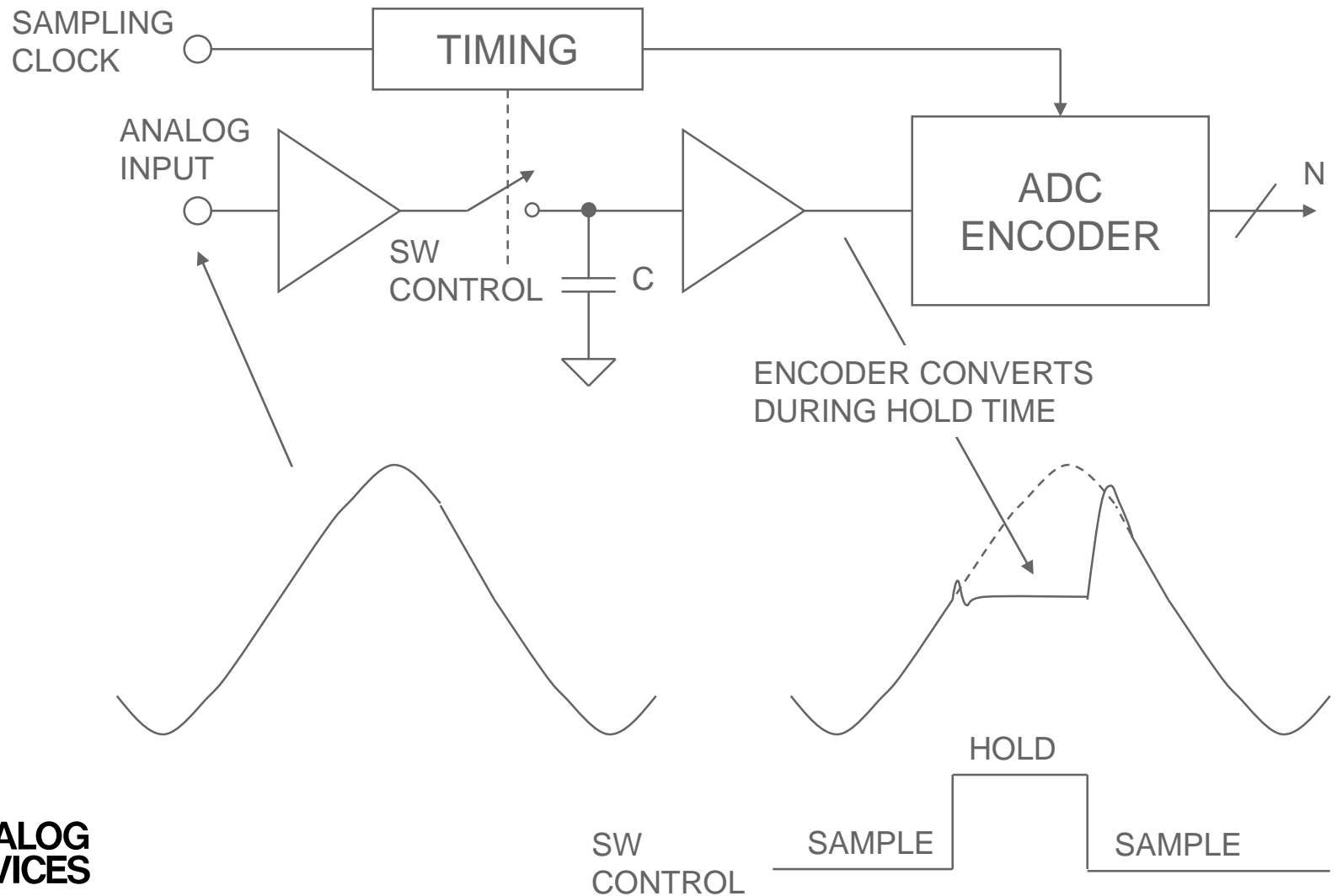Sample-and-Hold Function Required for Digitizing AC Signals



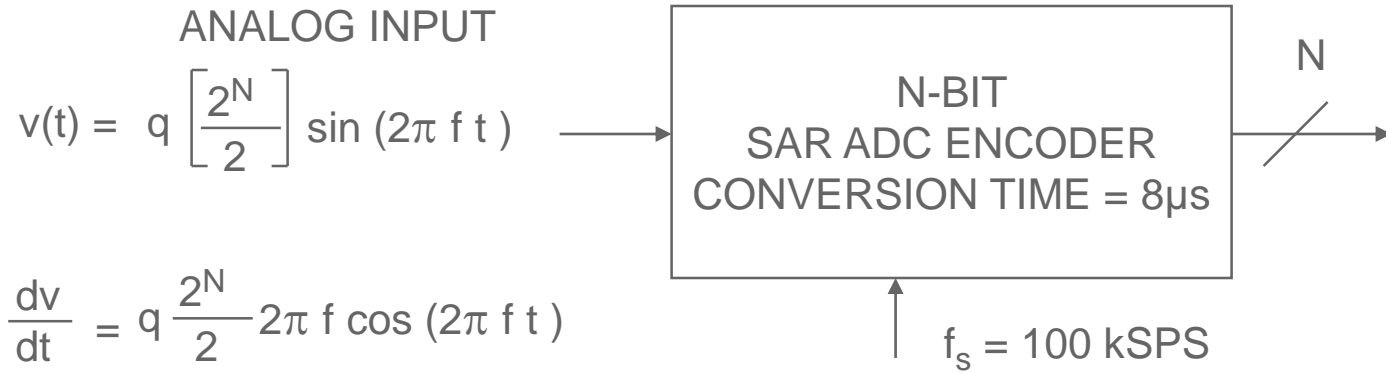Input Frequency Limitations of Non-Sampling ADC (Encoder)



$$\frac{dv}{dt} = q \frac{2^N}{2} 2\pi f \cos(2\pi f t)$$

$$\left. \frac{dv}{dt} \right|_{\max} = q 2^{(N-1)} 2\pi f$$

$$f_{\max} = \frac{\left. \frac{dv}{dt} \right|_{\max}}{2^{(N-1)} 2\pi q}$$

$$f_{\max} = \frac{\left. \frac{dv}{dt} \right|_{\max}}{q\pi 2^N}$$

EXAMPLE:


$$dv = 1 \text{ LSB} = q$$

$$dt = 8\mu\text{s}$$


$$N = 12, \quad 2^N = 4096$$

$$f_{\max} = 9.7 \text{ Hz}$$

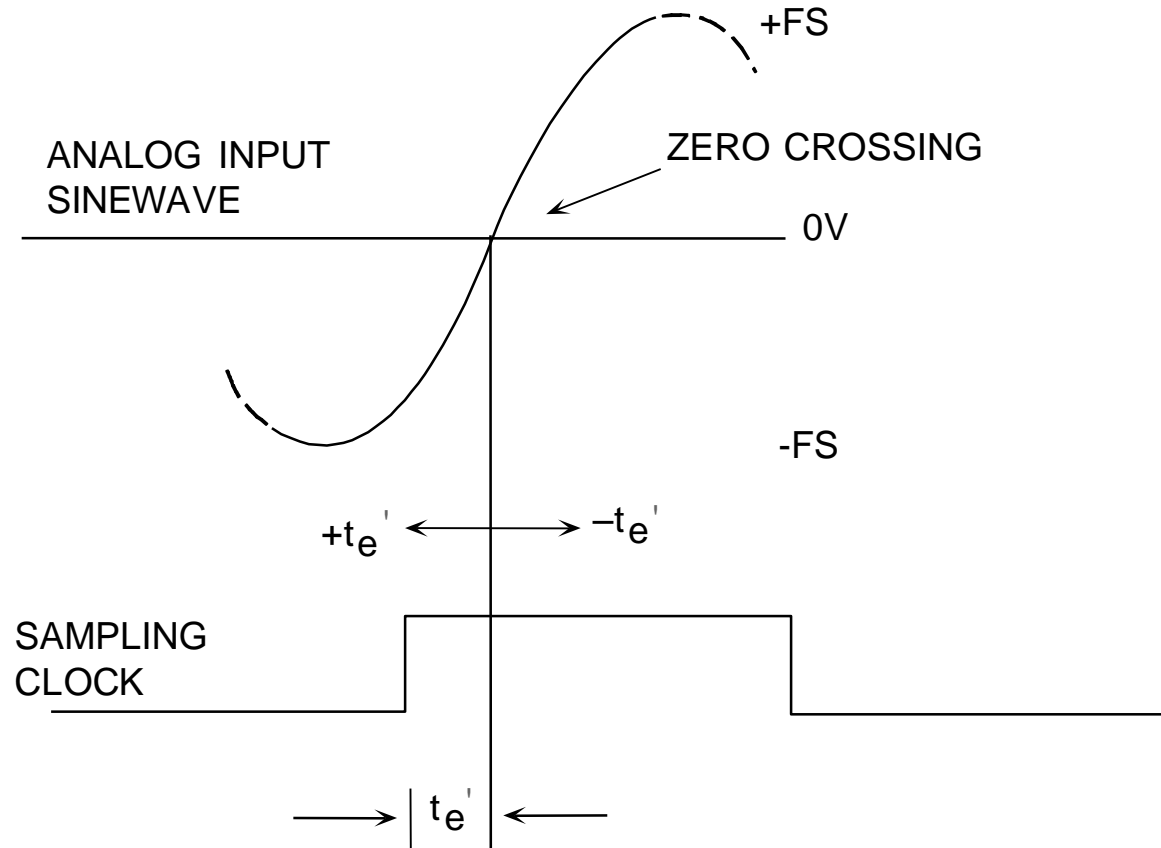
Effective Aperture Delay Time Measured with Respect to ADC Input



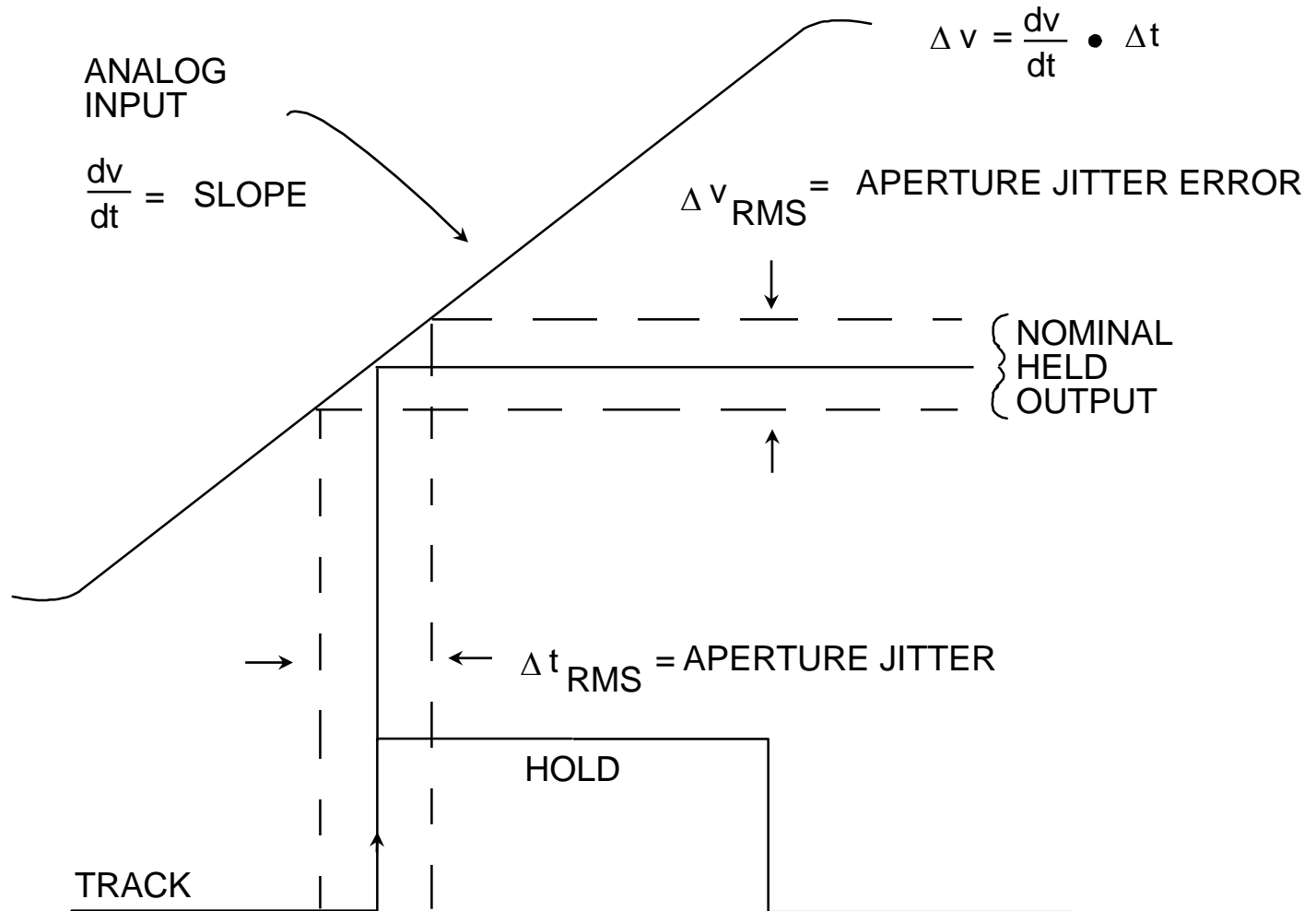
Effects of Aperture Jitter and Sampling Clock Jitter



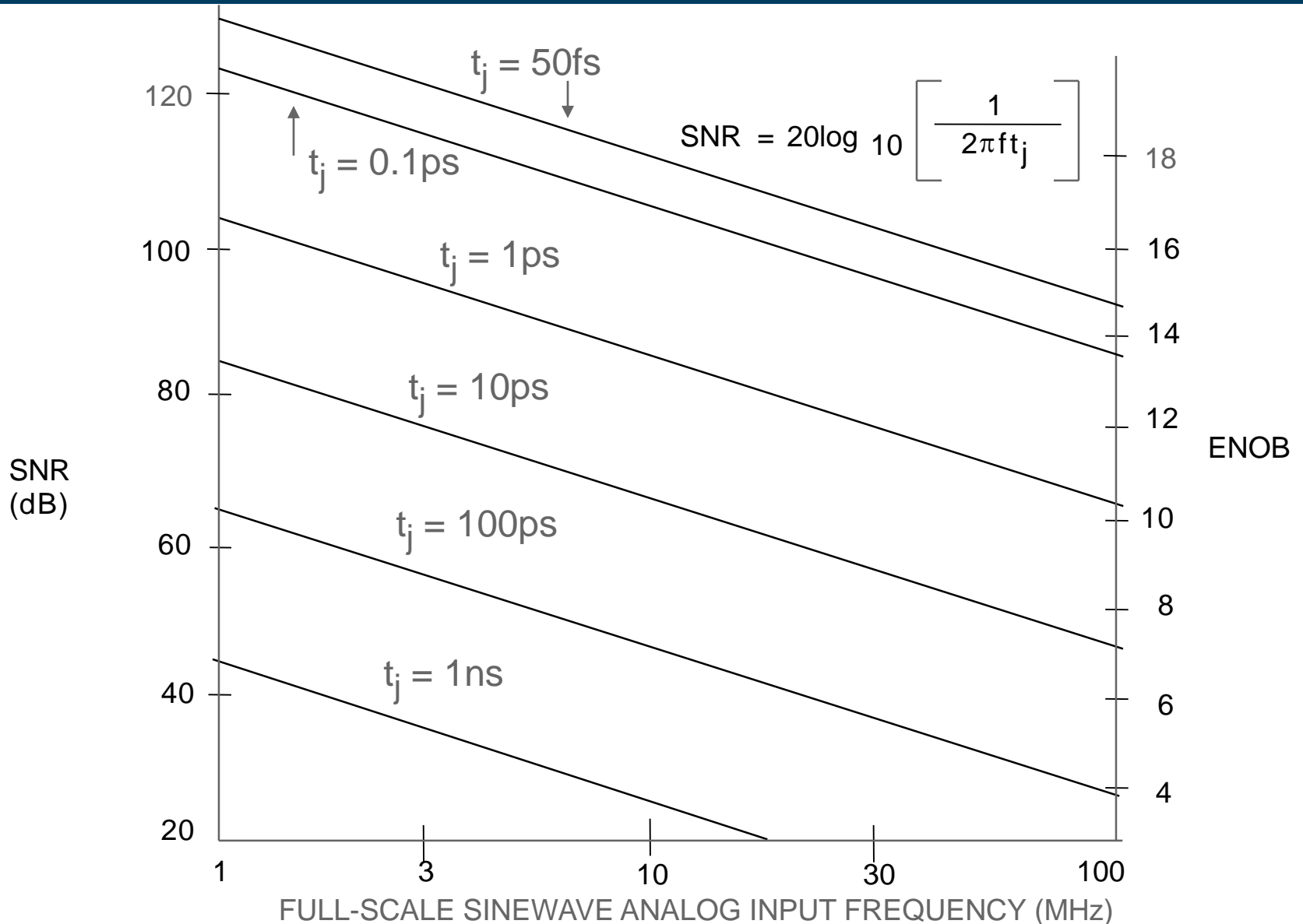
Theoretical SNR and ENOB Due to Jitter vs. Fullscale Sinewave Analog Input Frequency




1-Bit DAC: Changeover Switch (SPDT)

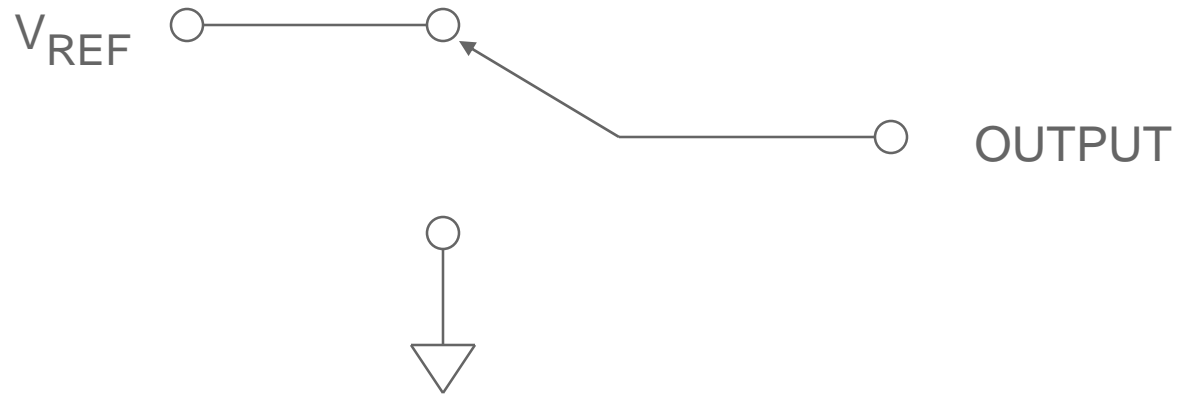

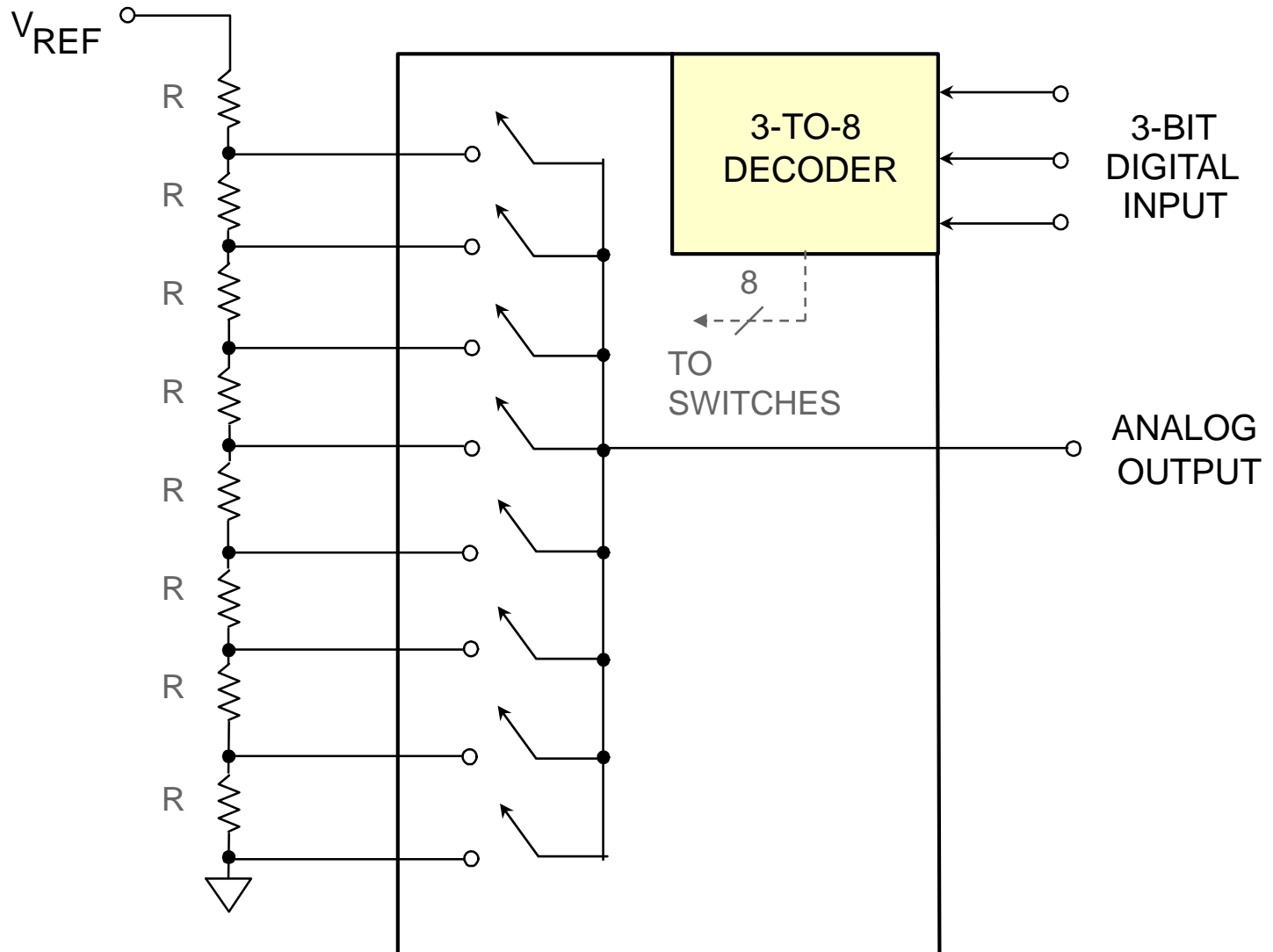
Simplest Voltage Output Thermometer DAC: The Kelvin Divider (AKA - "String DAC")



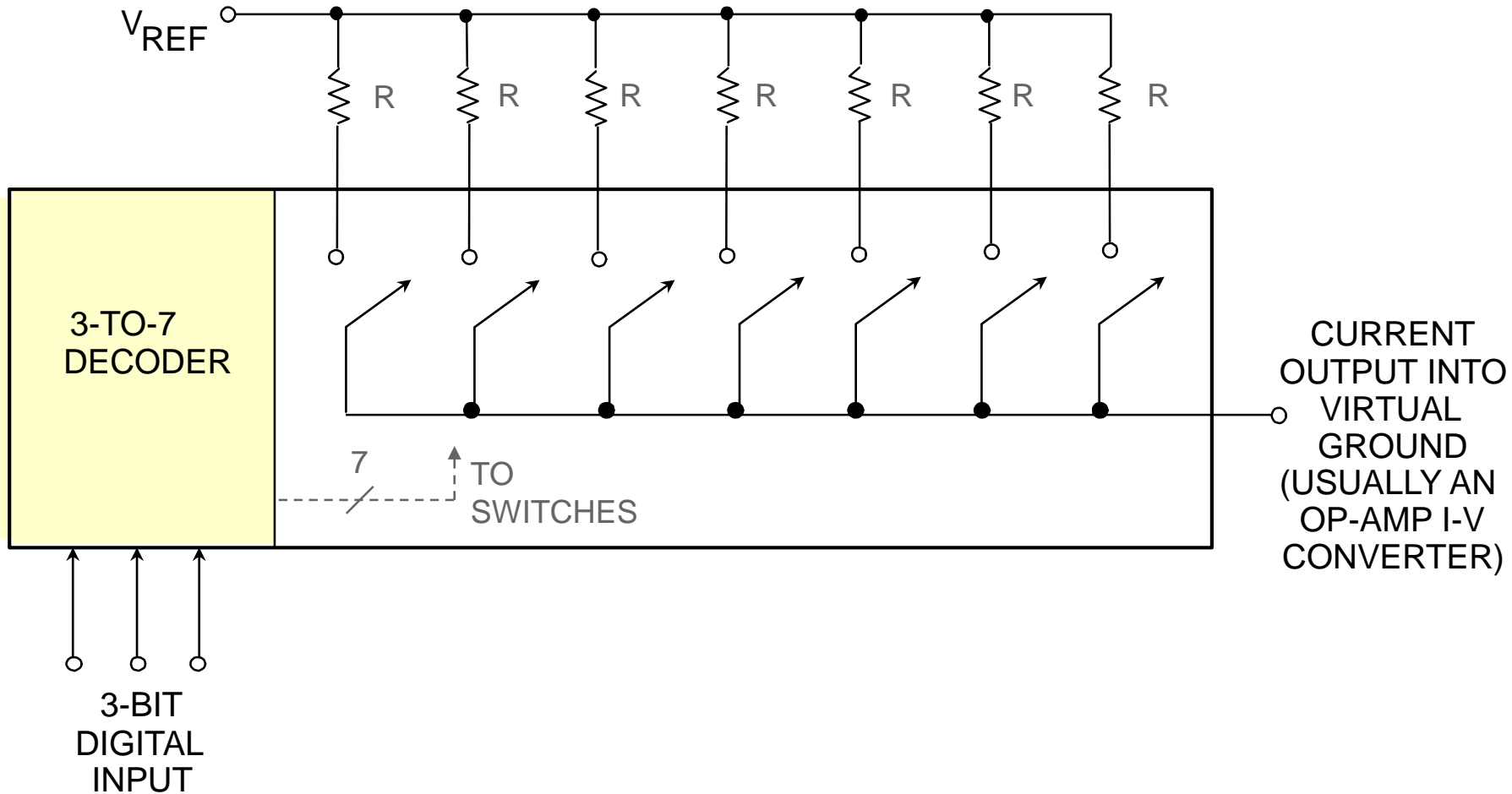
The Simplest Current Output Thermometer (Fully-Decoded) DAC



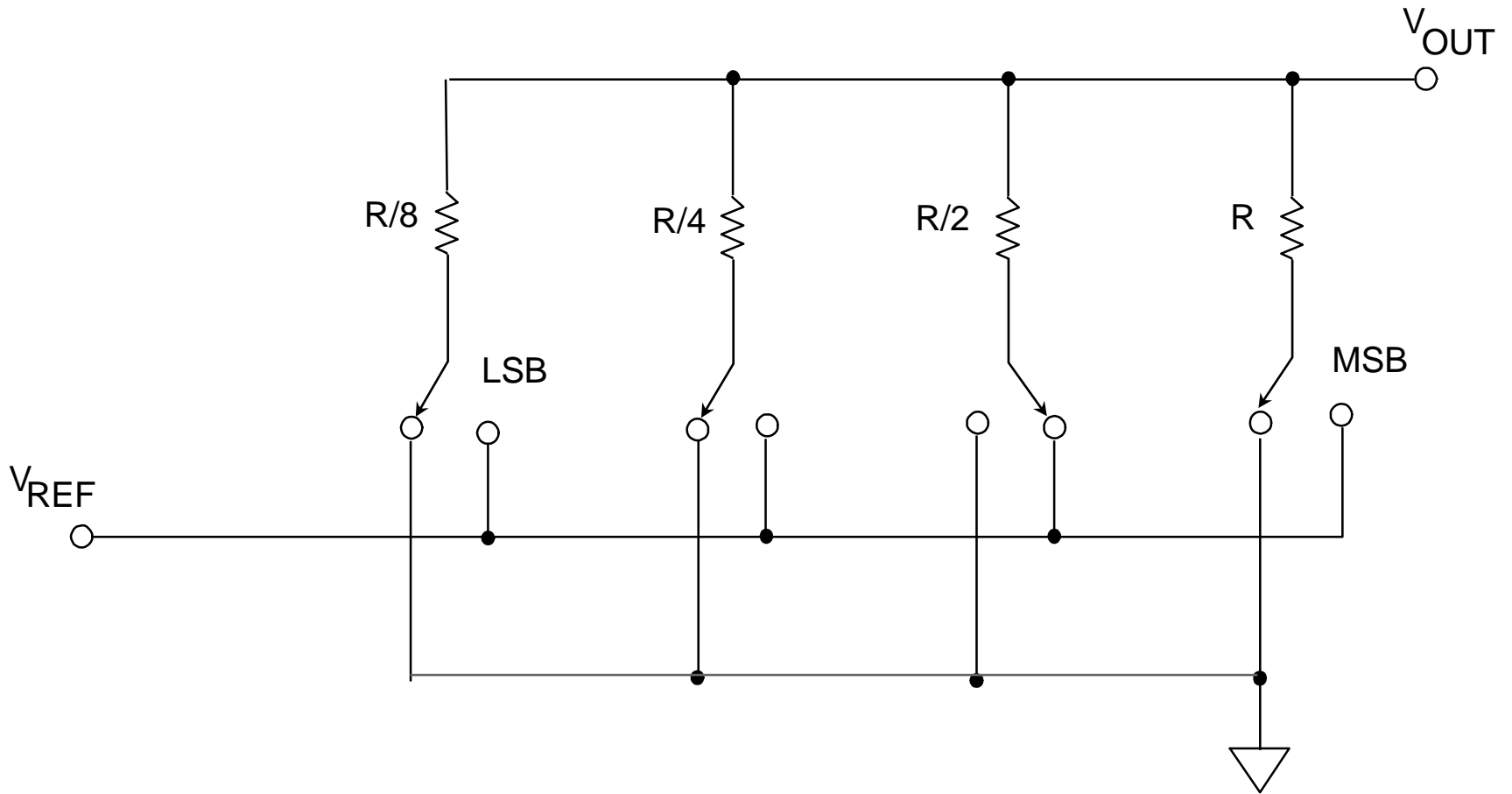Voltage-Mode Binary Weighted Resistor DAC




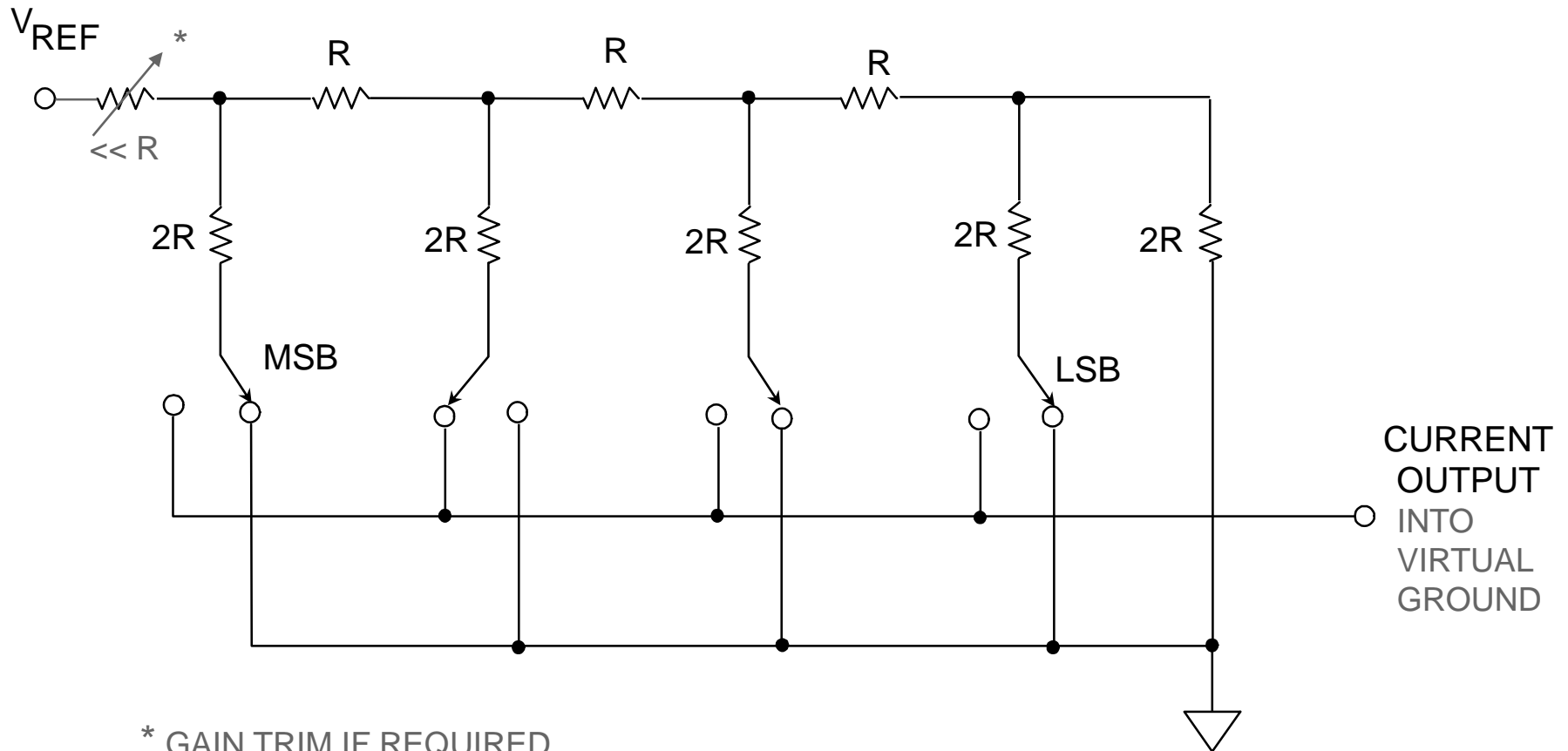Current-Mode R-2R Ladder Network Resistor-Based DAC




Segmented Voltage Output DACs

(A) KELVIN-VARLEY DIVIDER
("STRING DAC")

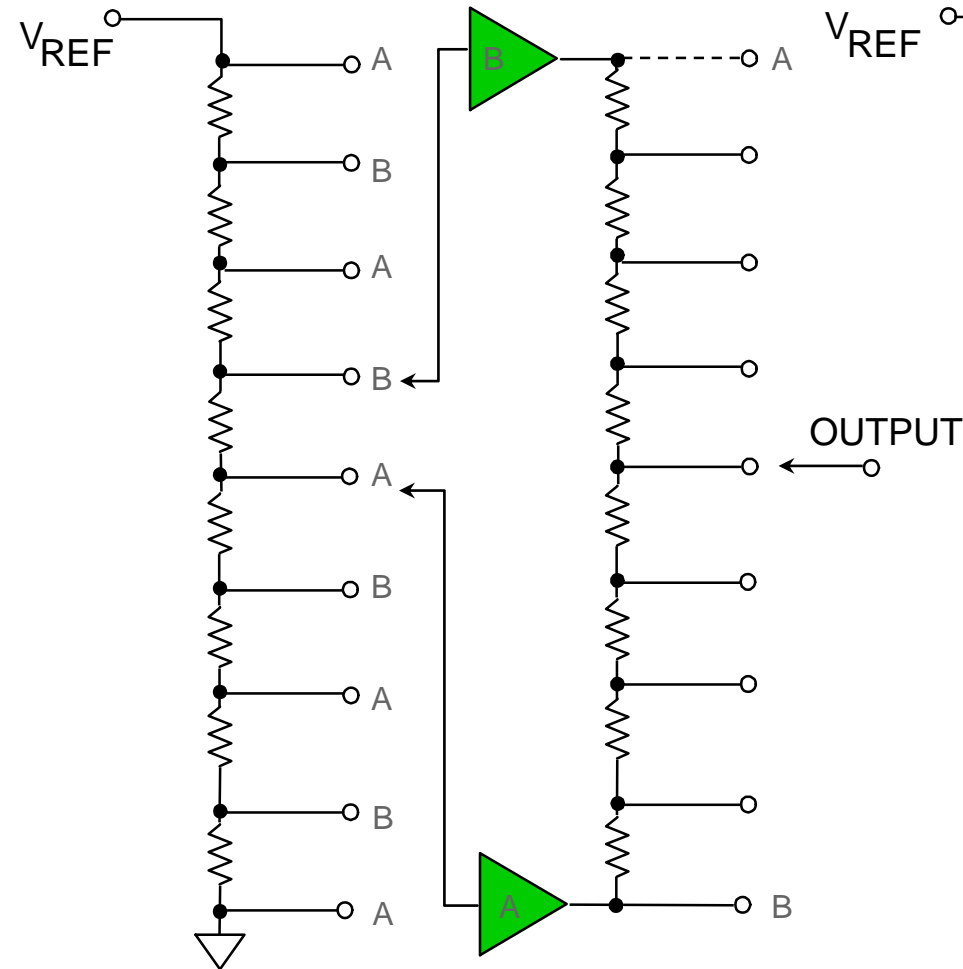


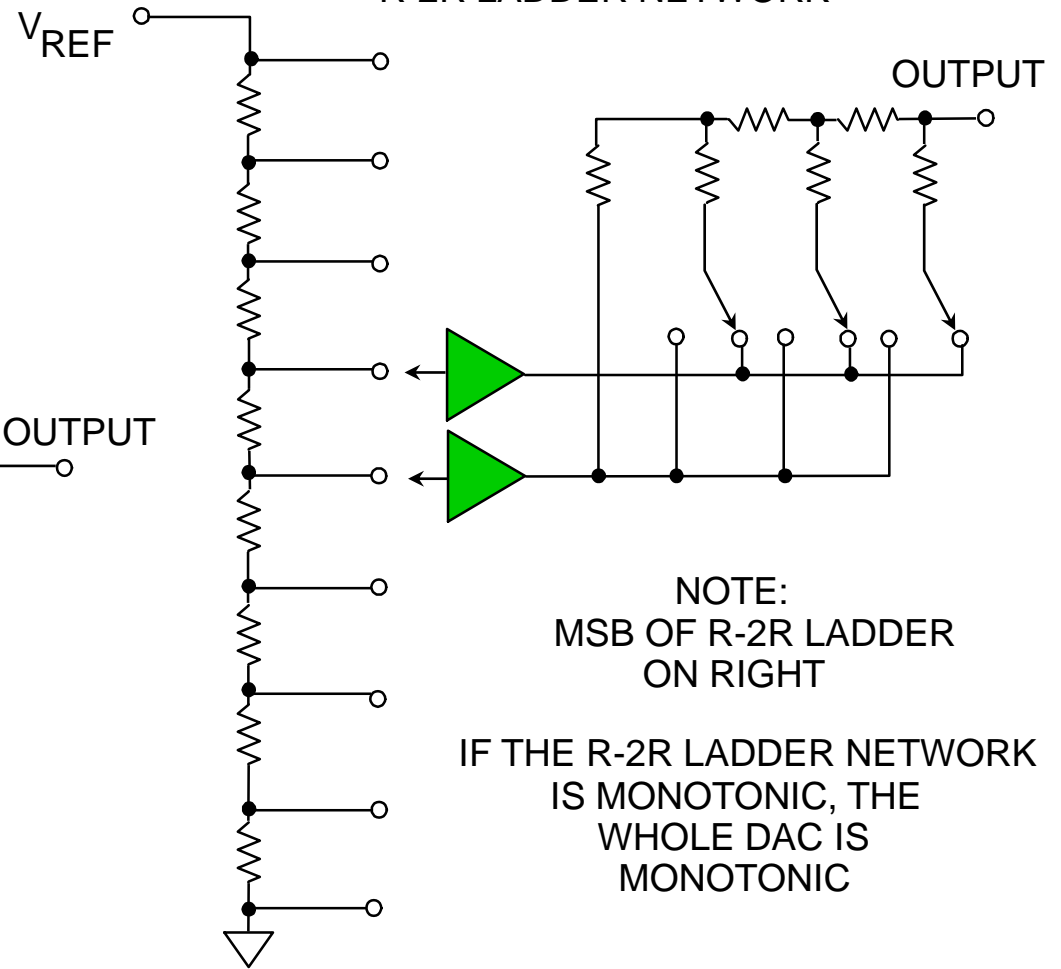(B) KELVIN DIVIDER AND
R-2R LADDER NETWORK



Circuits from the Lab

Multiplying DAC attenuates AC signal

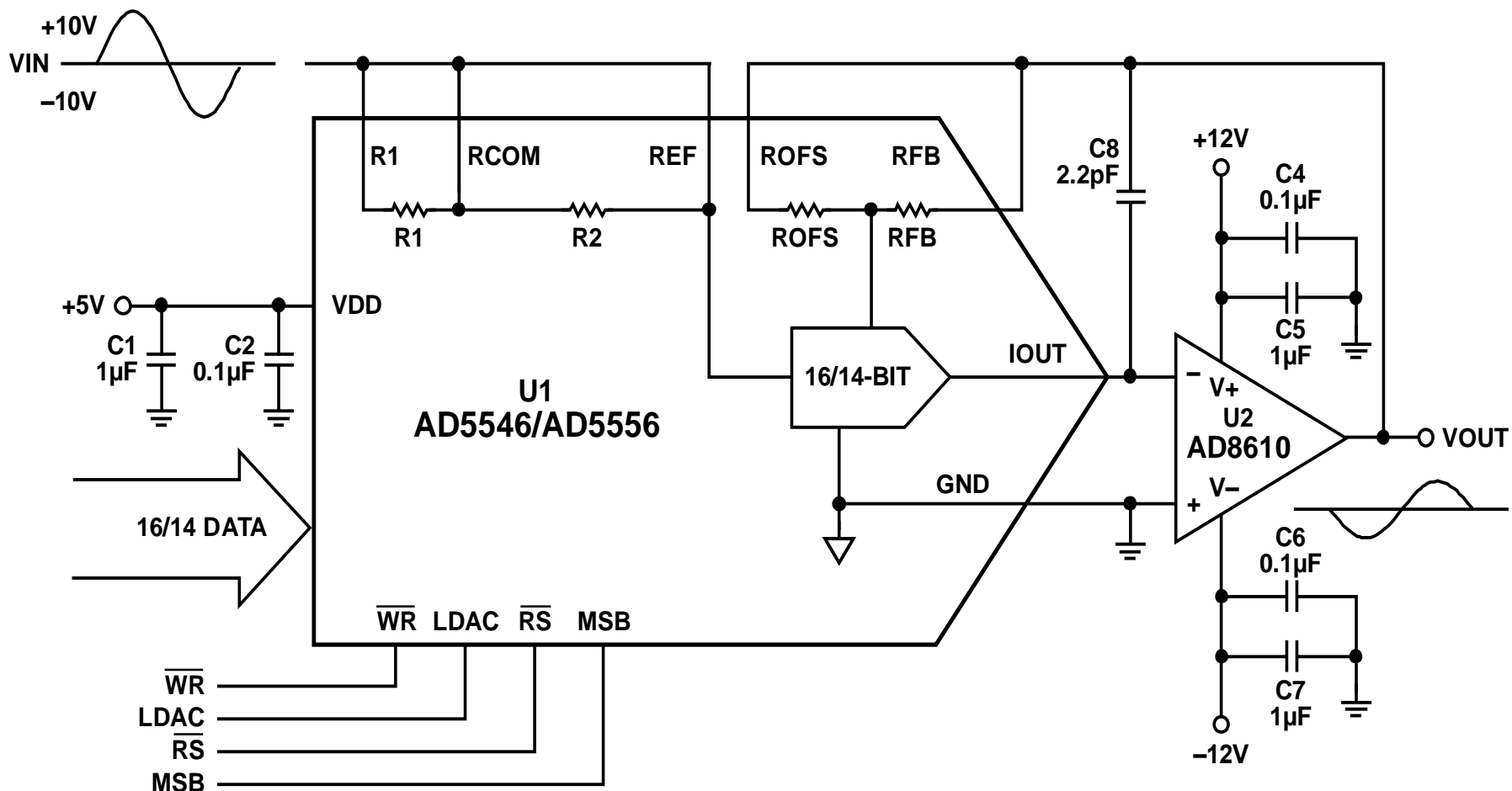


Digital Potentiometer Applications

- ▶ Amplifier and other component adjustment
 - Connect across offset-adjust pins
 - Gain adjustment or fine tuning
- ▶ System calibration
 - Digital pots inserted in strategic system locations
 - System tune-up automatically or manually
 - Non-volatile RAM setting returns on system power-up
 - RAM can be one-time program or re-programmable
 - Settings can be stored centrally and transmitted for system re-adjustment


Circuits from the Lab

Digital Potentiometer Gain Adjustment

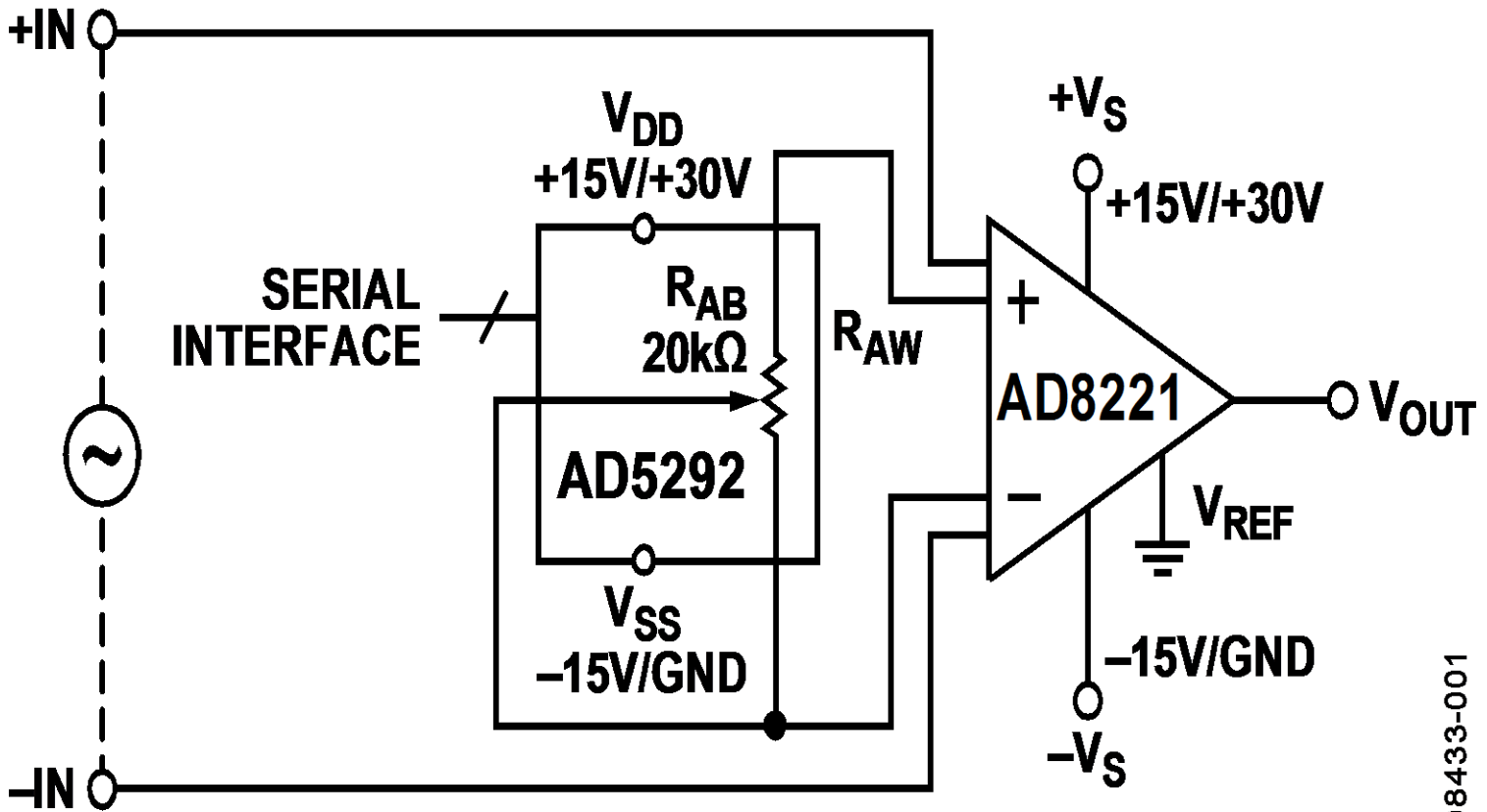


08433-001

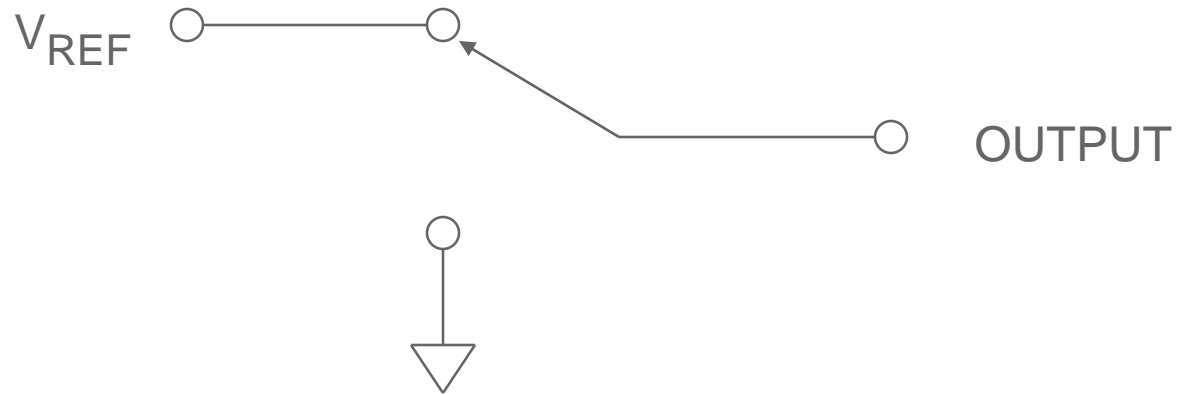
1-Bit DAC: Highly-sophisticated Digital-Audio DAC



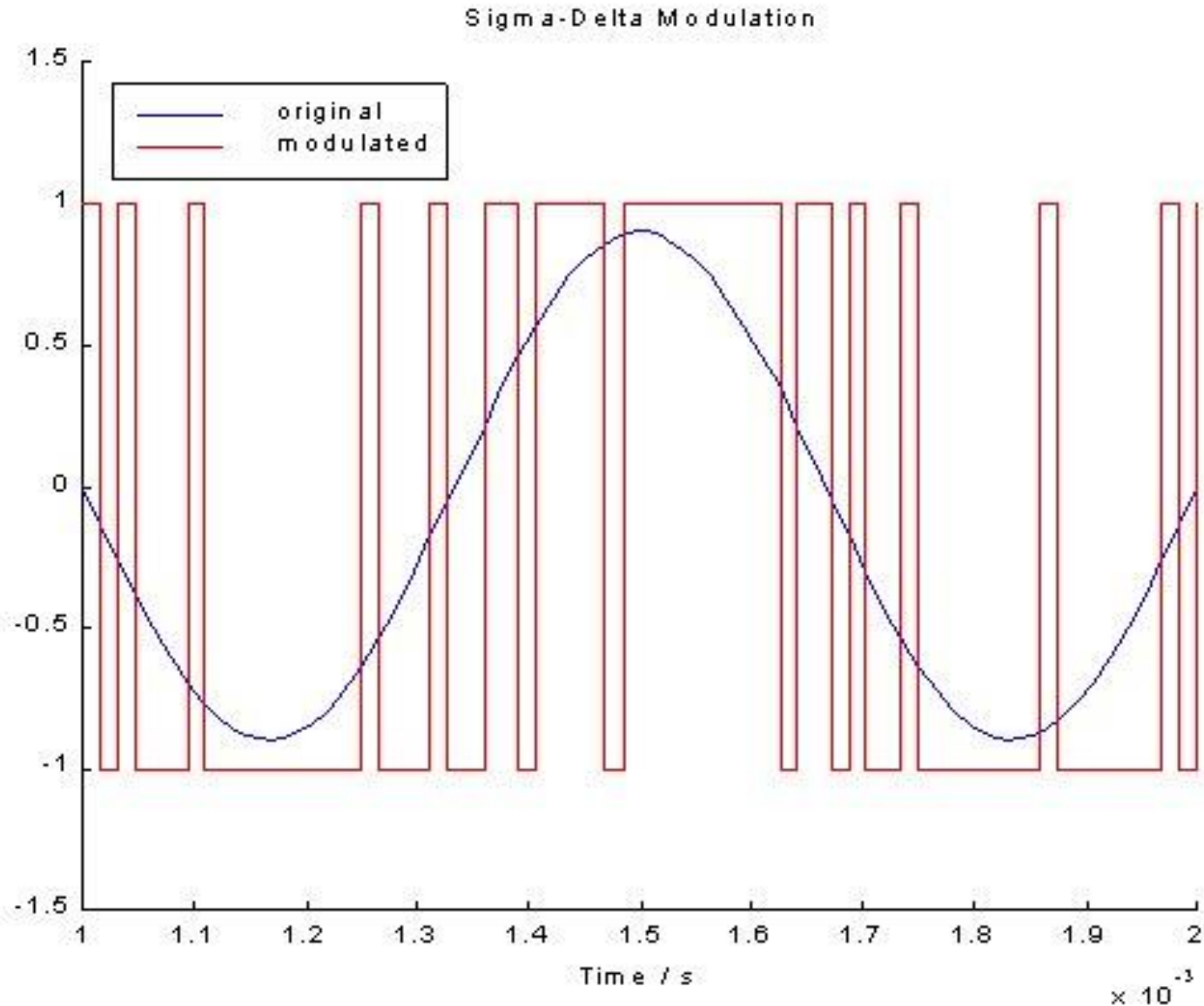
Sampled Data System: Sampling and Quantization



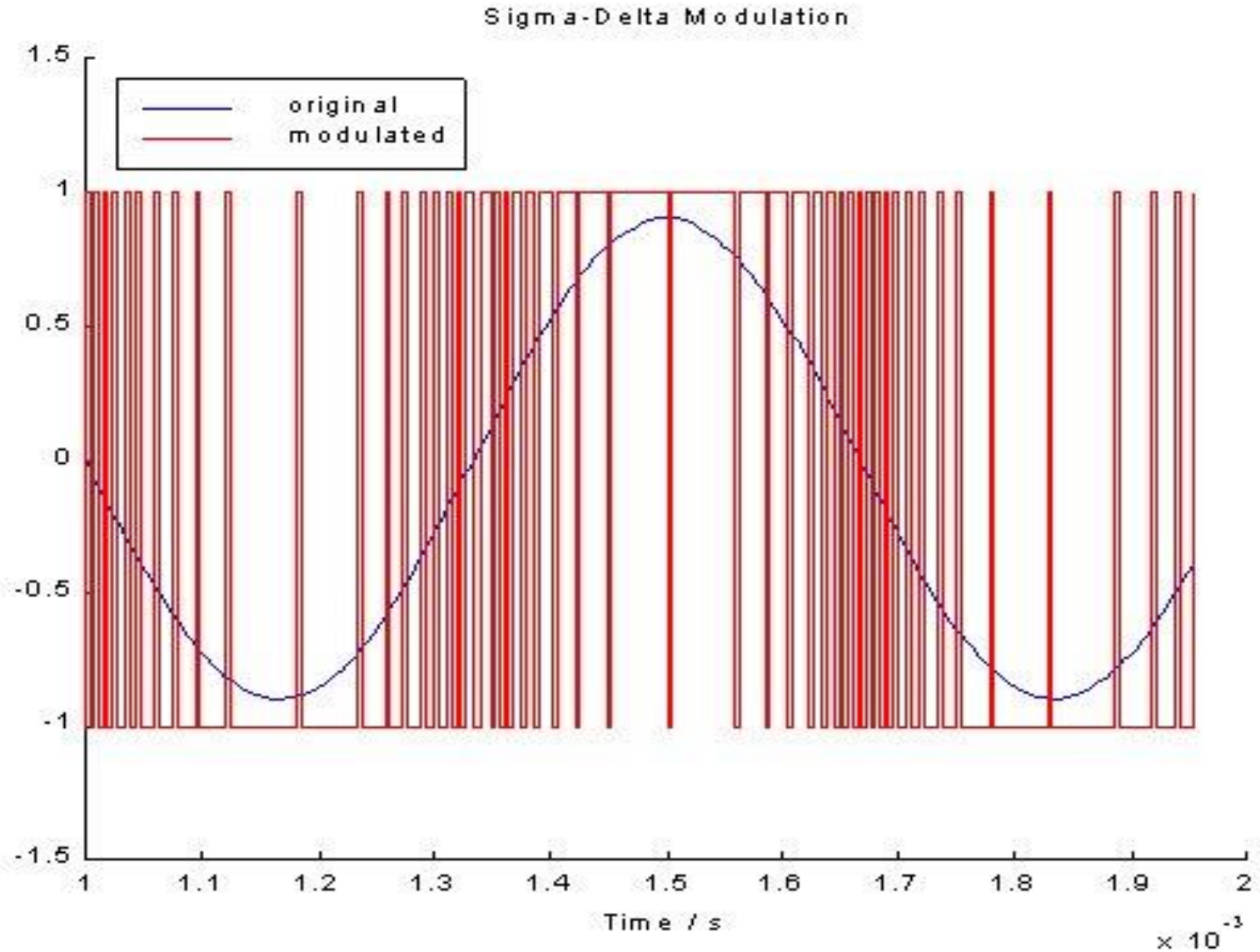
Sampled Data System: Sampling and Quantization




Basic ADC with External Reference

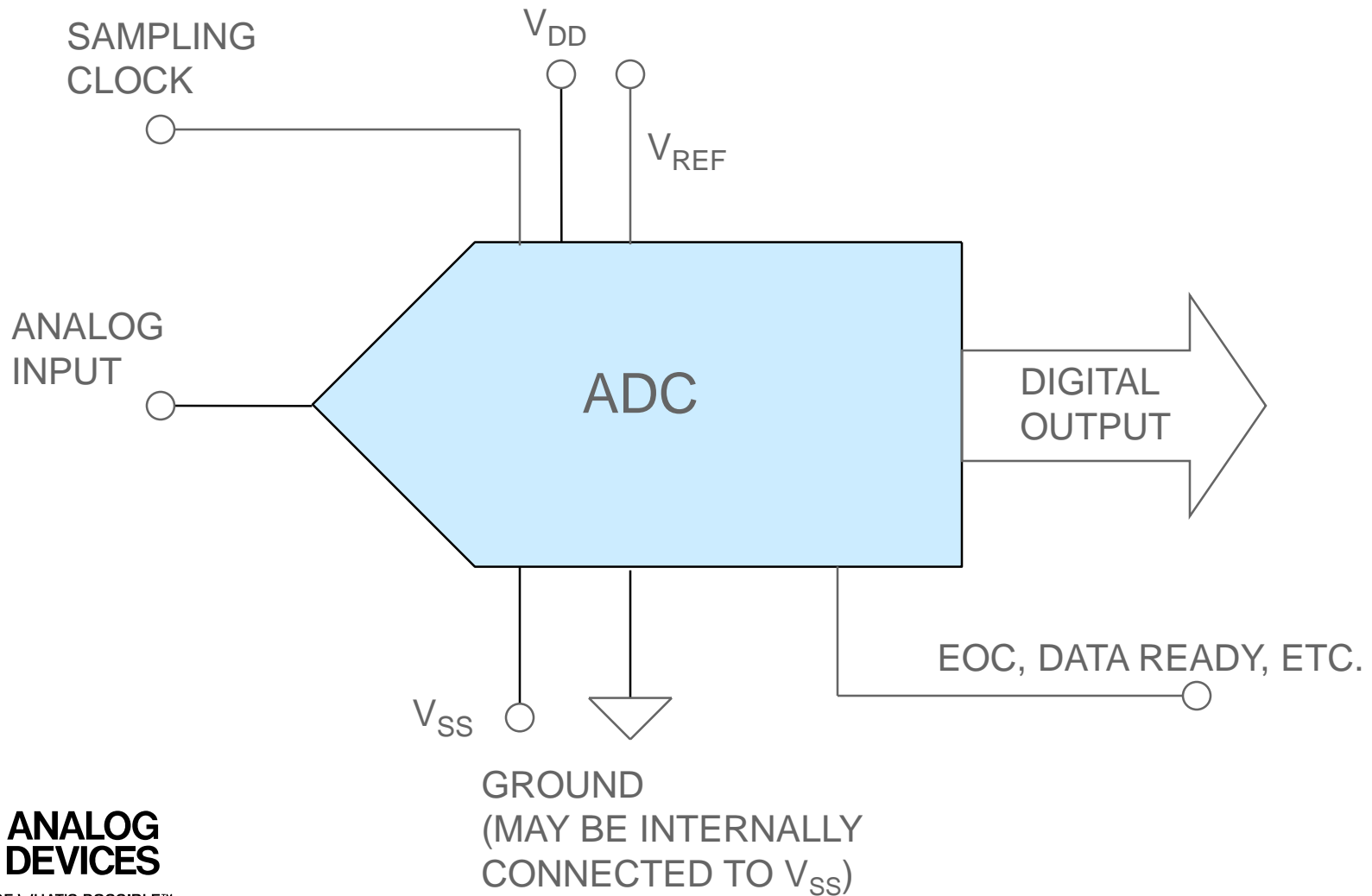



The Comparator: A 1-Bit ADC

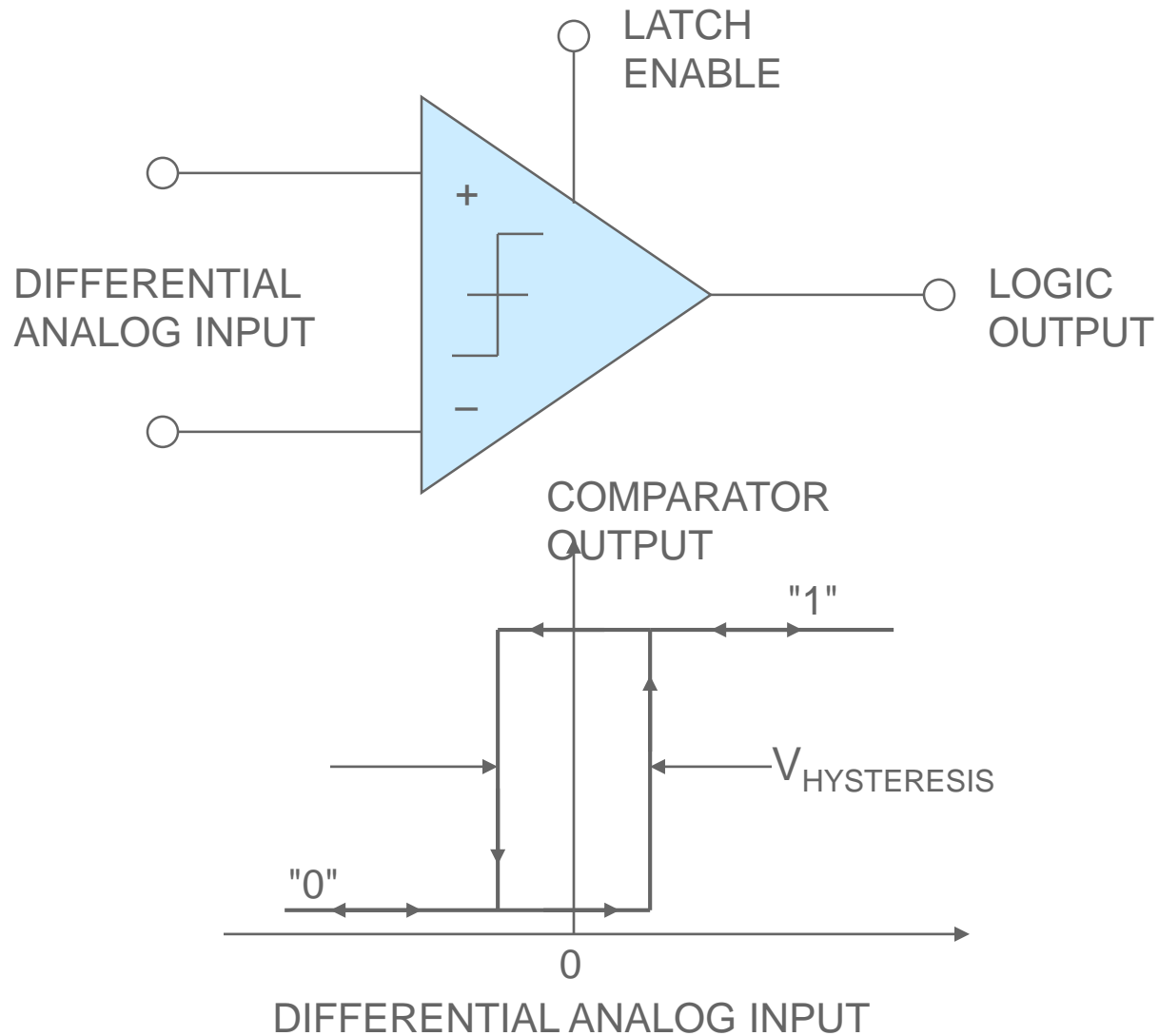

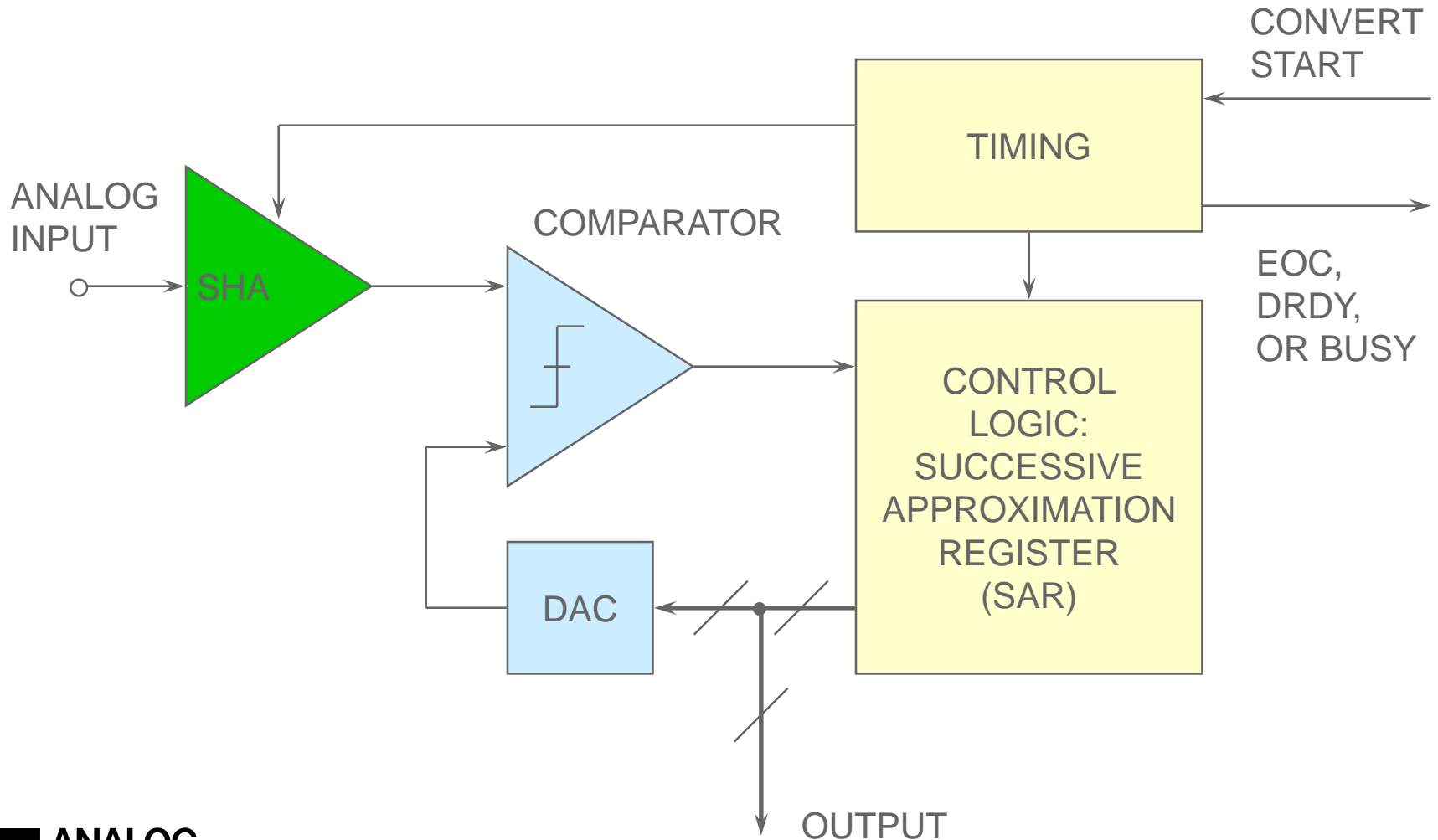Basic Successive Approximation ADC (Feedback Subtraction ADC)



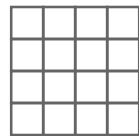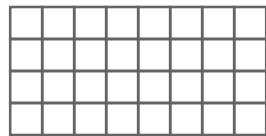Successive Approximation ADC Algorithm Analogy Using Binary Weights



TEST

IS $X \geq 32$?


IS $X \geq (32 + 16)$?

IS $X \geq (32 + 8)$?

IS $X \geq (32 + 8 + 4)$?

IS $X \geq (32 + 8 + 4 + 2)$?

IS $X \geq (32 + 8 + 4 + 2 + 1)$?

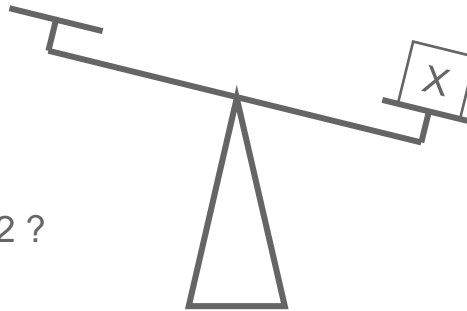

ASSUME $X = 45$

YES RETAIN 32 1

NO REJECT 16 0

YES RETAIN 8 1


YES RETAIN 4 1

NO REJECT 2 0


YES RETAIN 1 1

TOTALS: $X = 32 + 8 + 4 + 1 = 45_{10} = 101101_2$

3-bit All-Parallel (Flash) Converter

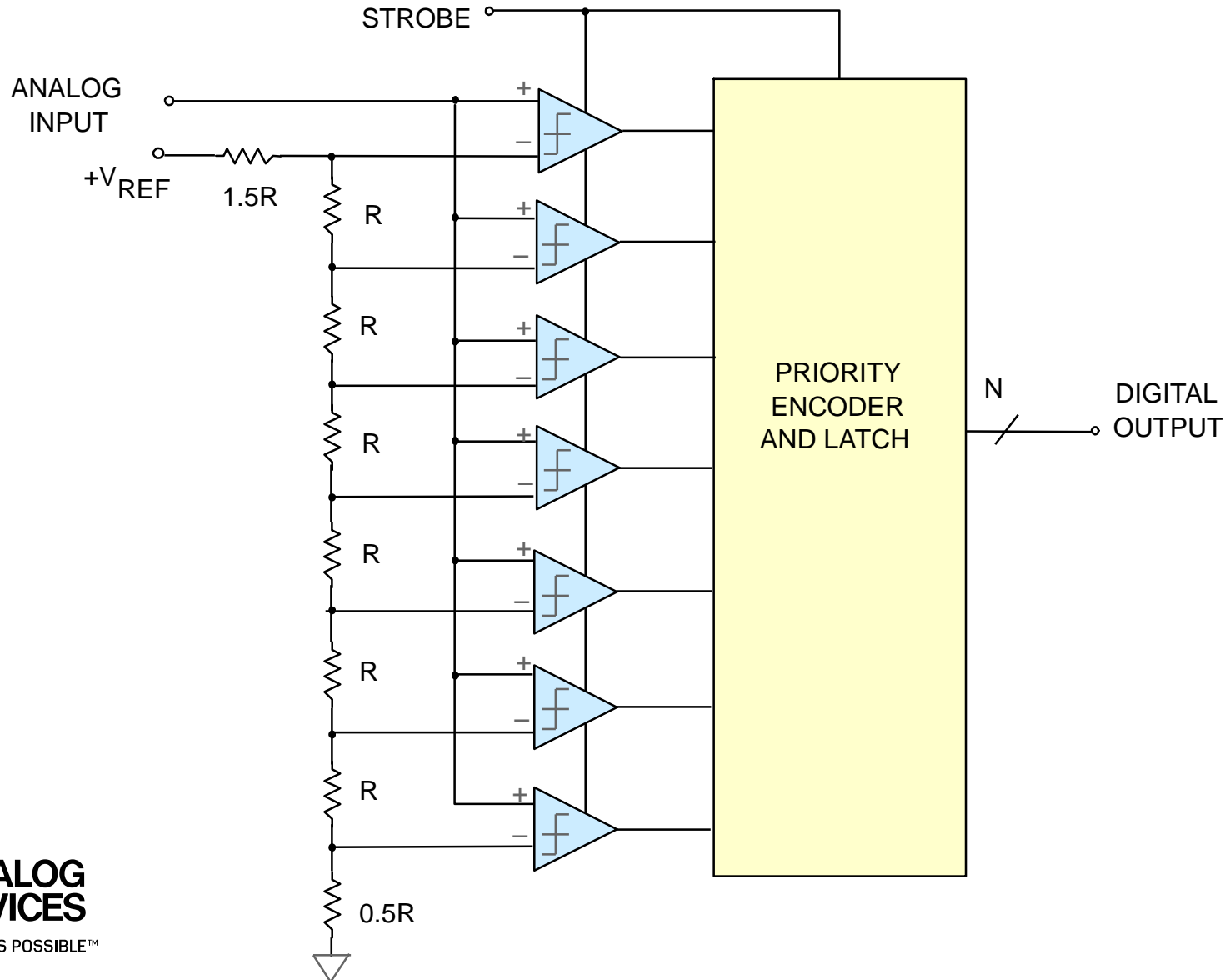

Sigma-Delta ADC - First-Order Modulator

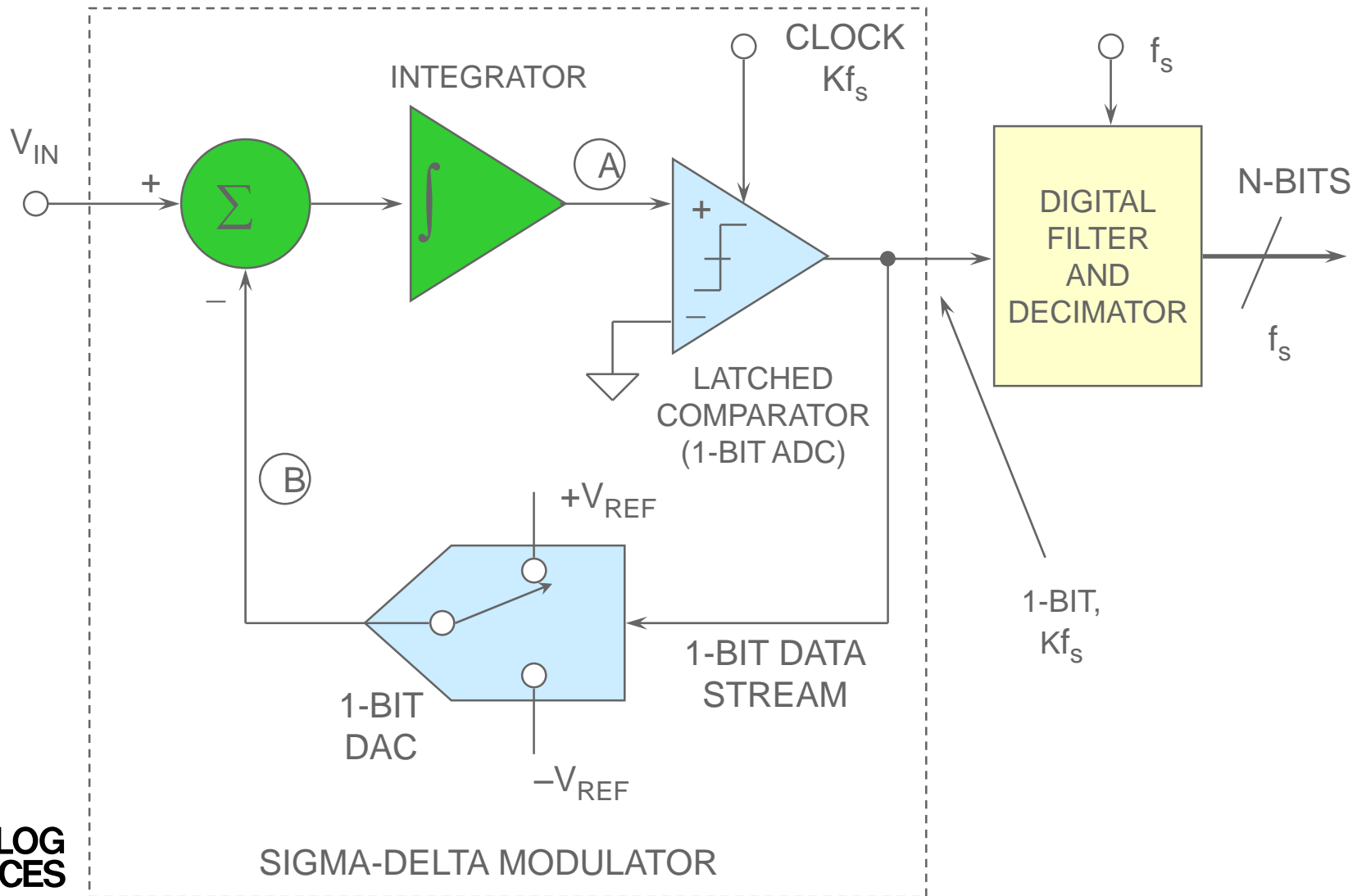

Thank You For Watching!

View Additional Webcasts at
www.analog.com/Webcasts

Ask Questions on EngineerZone
ez.analog.com/Webcasts

Order ADI Products on Avnet
www.avnet.com



AHEAD OF WHAT'S POSSIBLE™