

LED Lighting Proposal with IFX solution




2014-08-26




Our Application Focus is mainly General Lighting



Professional Lighting

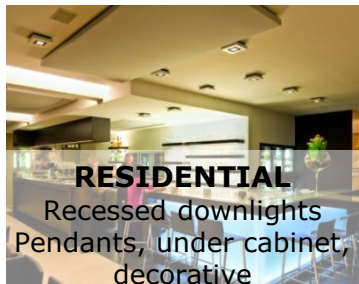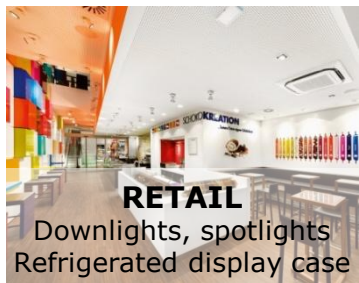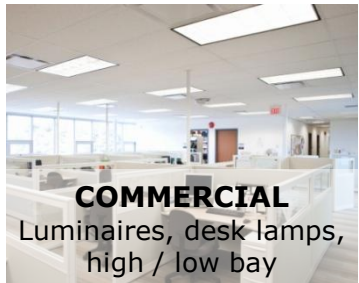

Architectural & Entertainment

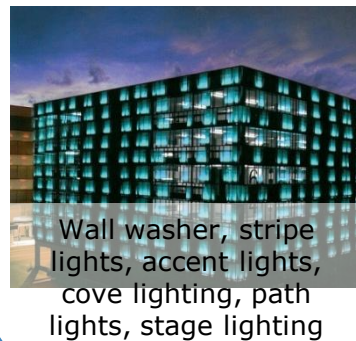


Outdoor area lighting



Replacement Lamps




Others

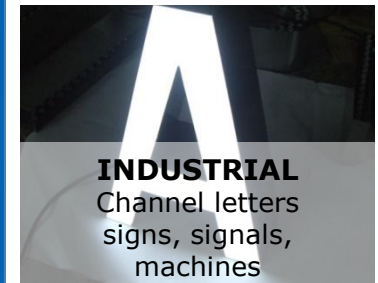

INDEX

- 48Watt Flat Lamp Solution
- DC/DC Dimming Solution
- 7Watt, 10Watt MR16 Solution
- Summary

Demo board 35.5mm

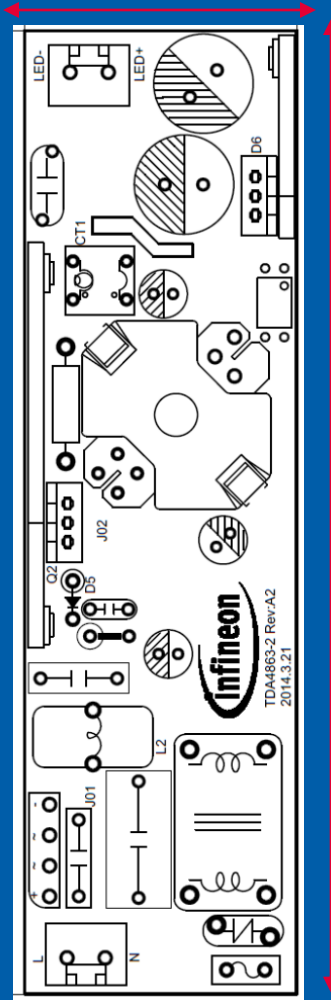

126mm

Operation

Single stage PFC/Flyback

Flexibility

- Universal input voltage range 85Vac – 305Vac
- Wide output voltage range 24V – 48V

Output current

- 1000mA output current
- High accuracy : 3.5%

Efficiency

Benchmark AC/DC efficiency up to 88.5%


PF/THD

- PF up to 0.97
- THD below to 18%


Protection

- Over Voltage protection
- Short Circuit Protection
- Over Power Protection


Typical Application Circuit

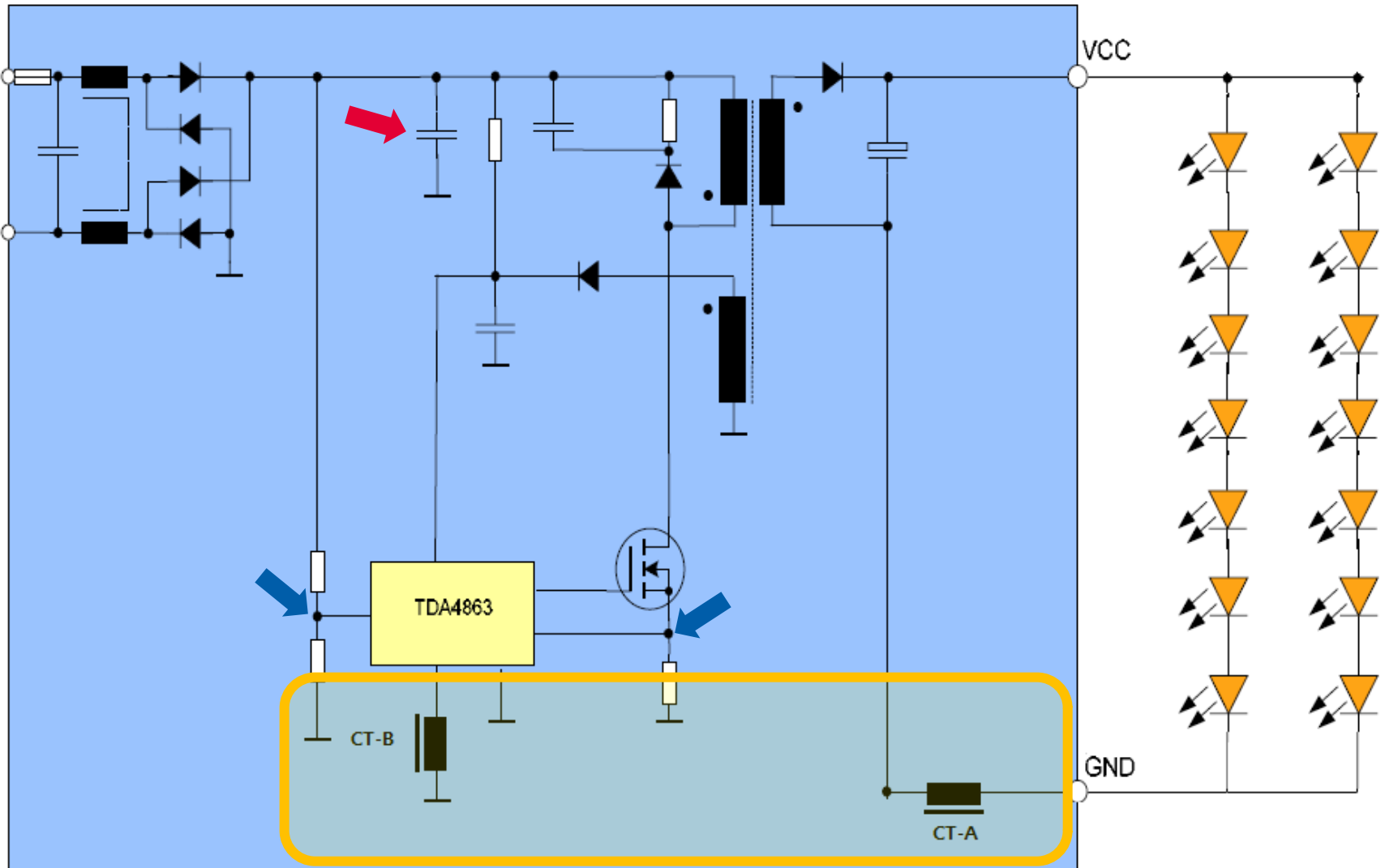


Load regulation

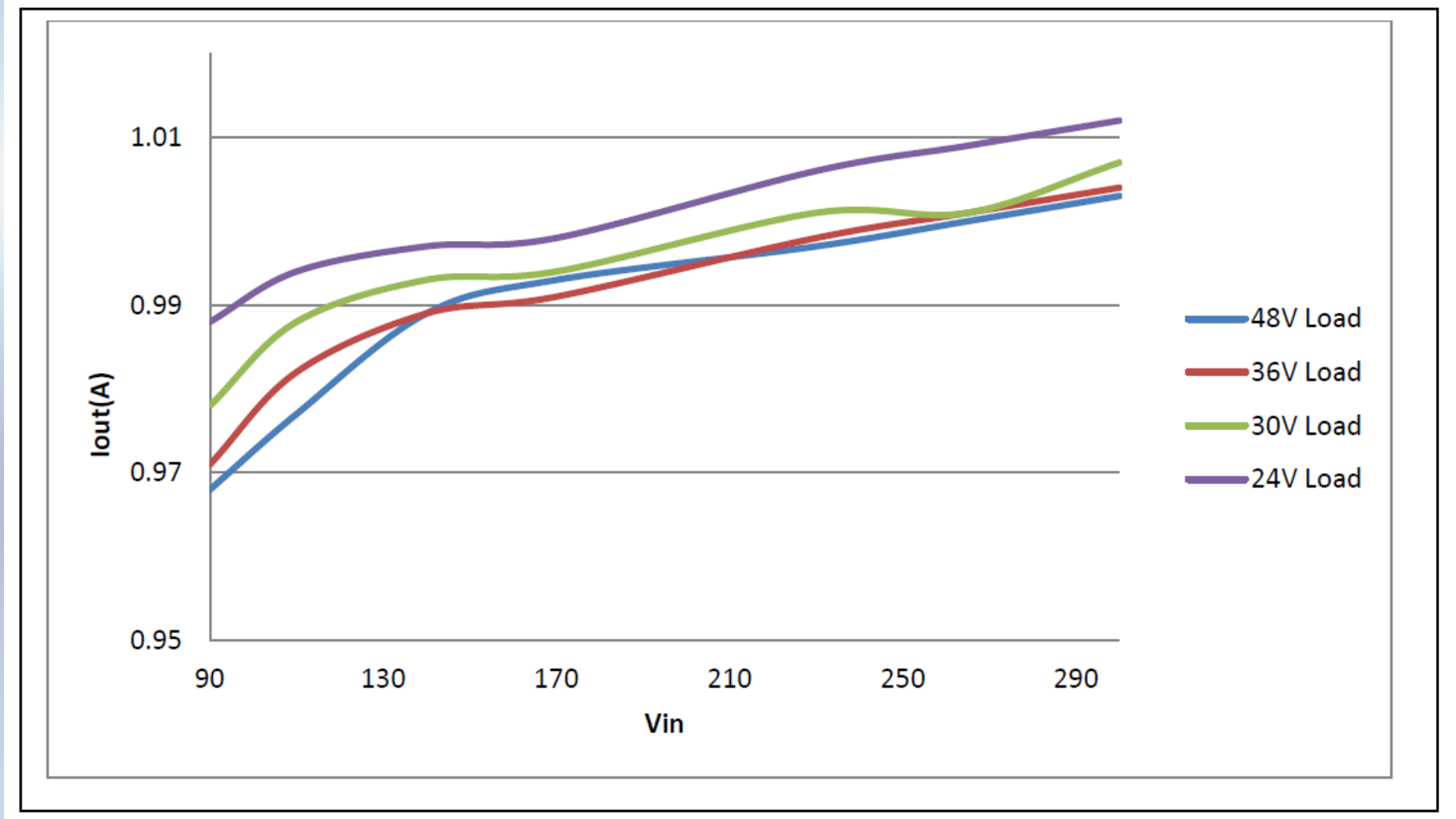


Efficiency Vs Vin at various loading

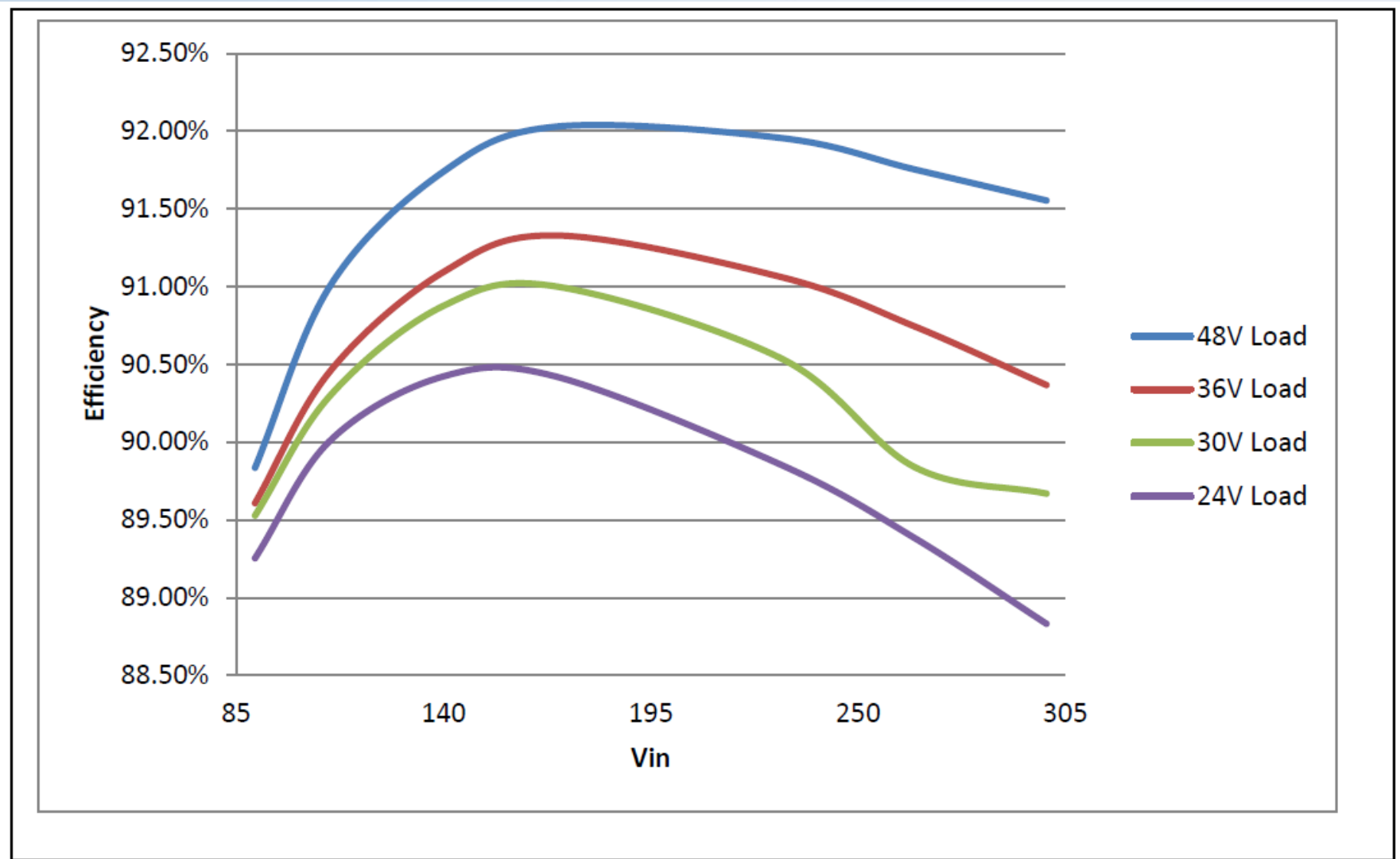


PF vs Vin

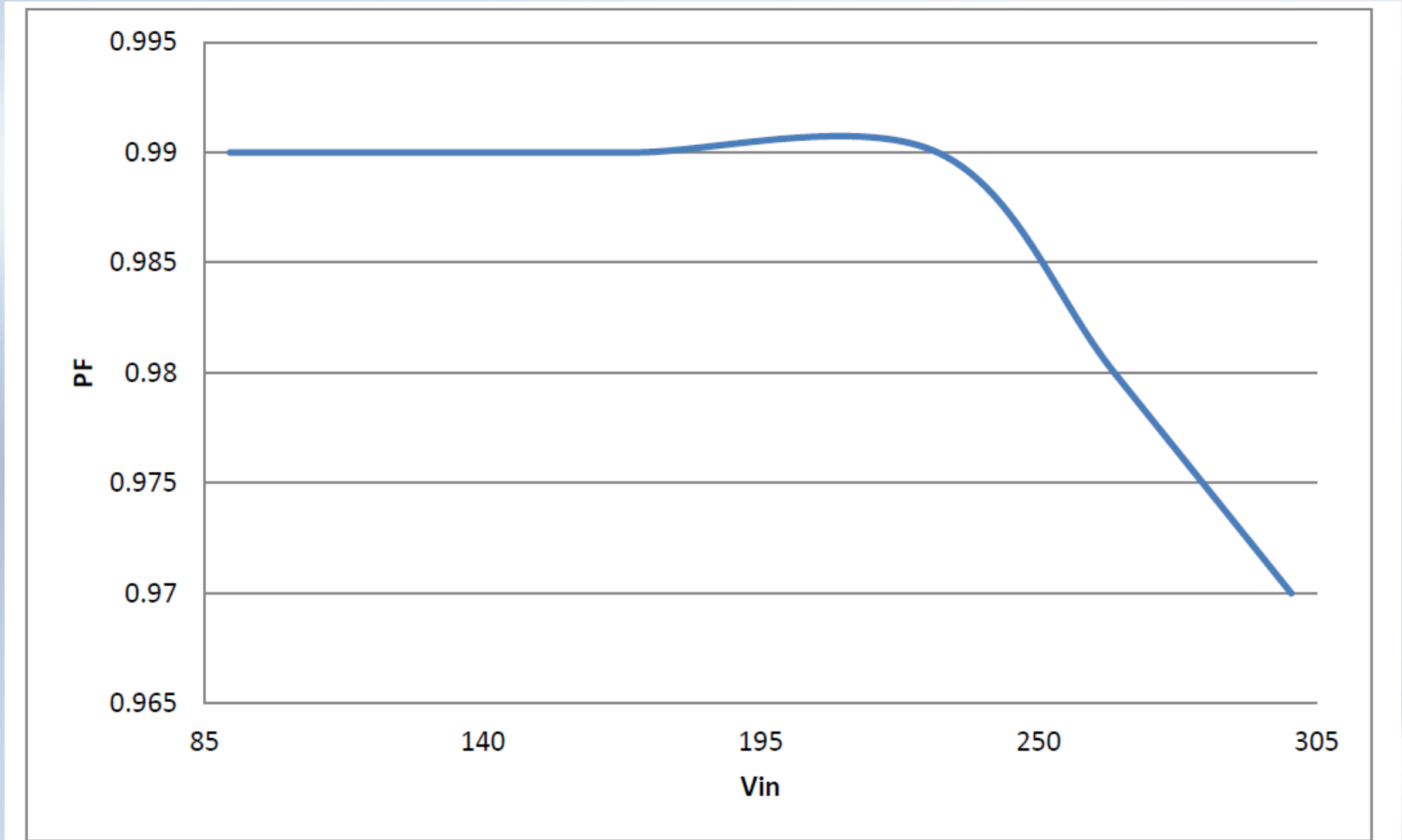


THD vs Vin at full load

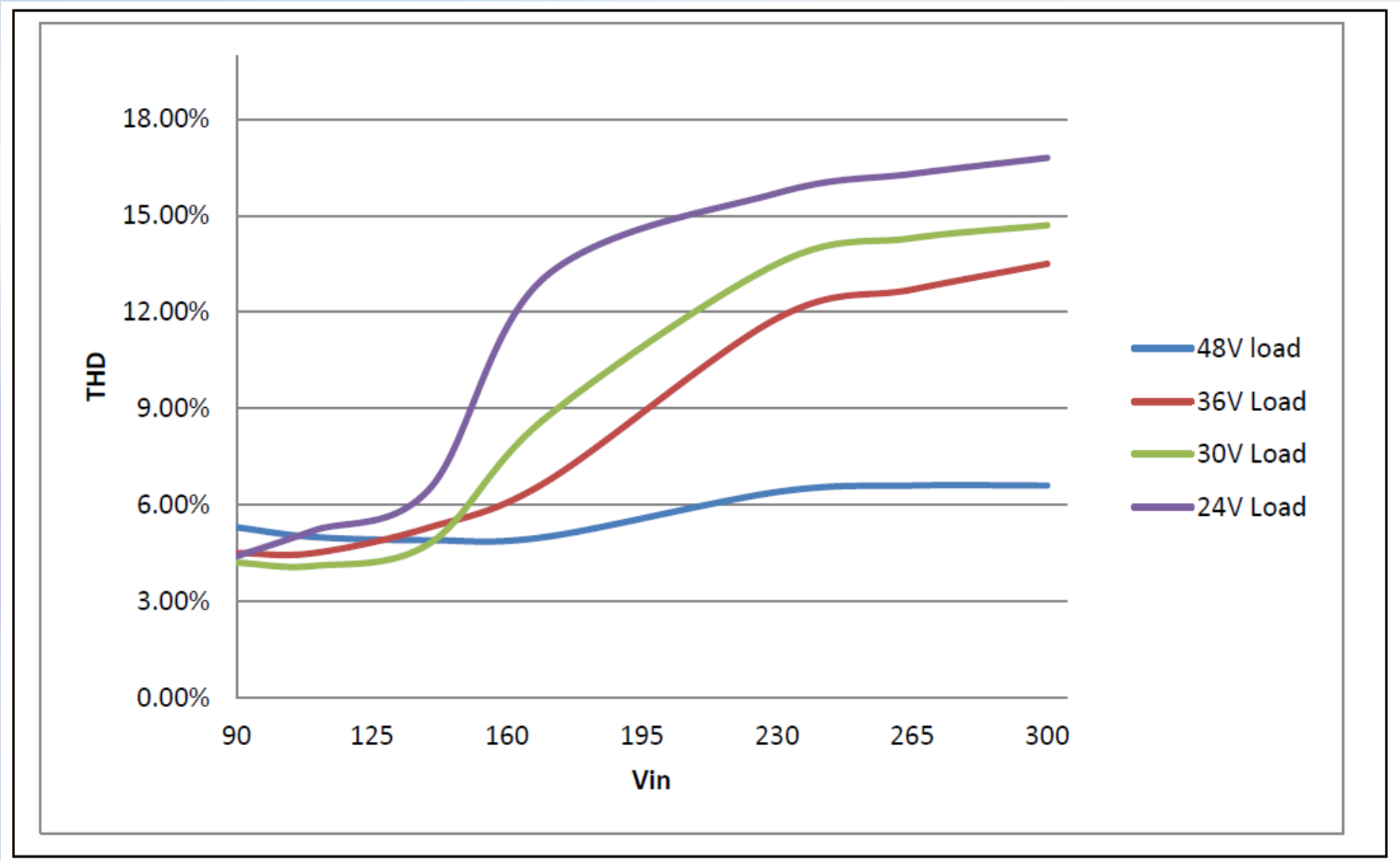


THD vs Vin at full load

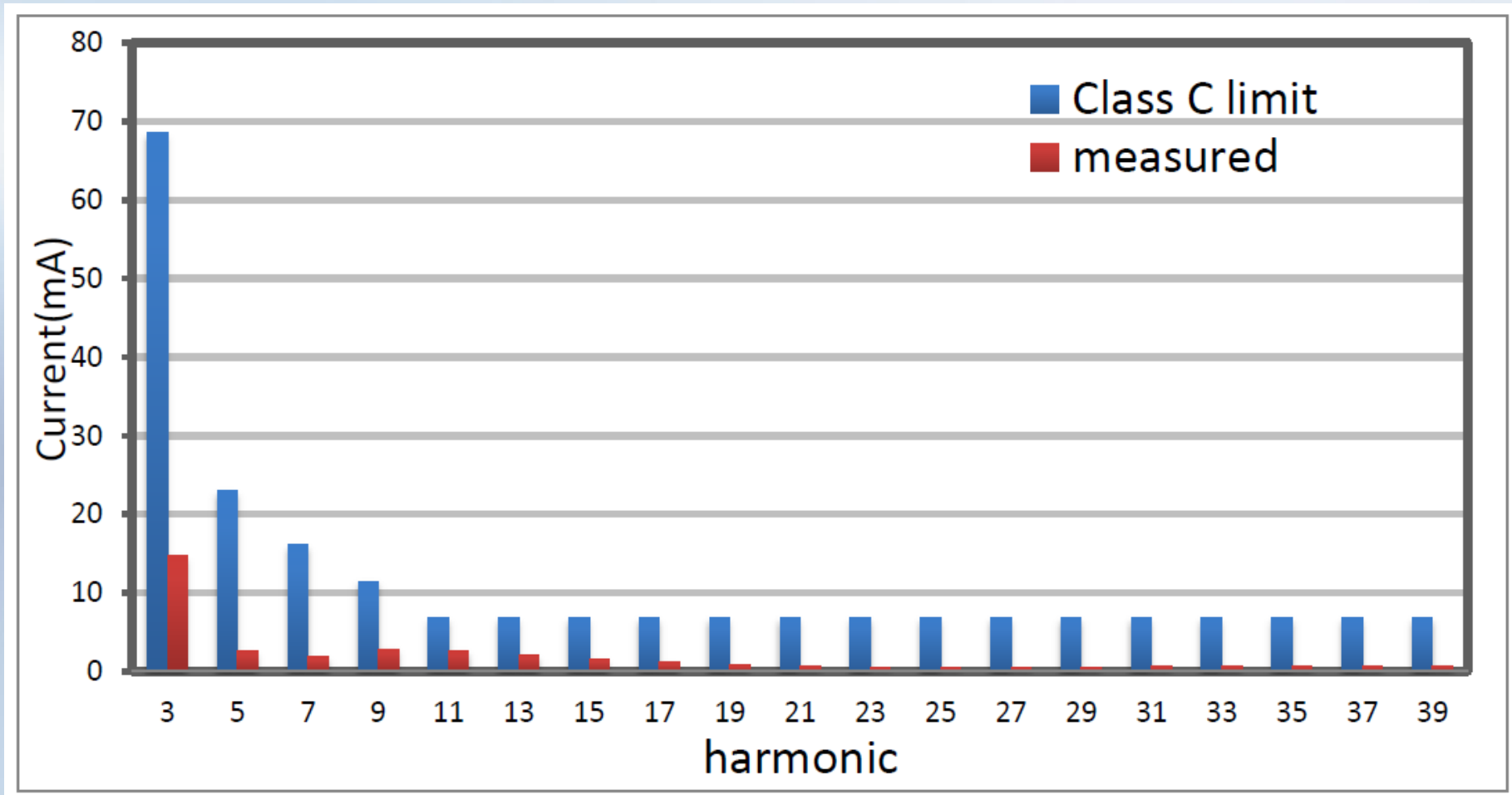

Thermal and Conducted EMI

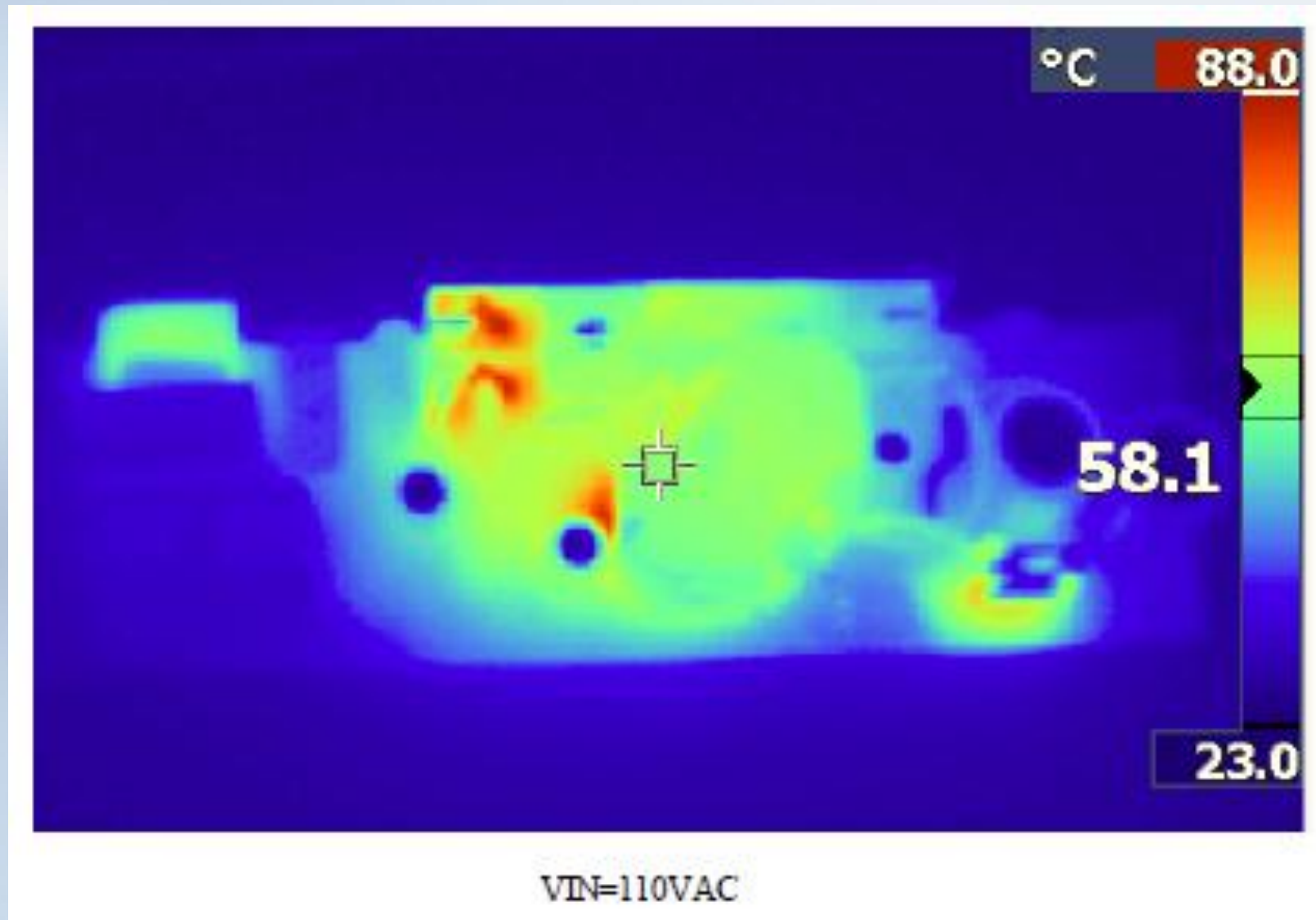

Thermal and Conducted EMI

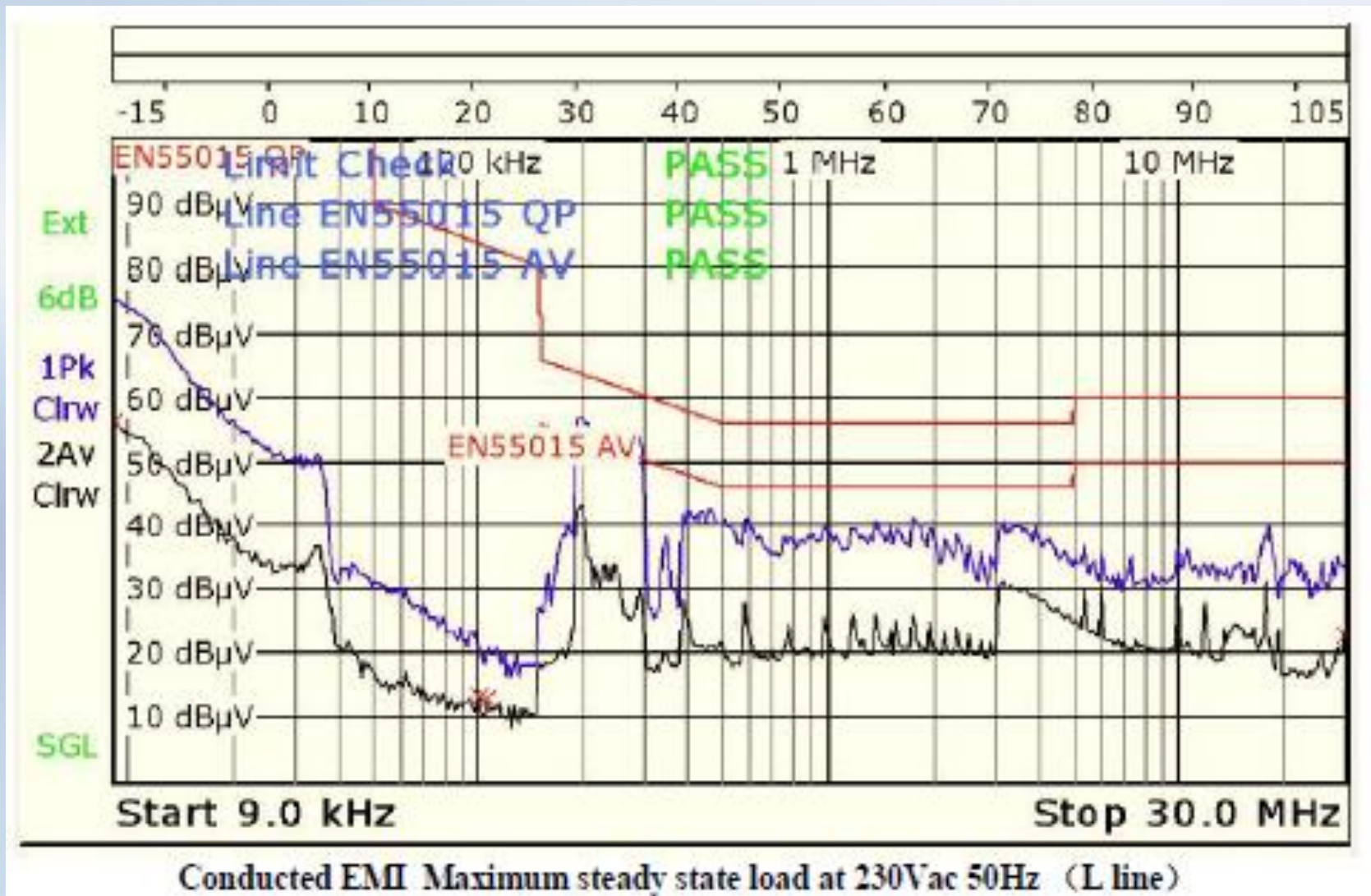


INDEX


- 48Watt Flat Lamp Solution
- DC/DC Dimming Solution
- 7Watt, 10Watt MR16 Solution
- Summary

ILD6070 / ILD6150


Demo boards

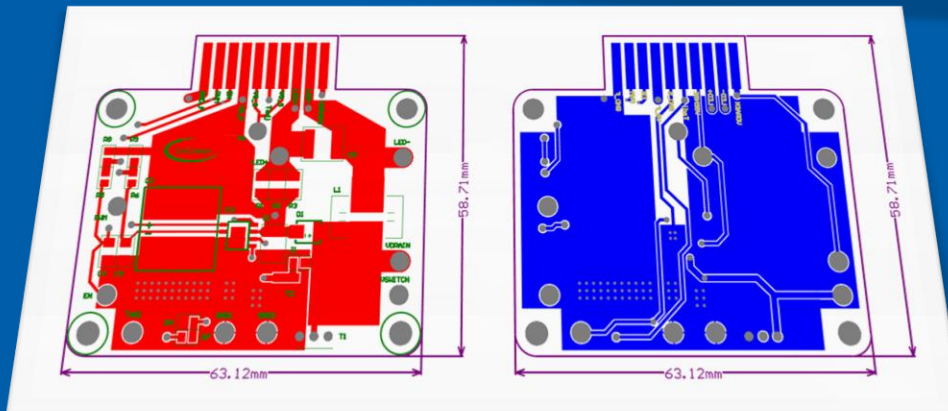

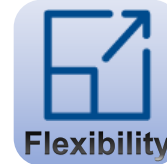- Buck topology
- Max 1MHz f_{sw}
- Low quiescence current



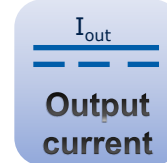- Wide usable input voltage range from 4.5V – 60V
- Current accuracy $\pm 3\%$



- Integrated MOSFET rated up to 700 / 1.500 mA



- Benchmark DC/DC efficiency up to 98%




- PWM & analog dimming
- Int. PWM generator for analog dimming
- 3000:1 contrast ratio





- Adjustable over temperature protection
- Over current protection

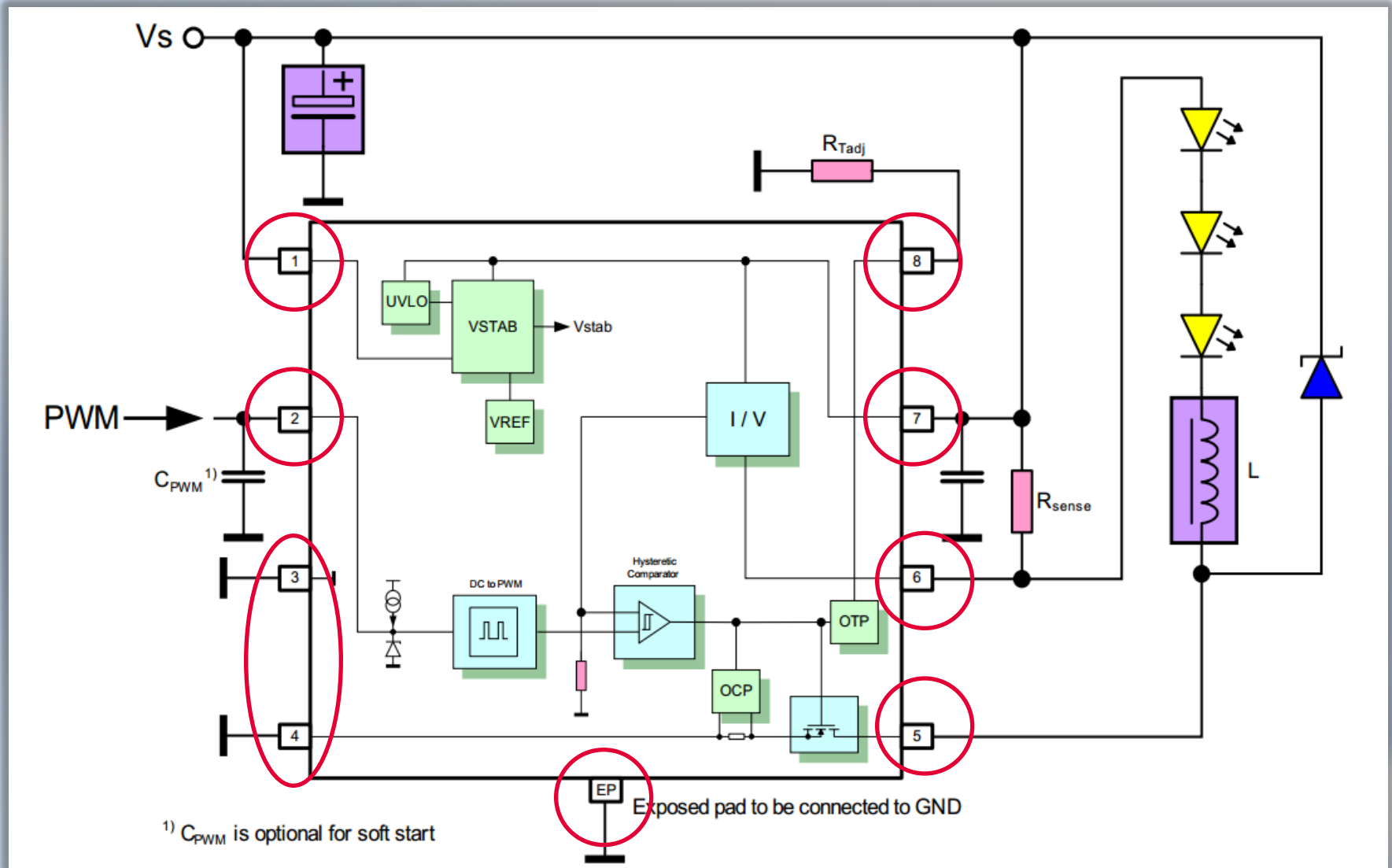ILD6070 / ILD6150 Typical Application Circuit




Hysteretic Buck Driver

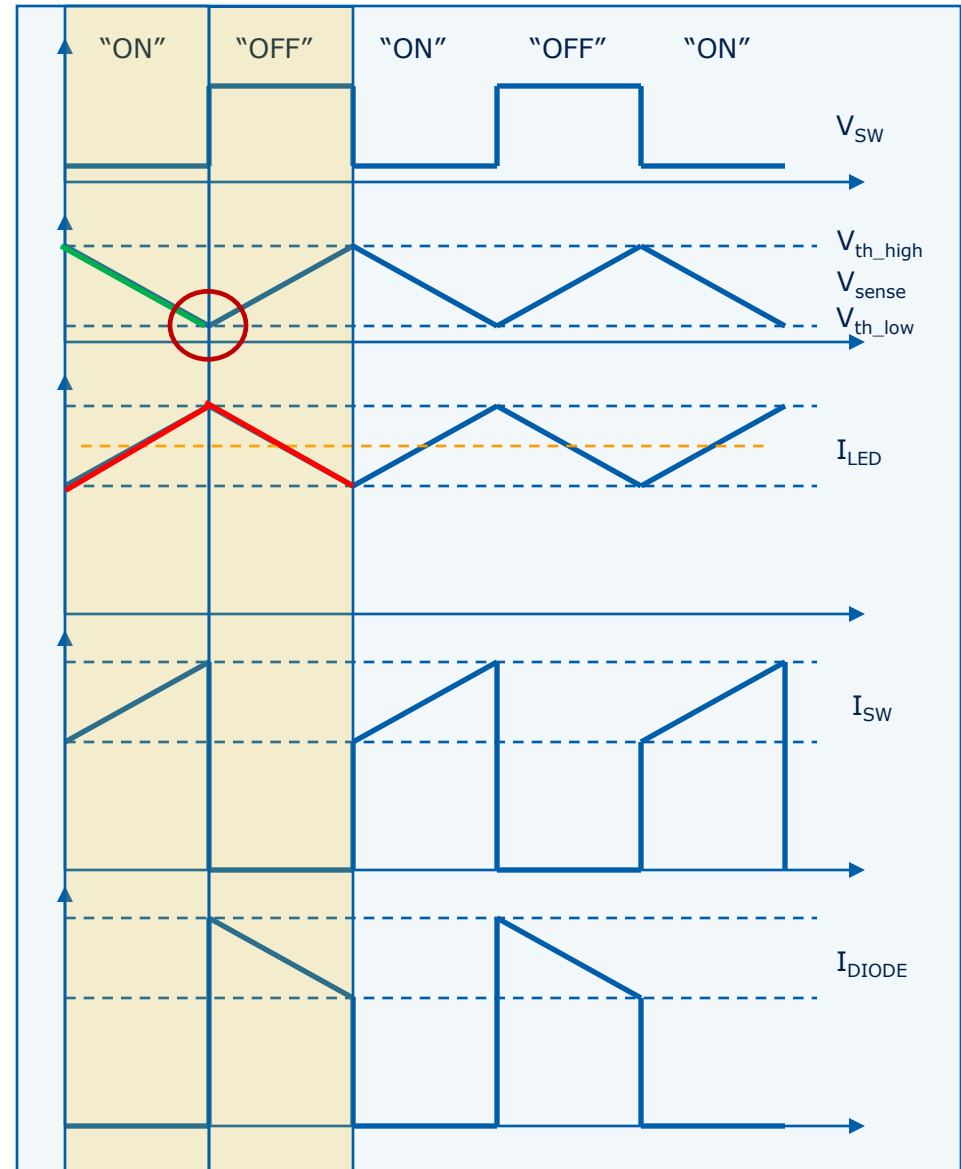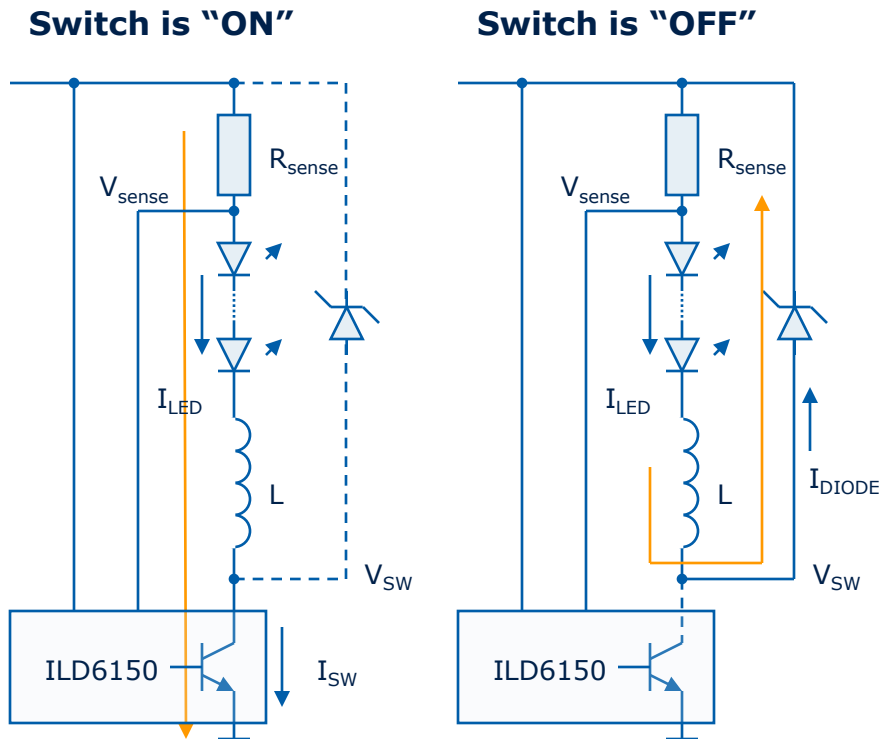

ILD6150 Measurement Results


■ Typical signal waveform

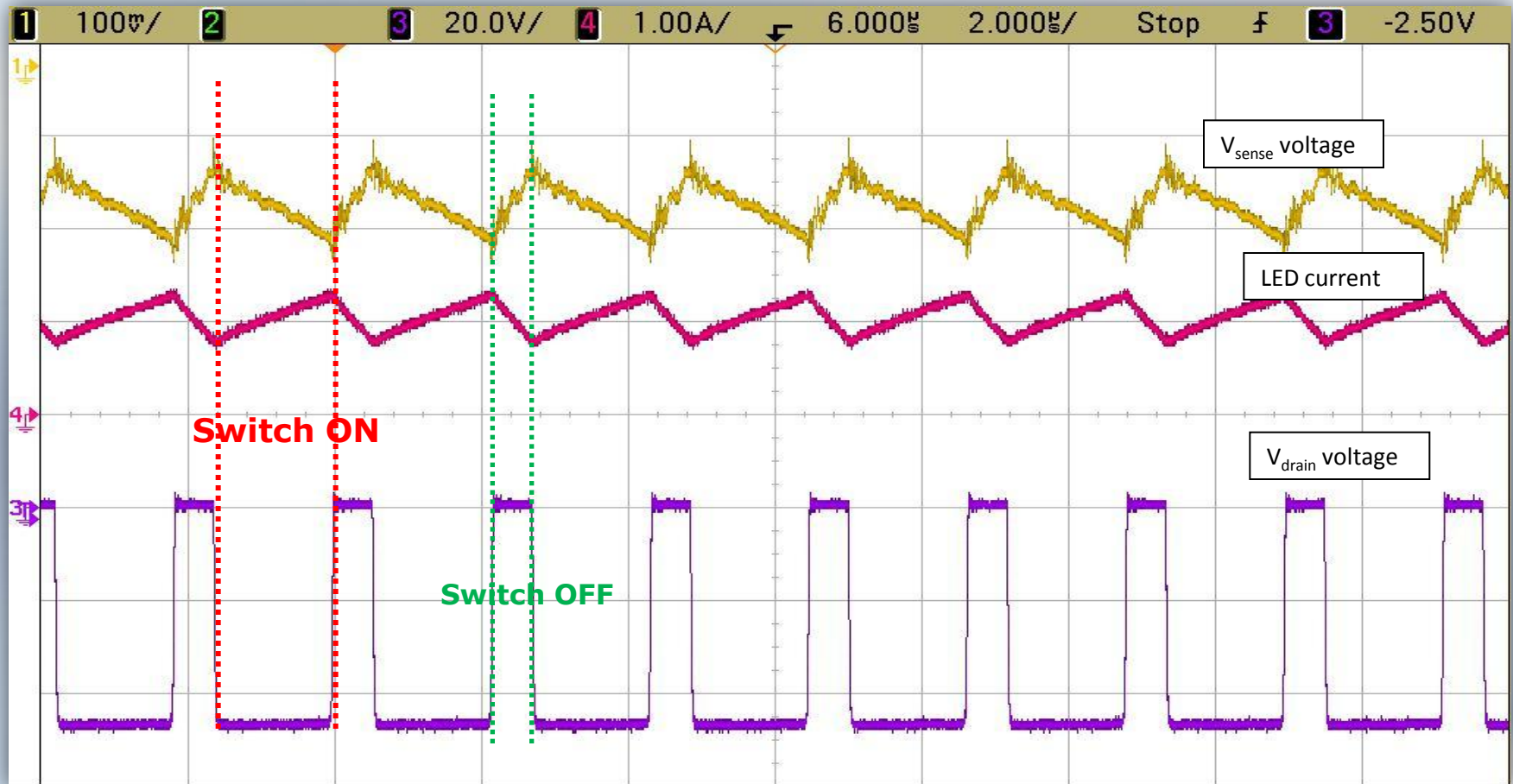

□ Frequency = 467 kHz, Duty = 73.8%

Power losses of switch mode driver

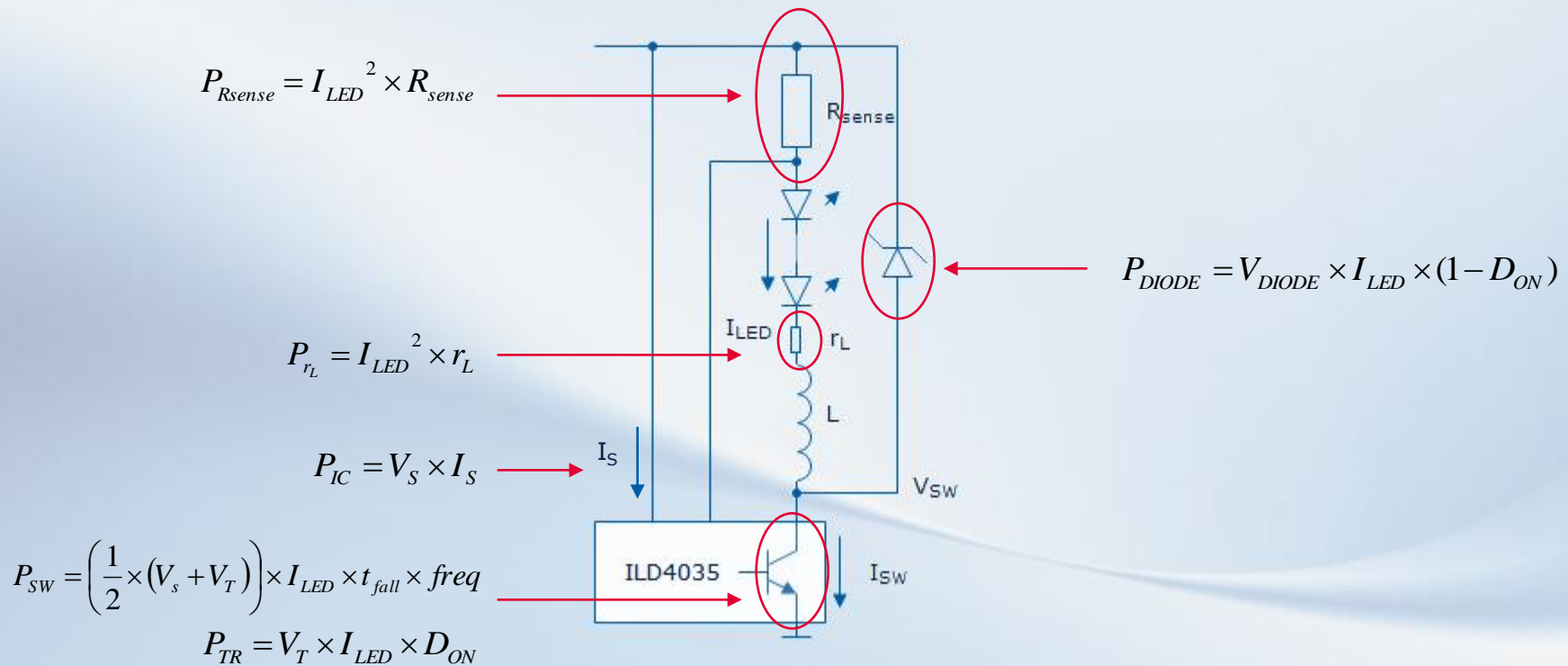
- The efficiency of the switch mode driver is known to be better than linear mode driver. This is due to if the voltage drop on the linear driver is higher, the power loss is larger.



ILD6150 Measurement Results

■ Efficiency

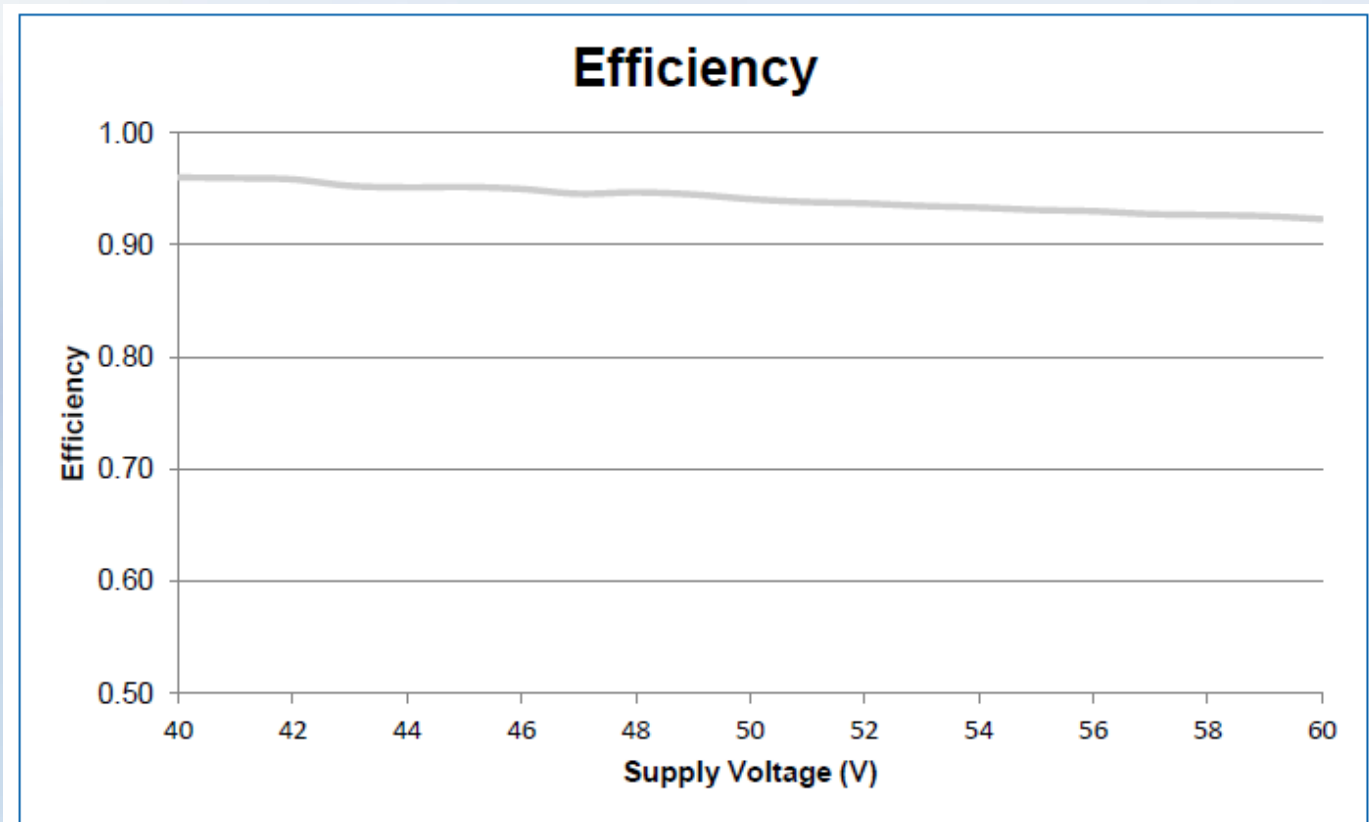
- Efficiency figure shows total efficiency of the application board including losses of external components as inductor and Schottky diode.




ILD6150 Measurement Results

■ Analog Dimming

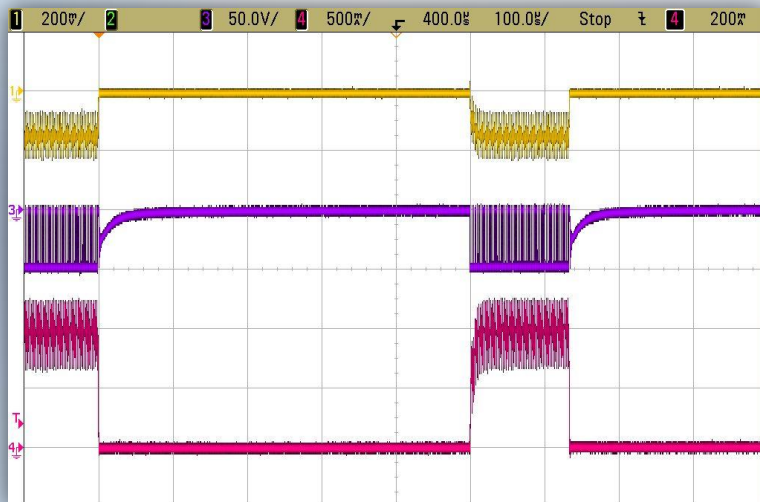- The analog DC voltage is converted to a 1.6 kHz PWM signal modulating the LED current.
- Linear range of analog dimming : 0.67 V ~ 2.43 V



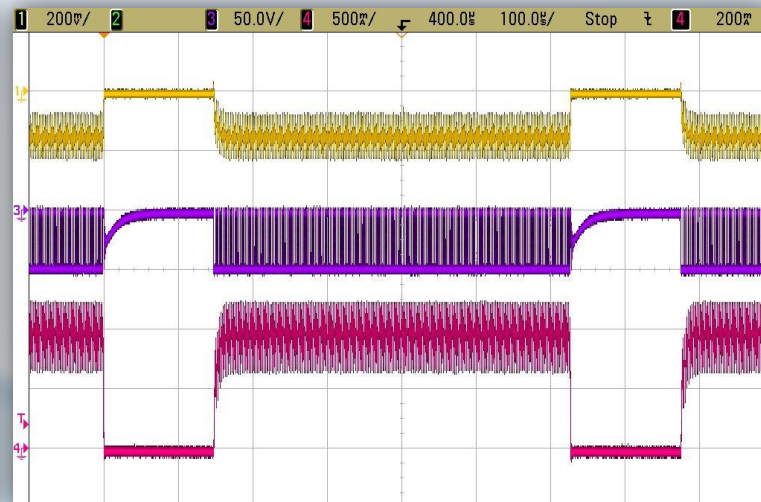Output waveform at $V_{PWM} = 1\text{ V}$



Output waveform at $V_{PWM} = 2\text{ V}$

V_{sense} voltage


V_{drain} voltage

LED current

ILD6150 Measurement Results

■ Over Temperature Protection

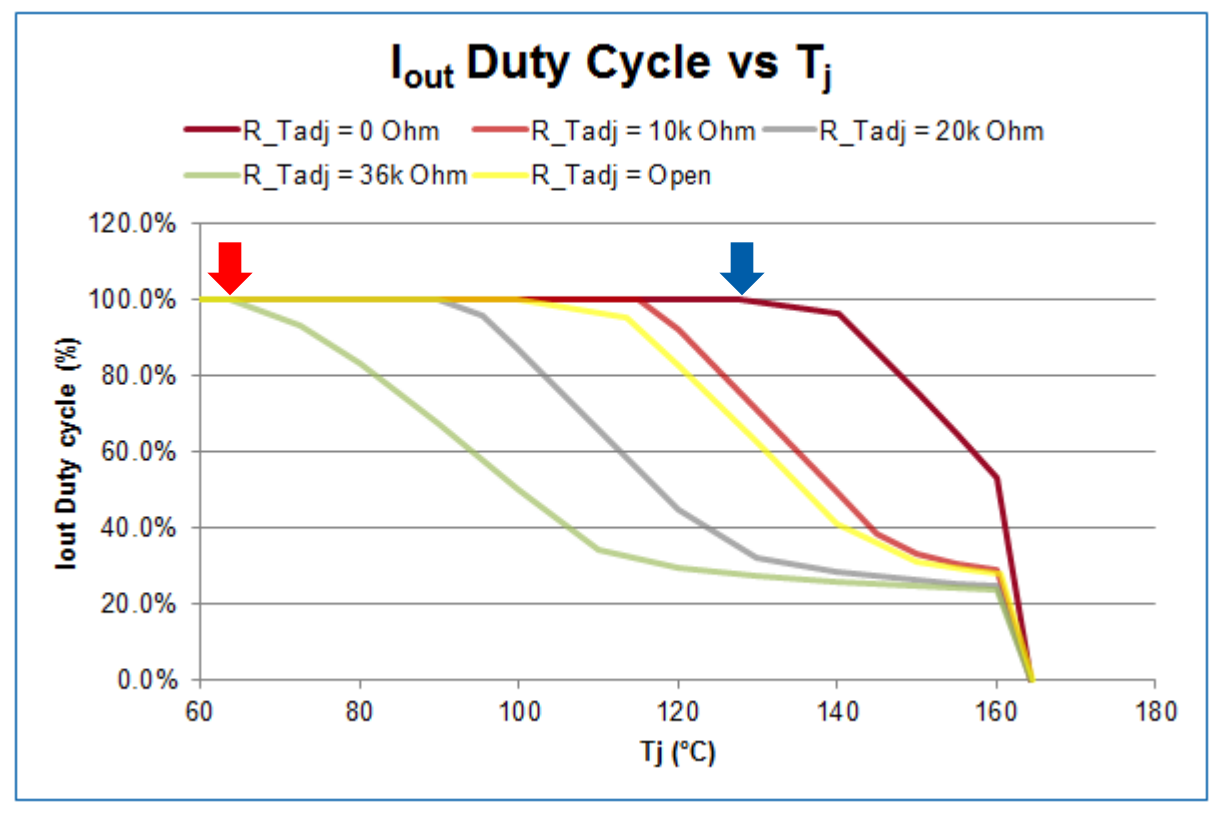
- ILD6150 feature with an integrated OTP will reduce the current by internal PWM modulation once the junction temperature of the IC is exceeded.



ILD6150 Measurement Results

■ Over current protection

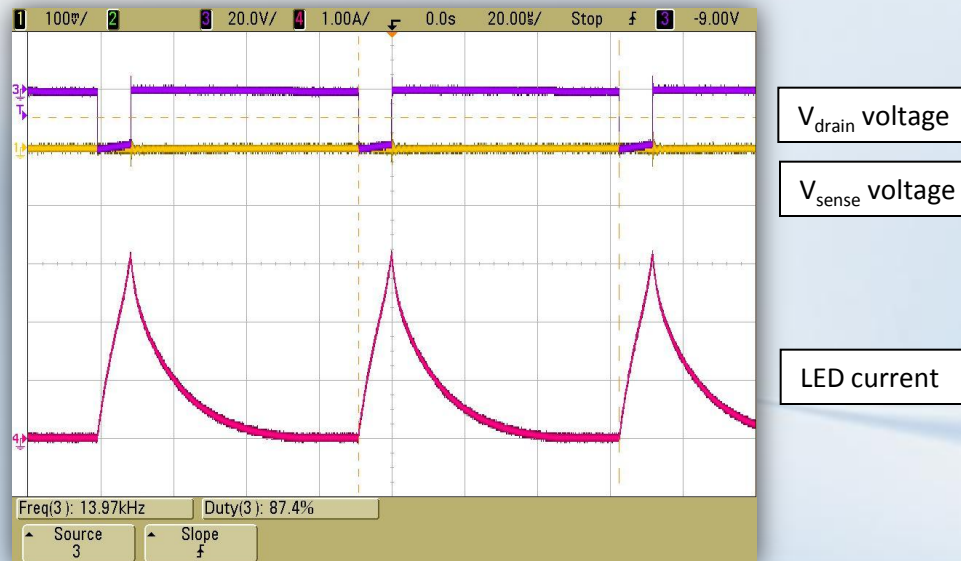
- The ILD6150 feature with over current protection where the current threshold is 2.5 A. The MOSFET will be turned off for 60 μ s when OCP is triggered.
- Waveforms below shows the OCP in operation when the R_{sense} is shorted and the LED load replaced by a 3 Ω resistive load.



INDEX

- 48Watt Flat Lamp Solution
- DC/DC Dimming Solution
- 7Watt, 10Watt MR16 Solution
- Summary

Demo board

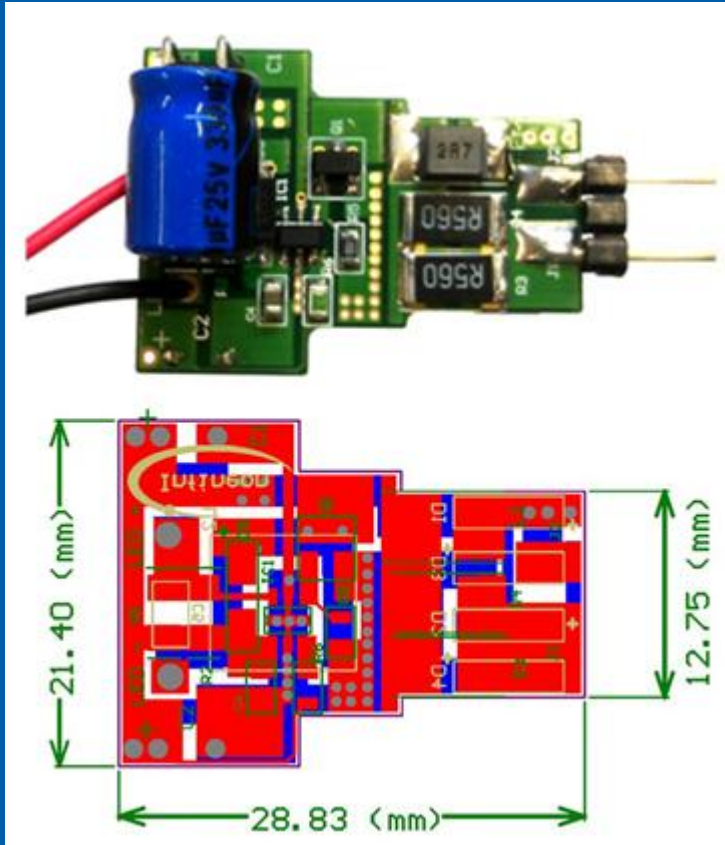


Recommended MOSFET BSR 302N (30V, SC59), BSP 318S (60V, SOT223)




Operation

Step-down topology

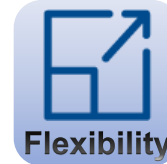

Flexibility

Wide input voltage range from 4.5V – 40V

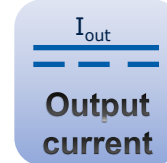

Output current

Scalability from 10mA – 3.000mA easily allows replication to new designs



Efficiency

DC/DC efficiency up to 98%



Dimming


Choice of dimming concept: Analog or digital



Protection


Thermal protection

MR16 solution Circuit

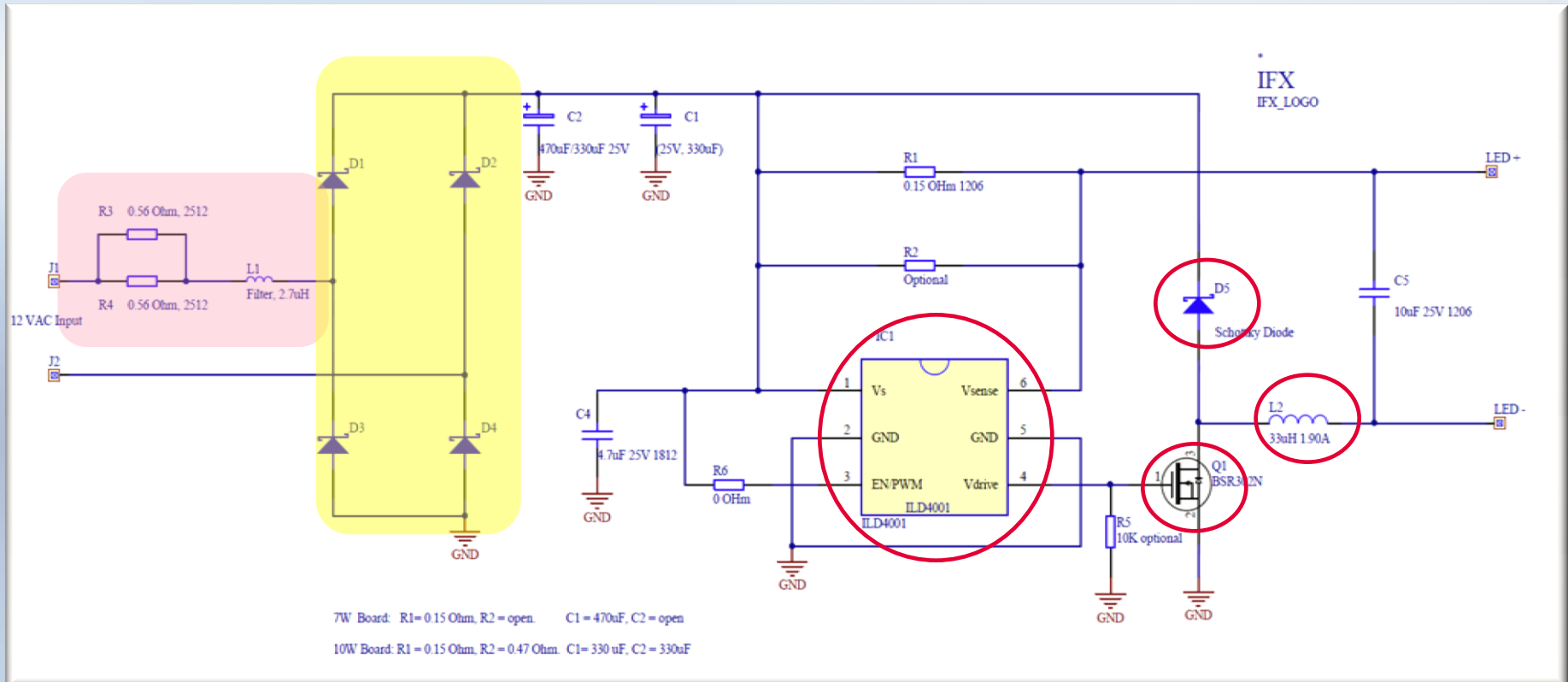

MR16 Test Condition


Test setup

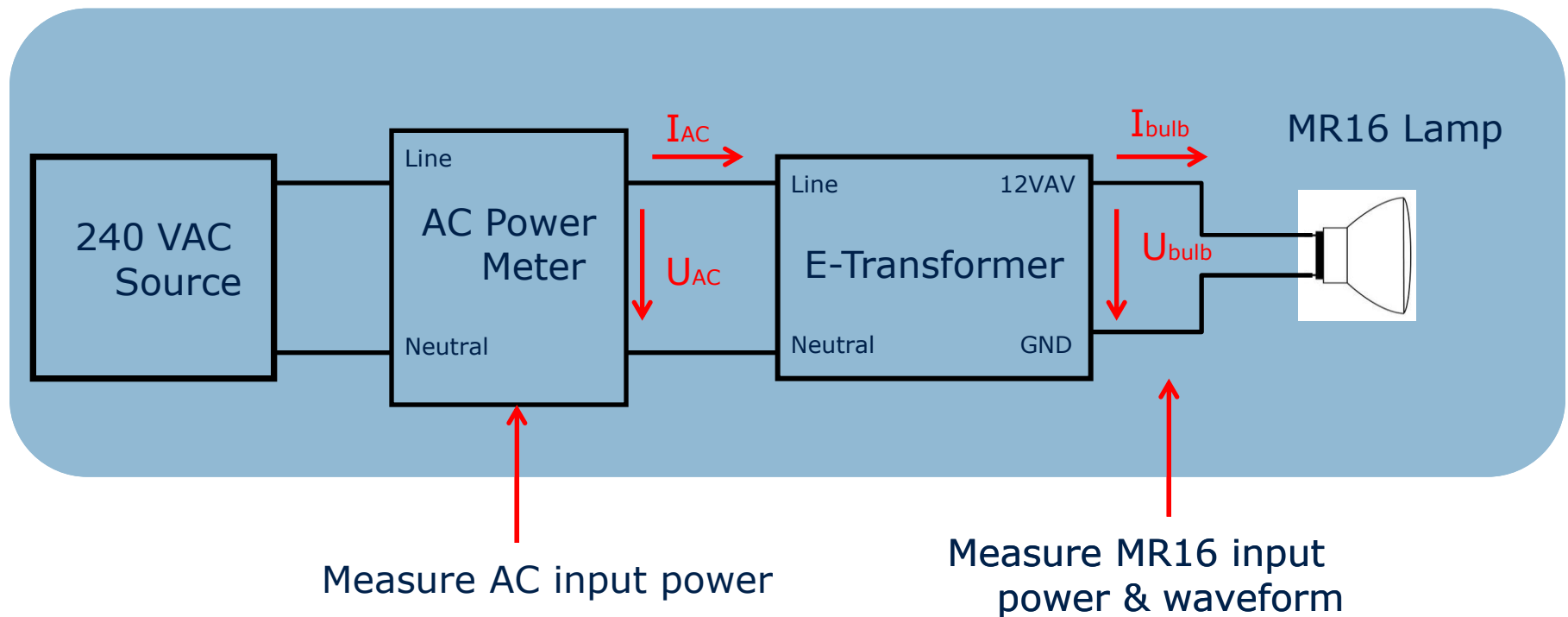

E-transformer compatibility

7 W board measurement results with Philips ET-E60.

Input voltage to electronic transformer	230 V_{AC}
V _f (avg)	6.45 V
I _{LED} (avg)	777 mA
P _{in}	6.94 W
P _{out}	5.08 W
Efficiency	73.2 %

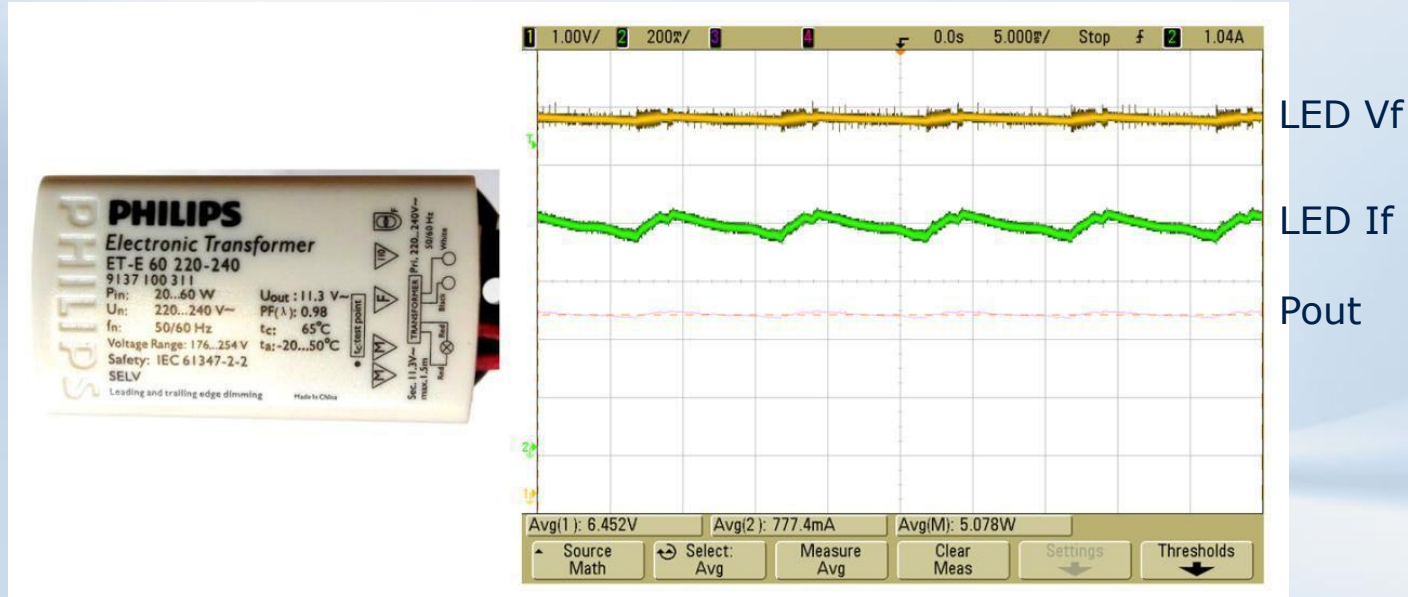


Output waveform for the 7 W MR16 board driven by Philips ET-E60.

E-transformer compatibility

10 W board measurement results with Tridonic TE0060.

Input voltage to electronic transformer	230 V _{AC}
V _{f(avg)}	6.63 V
I _{LED(avg)}	1.05 A
P _{in}	9.8 W
P _{out}	7.1 W
Efficiency	72.4 %

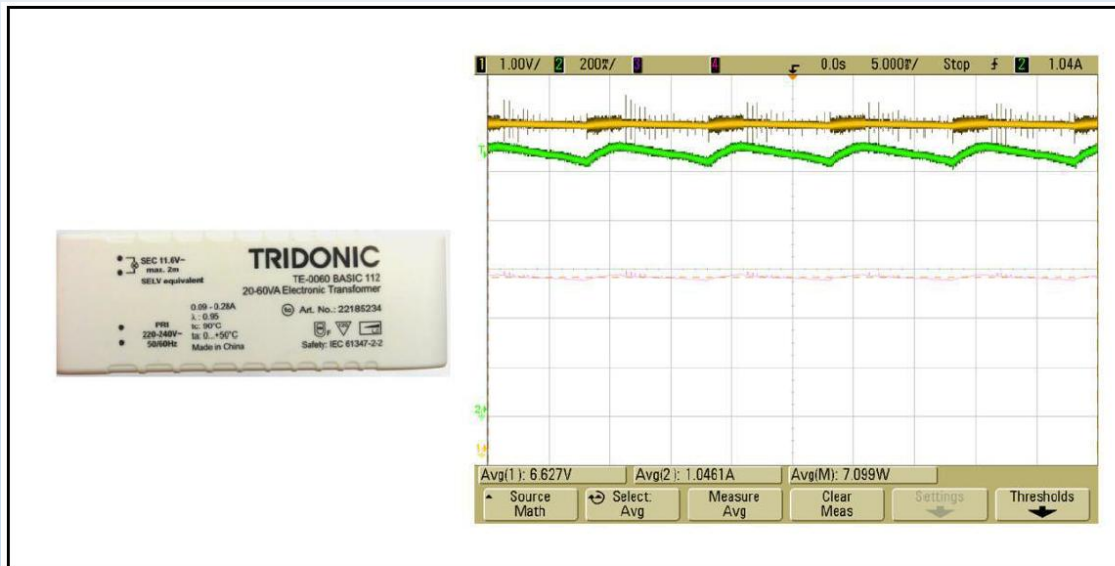


LED Vf

LED If

Pout

Output waveform for the 10 W MR16 board driven by Tridonic TE0060.

E-transformer compatibility

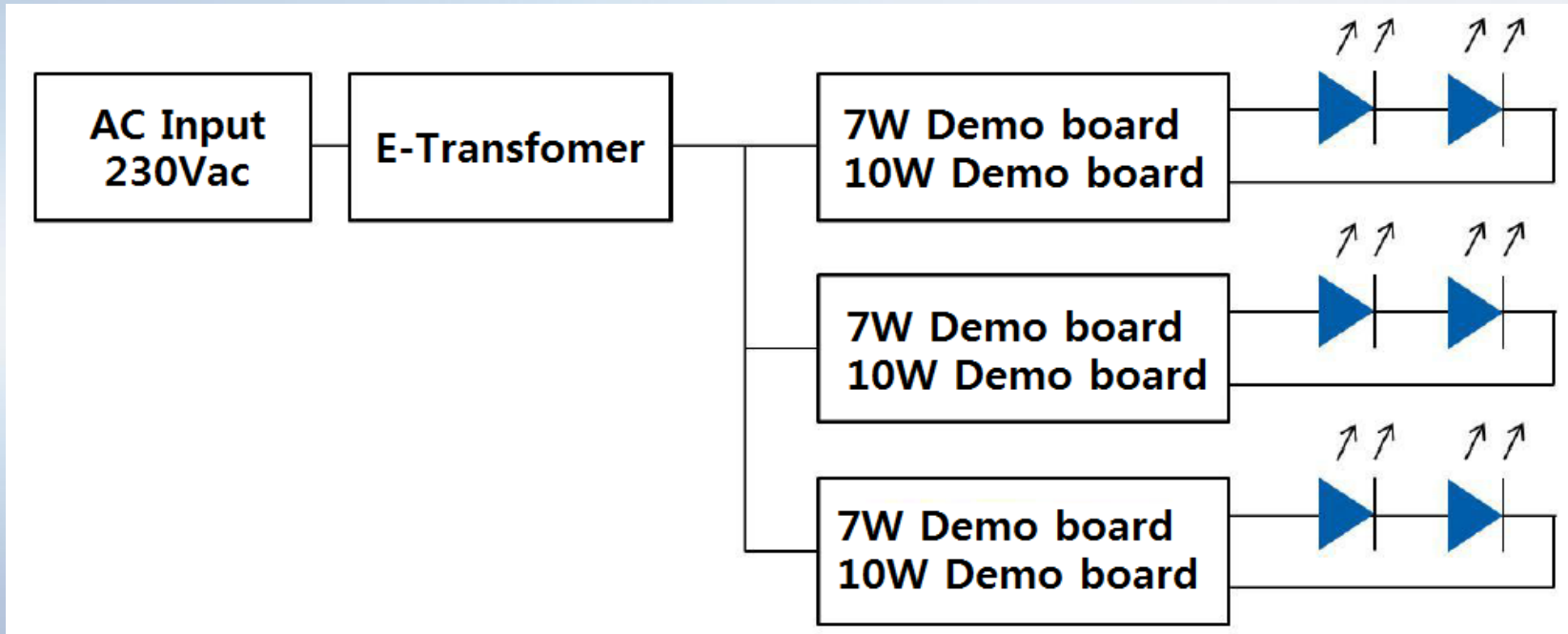


Electronic transformers list

E- transformer Model	7 W MR16	10 W MR16
Philips ET-E60	1	1
Osram ET-A60	1	1
Osram HTM 105	1,2 or 3	1 or 2
Tridonic TE-0060	1	1

INDEX

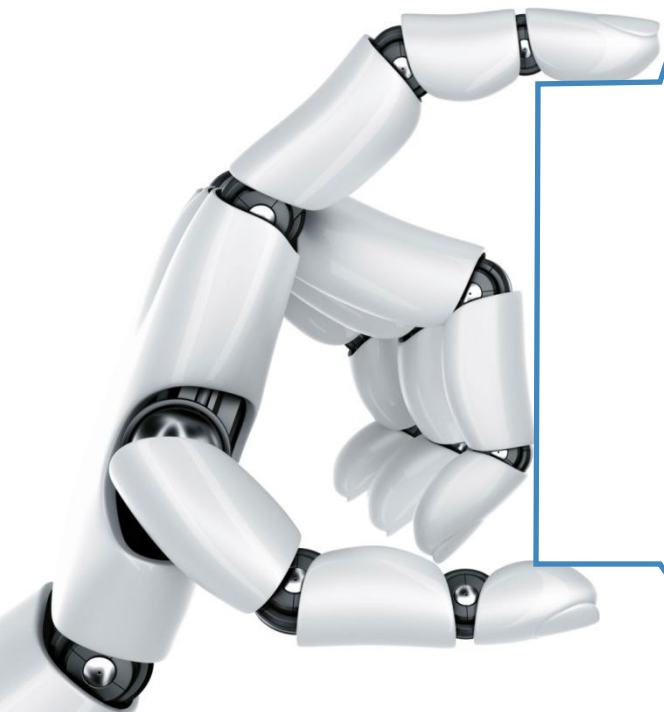- 48Watt Flat Lamp Solution
- DC/DC Dimming Solution
- 7Watt, 10Watt MR16 Solution
- Summary



- 1** Infineon's **48W Flat panel & MR16 solution** enable customers to reduce development cycle with high performance.
- 2** **ILD6xxx** series can support the highest dimming performance & efficiency and long life time of LED with Slope current reduction.
- 3** Infineon offers an **innovative products portfolio** of general lighting.




LED Lighting



- Application Brochure
- Application Examples
- Application Notes

■ www.infineon.com/cms/en/product/applications/lighting/led-lighting/

Technical Material

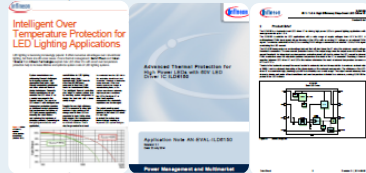


- Products + Datasheets
- Simulation Models
- PCB Design Data
- App Notes, White Paper

■ www.infineon.com/lowcostleddriver

■ www.infineon.com/ledoffline

■ www.infineon.com/led.documents


Evaluation Boards

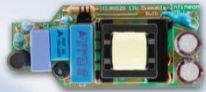

- Evaluation Boards
- Reference Designs

■ www.infineon.com/led.evalboards

■ www.infineon.com/led.appnotes

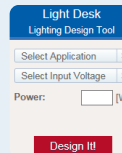

Light
Desk

- LED Driver Online Design Tool

■ www.infineon.com/lightdesk

Selection Guide

Product	Name	Packaging	Description
MM Controller	IDA983.2G	DSO-8	PFIC for High Power Factor and Low THD
ICV Regulator	TLE4305G	DSO-8	Minimized external circuitry
	TC240B3000CE	DFPAKPAK	800V, 4.5A, 0.95ohm
	ED440B3000CE	DFPAKPAK	800V, 5.7A, 0.95ohm
CoMoS	SMA3000CE	TO220FPAK	800V, 5A, 0.65ohm
	SFALLNRC3	TO220FPAK	800V, 11A, 0.45ohm

- Selection Guide



Selection guide

감사합니다.

- 김성호 차장 (반도체 기술 담당 엔지니어)
 - E-mail : Sungho.kim@infoneon.com

- 전광일 과장 (애플리케이션 마케팅)
 - E-mail : Kyle.jeon@infoneon.com



ENERGY EFFICIENCY MOBILITY SECURITY

Innovative semiconductor solutions for energy efficiency, mobility and security.

