



uModule & uSLIC 전력 설계의 단순화

송영한


Field Application Engineer
alexander.song@analog.com

analog.com

Past and Present



Buck Converter Integration Levels

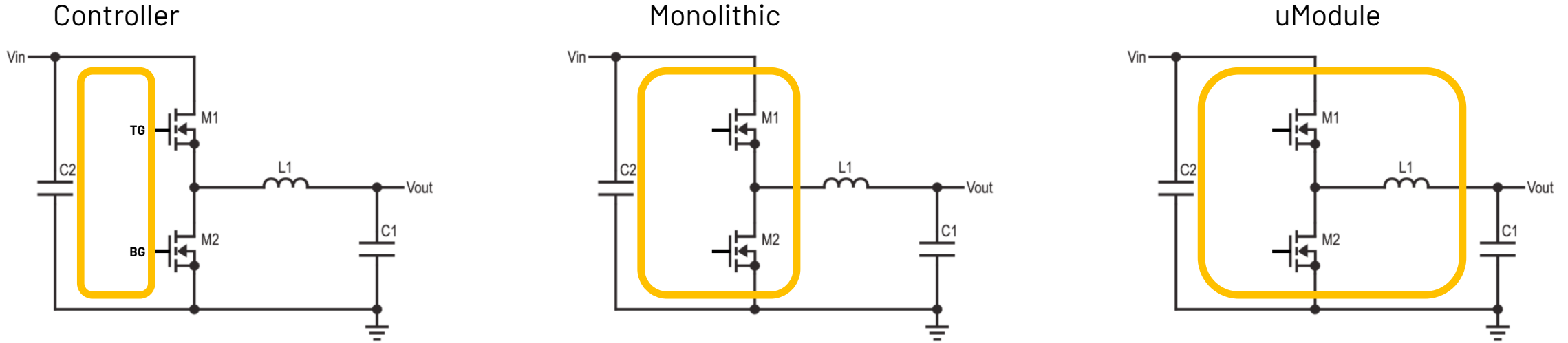

특징	Controller	Monolithic	uModule
집적도	낮음	중간	높음
효율	매우 높음 최적화 시 95%+	높음 90~95%	높음 Monolithic ±1~2%
설계 난이도	어려움 외장 부품/레이아웃 최적화 필요	중간 외장 인덕터, 패시브 최적화 필요	쉬움 Plug and Play
디자인 사이즈	큼 외장 부품 다수	중간	작음 부품 수 감소
열 관리	주의 요함 발열 경로 설계 필수	중간	최적화 패키지 차원
EMI 리스크	높음 루프/게이트 드라이브 영향	중간	낮음
부품 단가	낮음	중간	높음

Controller vs uModule

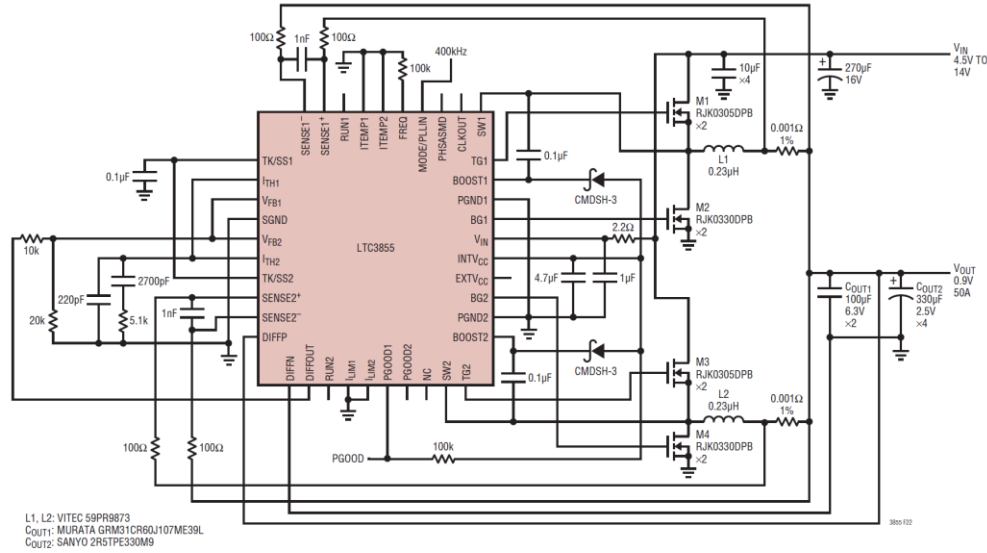


Figure 22. Small Size, Dual Phase 0.9V, 50A Supply, $f_{sw} = 400kHz$



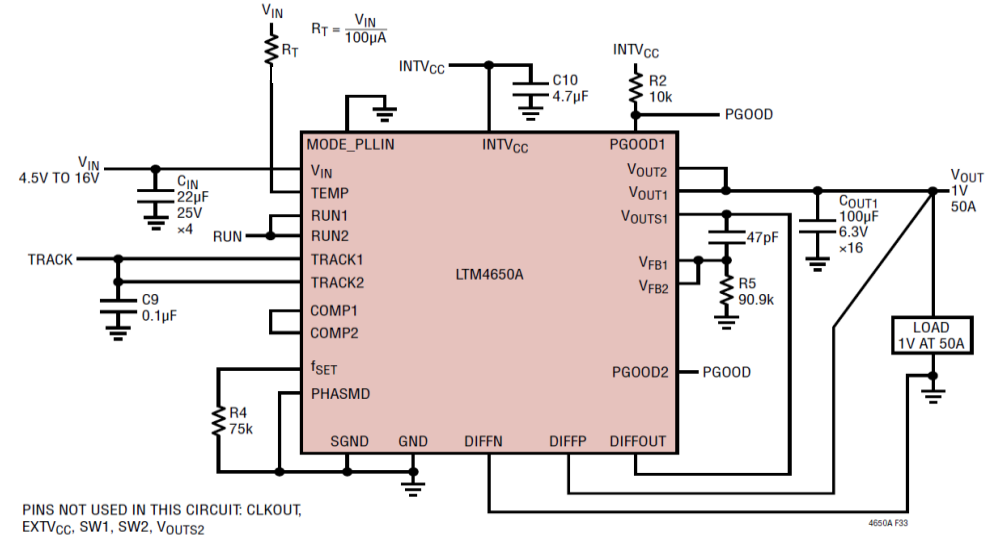
 


Figure 33. LTM4650A 2-Phase, 1V at 50A Design

 

Controller Circuit Operation Sequence

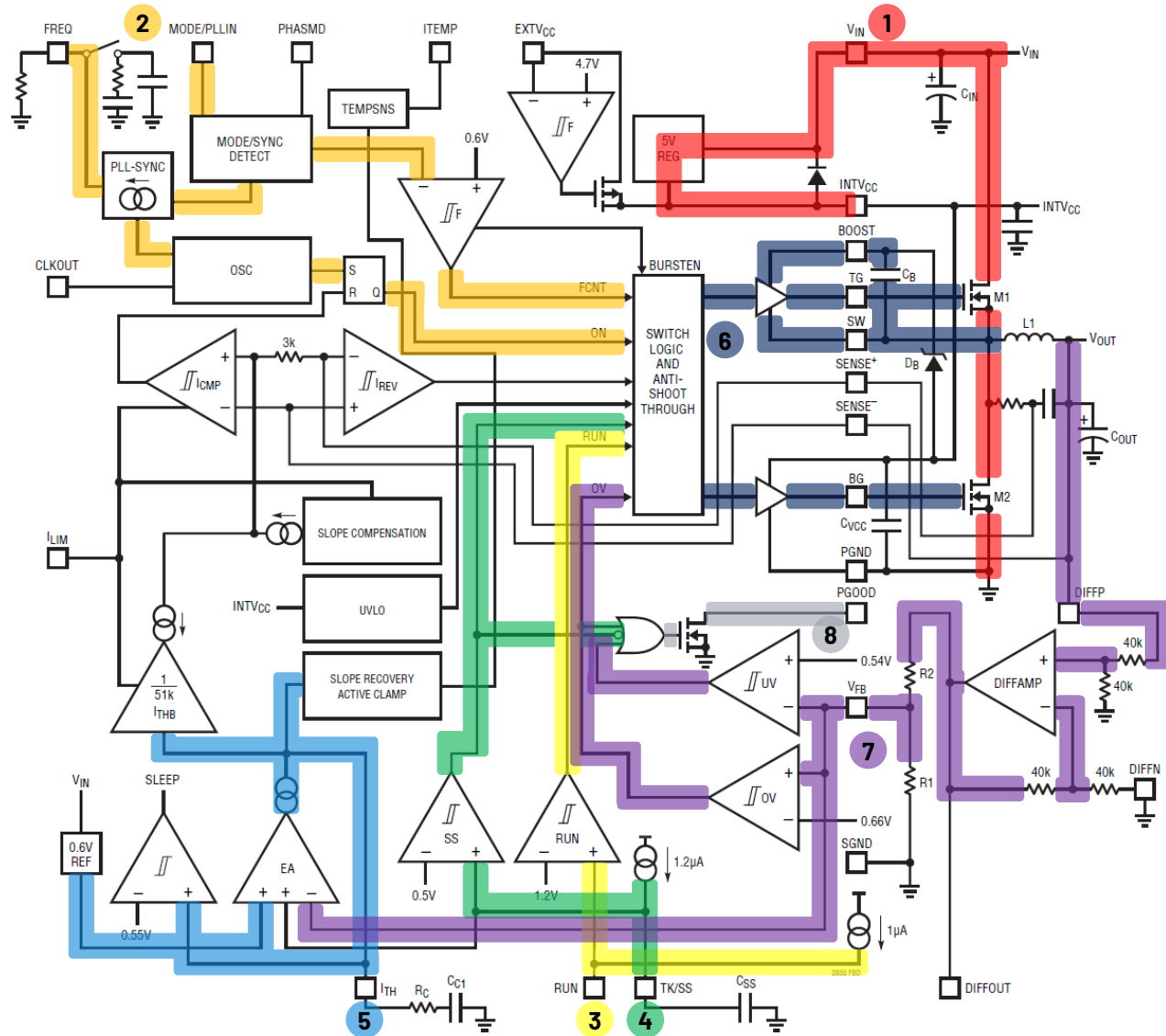

Controller Circuit Design : Switching Frequency

 


Figure 12. Relationship Between Oscillator Frequency and Voltage at the FREQ Pin

	MIN	TYP	MAX	
I_{FREQ}	9	10	11	μA

- $300kHz \cong V_{freq}$
- $0.75V = 10\mu A \times 75K\Omega (= R_{freq})$

- 인덕터 값 선정
- Duty Cycle 영향
- 전력 손실
- EMI 스펙트럼 변화
- Cin, Cout 용량

	MIN	TYP	MAX	
$t_{ON(MIN)}$	Minimum On-Time	90		ns

- $V_{OUT.min} = V_{IN} \times f_{sw} \times t_{on.min}$
- $0.81V = 20V \times 450kHz \times 90ns$

Controller Circuit Design : Inductor Selection




STANDARD ELECTRICAL SPECIFICATIONS					
L_0 INDUCTANCE ± 20 % AT 100 kHz, 0.25 V, 0 A (μ H)	DCR TYP. 25 °C (m Ω)	DCR MAX. 25 °C (m Ω)	HEAT RATING CURRENT DC TYP. (A) ⁽¹⁾	SATURATION CURRENT DC TYP. (A) ⁽²⁾	SRF TYP. (MHz)
0.10	2.7	2.9	21.0	25.0	266
0.22	4.1	4.5	17.0	13.0	146
0.33	5.5	5.9	13.0	7.5	108
0.47	7.1	7.7	12.5	8.0	83
1.0	16.8	18.1	7.5	7.0	66
2.2	34.9	37.7	5.0	5.5	41
3.3	53.5	57.8	4.1	4.7	29
4.7	75.3	81.3	3.2	3.0	27
5.6	85.2	92.0	3.0	2.2	24
6.8	114.0	121.0	2.8	2.1	21
10.0	169.3	182.8	2.2	2.0	17

$$t_{ON(MIN)} < \frac{V_{OUT}}{V_{IN}(f)}$$



$$I_{RIPPLE} = \frac{V_{OUT}}{V_{IN}} \left(\frac{V_{IN} - V_{OUT}}{f_{OSC} \cdot L} \right)$$

$$L \geq \frac{V_{IN} - V_{OUT}}{f_{OSC} \cdot I_{RIPPLE}} \cdot \frac{V_{OUT}}{V_{IN}}$$

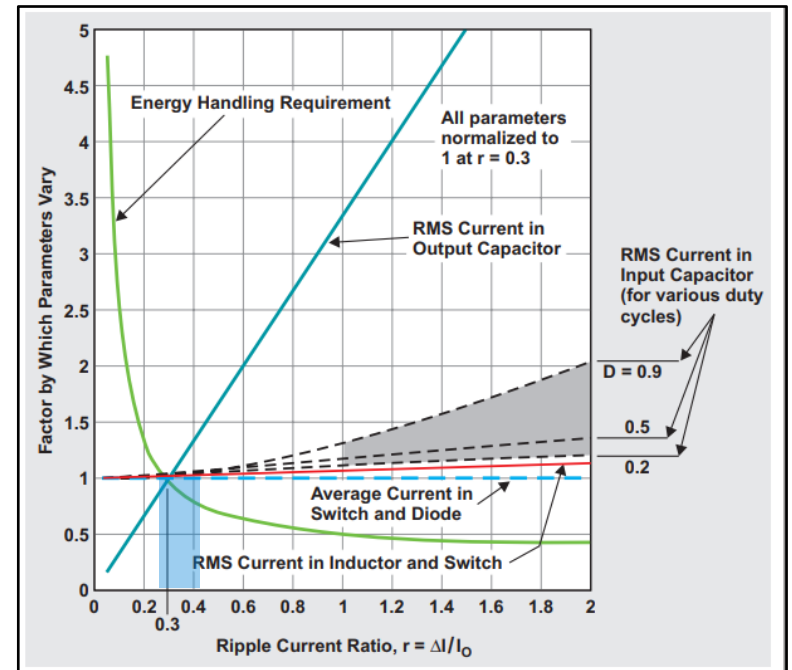
$$L_{MIN} > \frac{V_{OUT}}{f_{SW} \cdot I_{LOAD(MAX)}} \cdot 1.4$$



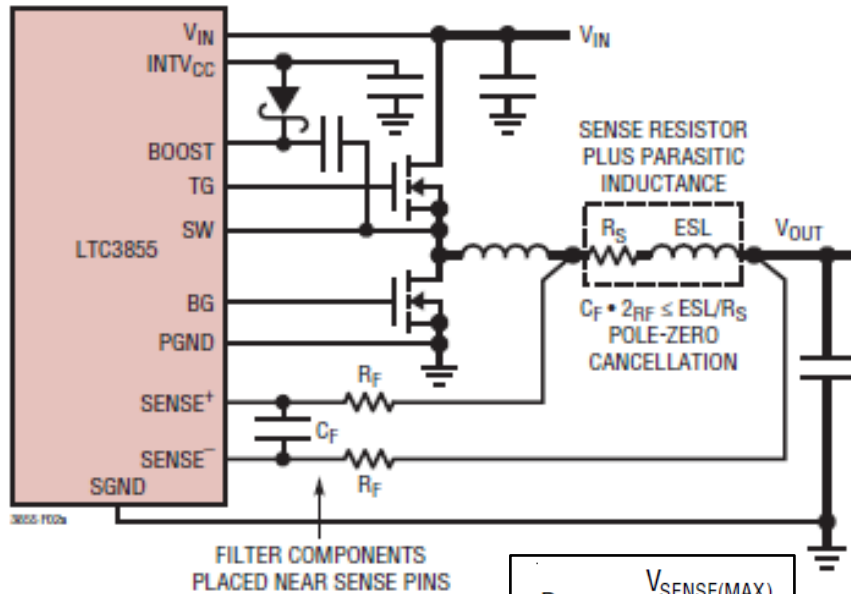 Controller Circuit Design : Current Sense


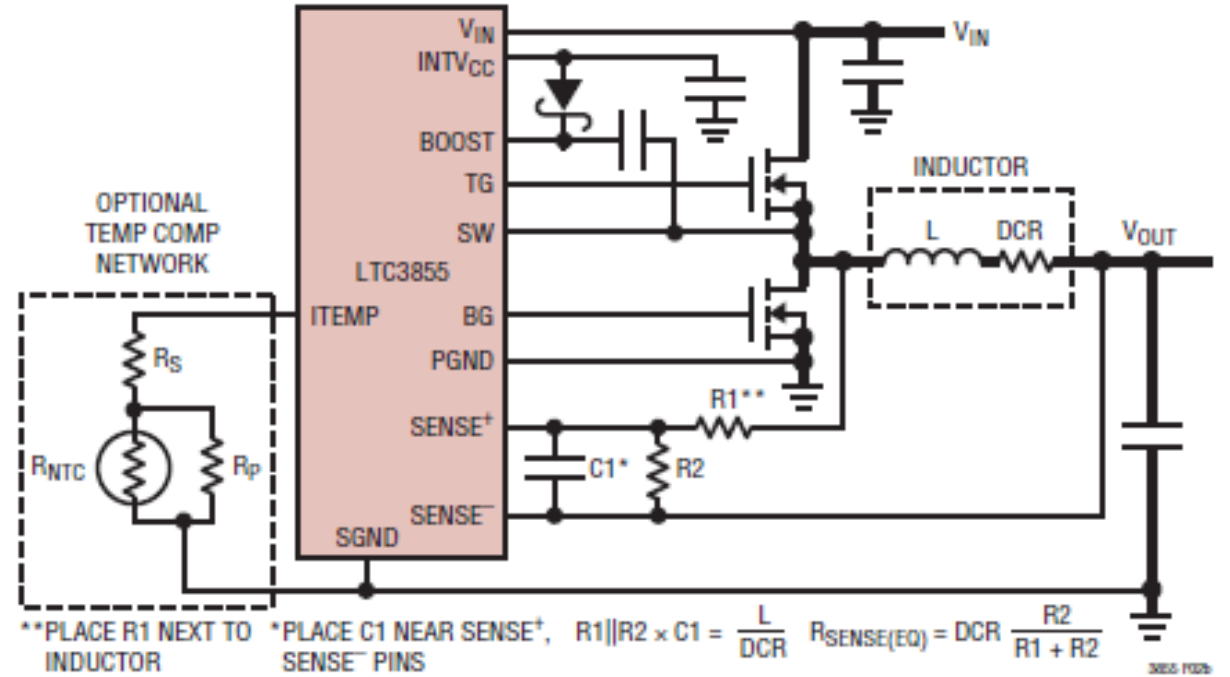
$$R_{SENSE} = \frac{V_{SENSE(MAX)}}{I_{(MAX)} + \frac{\Delta I_L}{2}}$$



**PLACE R1 NEXT TO INDUCTOR *PLACE C1 NEAR SENSE+, R1||R2 x C1 = L / DCR R_SENSE(EQ) = DCR * R2 / (R1 + R2)

$$R_{SENSE(EQUIV)} = \frac{V_{SENSE(MAX)}}{I_{(MAX)} + \frac{\Delta I_L}{2}}$$

$$R1||R2 = \frac{L}{(DCR \text{ at } 20^{\circ}C) \cdot C1}$$


$$\Delta V_{SENSE} = \frac{V_{IN} - V_{OUT}}{R1 \cdot C1} \cdot \frac{V_{OUT}}{V_{IN} \cdot f_{OSC}}$$

The sense resistor values are:


$$R_D = \frac{R_{SENSE(EQUIV)}}{DCR_{(MAX)} \text{ at } T_{L(MAX)}}$$

$$R1 = \frac{R1||R2}{R_D}; R2 = \frac{R1 \cdot R_D}{1 - R_D}$$

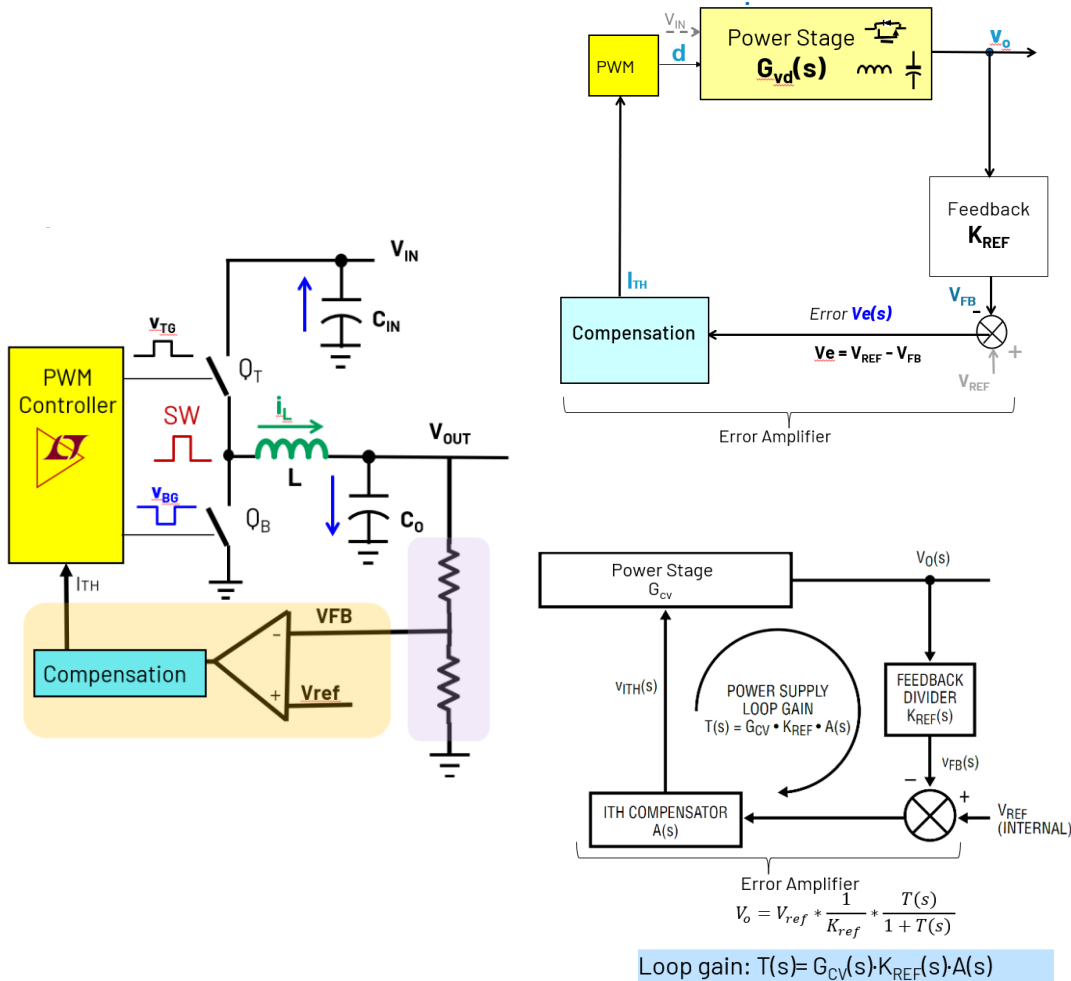
Controller Circuit Design : Loop Stability




높은 대역폭 & 안정

 


낮은 대역폭 & 안정

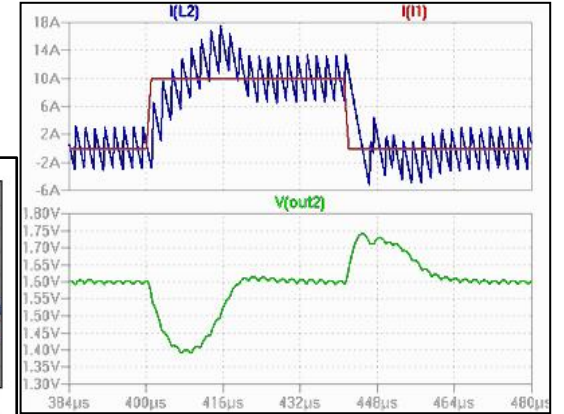

높은 대역폭 & 불안정

 

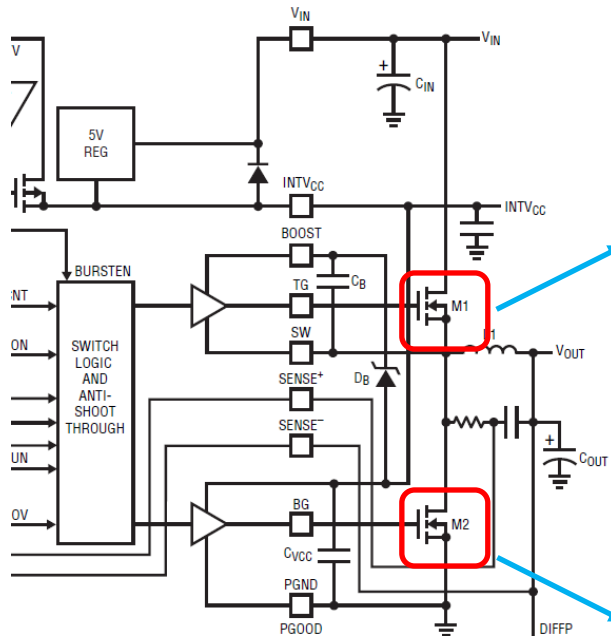Controller Circuit Design : MOSFET Selection



$$P_{MAIN} = \frac{V_{OUT}}{V_{IN}} (I_{MAX})^2 (1+\delta) R_{DS(ON)} + (V_{IN})^2 \left(\frac{I_{MAX}}{2} \right) (R_{DR}) (C_{MILLER}) \cdot \left[\frac{1}{V_{INTVCC} - V_{TH(MIN)}} + \frac{1}{V_{TH(MIN)}} \right] \cdot f_{OSC}$$

*또는 C_{RSS}

MOSFET results in: $R_{DS(ON)} = 13m\Omega$ (max), $V_{MILLER} = 2.6V$, $C_{MILLER} \cong 150pF$. At maximum input voltage with T_J (estimated) = 75°C:


$$P_{MAIN} = \frac{1.8V}{20V} (15A)^2 [1 + (0.005)(75^\circ C - 25^\circ C)] \cdot (0.013\Omega) + (20V)^2 \left(\frac{15A}{2} \right) (2\Omega) (150pF) \cdot \left[\frac{1}{5V - 2.6V} + \frac{1}{2.6V} \right] (400kHz)$$

$$= 329mW + 288mW = 617mW$$

$$P_{SYNC} = \frac{V_{IN} - V_{OUT}}{V_{IN}} (I_{MAX})^2 (1+\delta) R_{DS(ON)}$$

A Renesas RJK0330DPB, $R_{DS(ON)} = 3.9m\Omega$, is chosen for the bottom FET. The resulting power loss is:

$$P_{SYNC} = \frac{20V - 1.8V}{20V} (15A)^2 \cdot [1 + (0.005) \cdot (75^\circ C - 25^\circ C)] \cdot 0.0039\Omega$$
 
$$P_{SYNC} = 1W$$


Controller Circuit Design : Input & Output Capacitor

ANALOG DEVICES Hardware Design Techniques



Practical Power Solutions

1. Point-of-Load Power
2. System Power Management and Portable Power
3. Power for Mixed Analog/Digital Systems
4. **Hardware Design Techniques**

Copyright © 2009 By Analog Devices, Inc. All rights reserved. This book, or parts thereof, must not be reproduced in any form without permission of the copyright owner.

SECTION 4
HARDWARE DESIGN TECHNIQUES

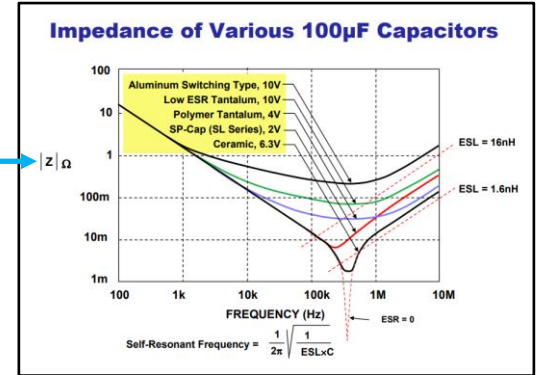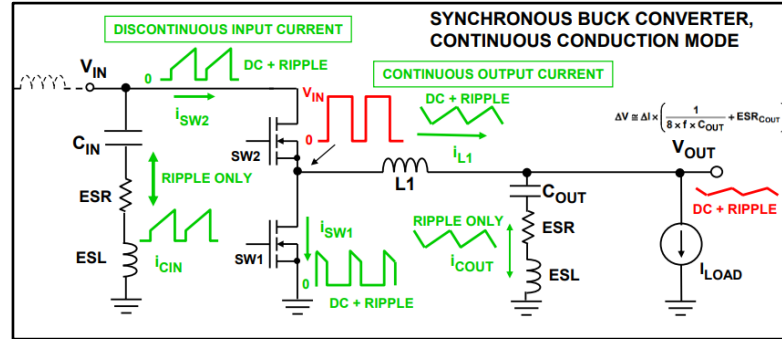- Passive Components.....4.1
- Active Components.....4.39
- Power Supply Layout and Grounding.....4.52
- Shielding.....4.73
- Thermal Design.....4.76
- Technical References.....4.84



$$|Z| = \frac{I}{\omega C} \rightarrow |z|_{\Omega}$$

$$C_{IN} \text{ Required } I_{RMS} \approx \frac{I_{MAX}}{V_{IN}} [(V_{OUT})(V_{IN} - V_{OUT})]^{1/2}$$

$$\Delta V_{OUT} \approx I_{RIPPLE} \left(ESR + \frac{1}{8fC_{OUT}} \right)$$


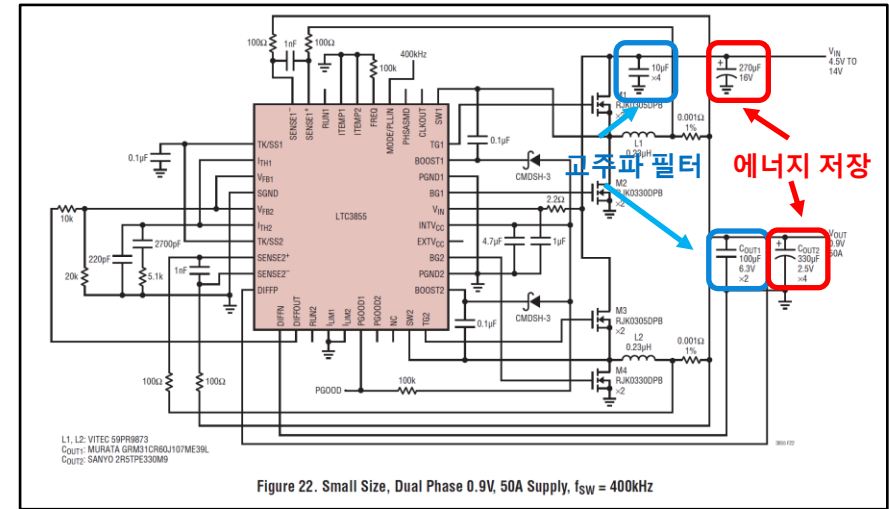
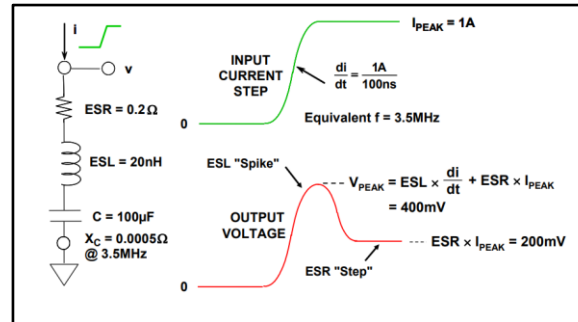


Figure 22. Small Size, Dual Phase 0.9V, 50A Supply, f_{SW} = 400kHz

<https://www.analog.com/media/en/training-seminars/design-handbooks/Practical-Power-Solutions/Section4.pdf>

Controller Circuit Design : Output Voltage

 To improve the frequency response, a feed-forward capacitor, C_{FF} , may be used. Great care should be taken to route the V_{FB} line away from noise sources, such as the inductor or the SW line.







$$V_{OUT} = 0.6V \cdot \left(1 + \frac{R_B}{R_A} \right)$$

- $f_{zero-CFF} = \frac{1}{2\pi \times C_{FF} \times R_B}$
- $f_{pole-CFF} = \frac{1}{2\pi \times C_{FF} \times (R_B || R_A)}$
- $C_{FF} = \frac{1}{2\pi \times f_x} \times \frac{1}{\sqrt{R_B \times (R_B || R_A)}}$
- $f_x = \frac{K}{V_{OUT} \times C_{OUT}}$
(단, K = 제어 루프 고유 상수로 제품마다 다름)

1Ω	10Ω	11Ω	12Ω	13Ω	15Ω	16Ω	18Ω	20Ω	22Ω	24Ω	24.9Ω	27Ω	30Ω
33Ω	36Ω	39Ω	43Ω	47Ω	49.9Ω	51Ω	56Ω	62Ω	68Ω	75Ω	82Ω	91Ω	100Ω
110Ω	120Ω	124Ω	130Ω	140Ω	150Ω	160Ω	180Ω	200Ω	210Ω	220R	240Ω	249Ω	270Ω
280Ω	300Ω	316Ω	330Ω	360Ω	374Ω	390Ω	412Ω	430Ω	470Ω	499Ω	510Ω	560Ω	590Ω
604Ω	620Ω	680Ω	750Ω	806Ω	820Ω	910Ω	1K	1.05K	1.1K	1.15K	1.2K	1.24K	1.3K
1.4K	1.5K	1.6K	1.65K	1.74K	1.8K	2K	2.1K	2.2K	2.32K	2.4K	2.49K	2.7K	2.8K
2.94K	3K	3.09K	3.3K	3.4K	3.6K	3.74K	3.9K	4.02K	4.3K	4.42K	4.64K	4.7K	4.99K
5.1K	5.23K	5.49K	5.6K	5.9K	6.04K	6.2K	6.49K	6.8K	7.15K	7.5K	8.06K	8.2K	9.1K
10K	11K	12K	13K	14K	15K	16K	18K	20K	21K	22K	24K	24.9K	27K
28K	30K	33K	36K	39K	40.2K	43K	47K	49.9K	51K	56K	59K	60.4K	62K
68K	75K	82K	91K	100K	120K	130K	150K	180K	200K	220K	270K	300K	330K
390K	470K	499K	560K	680K	1M								




Controller Circuit Design Simulation Result

  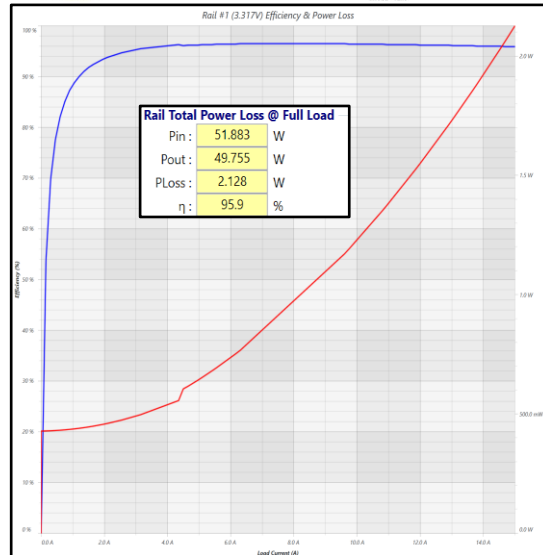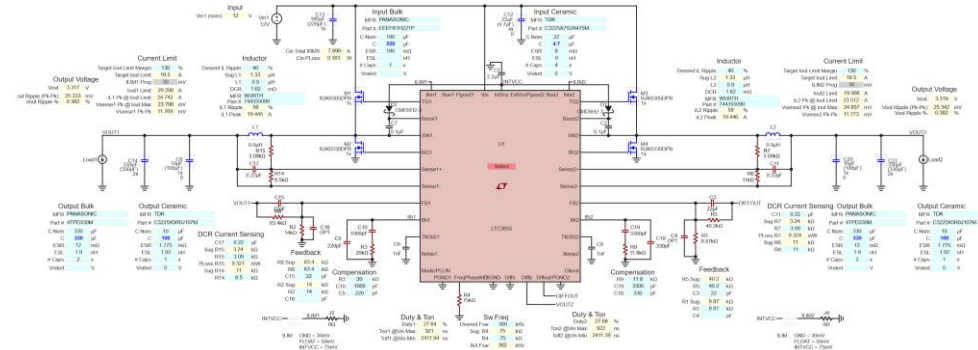- LTpowerCAD.exe Configuration
 - 12Vin
 - 300kHz
 - 3.3Vout @15A/ch




- Target Compensation Network
 - Bandwidth $\leq \frac{1}{5} \sim \frac{1}{10} f_{sw} (= 300kHz)$
 - Phase Margin $\geq 45^\circ$
 - Gain @ $\frac{f_{sw}}{2} \leq -8dB$
 - Gain @ $-180^\circ \geq 10dB$

Controller Artwork Design

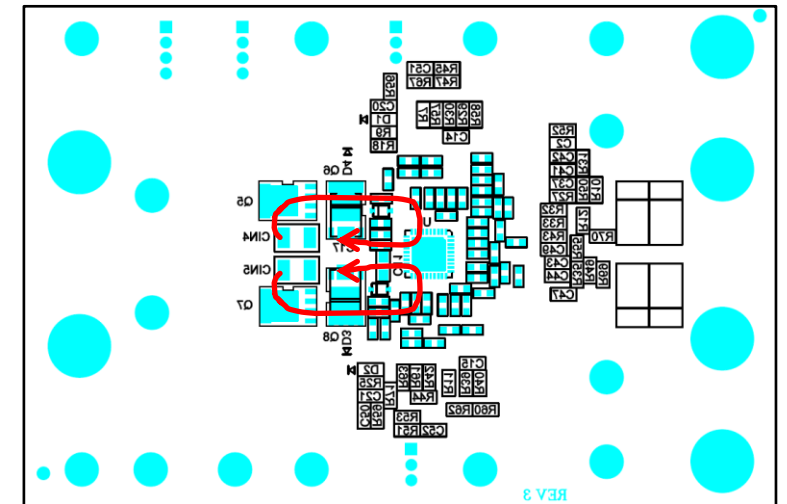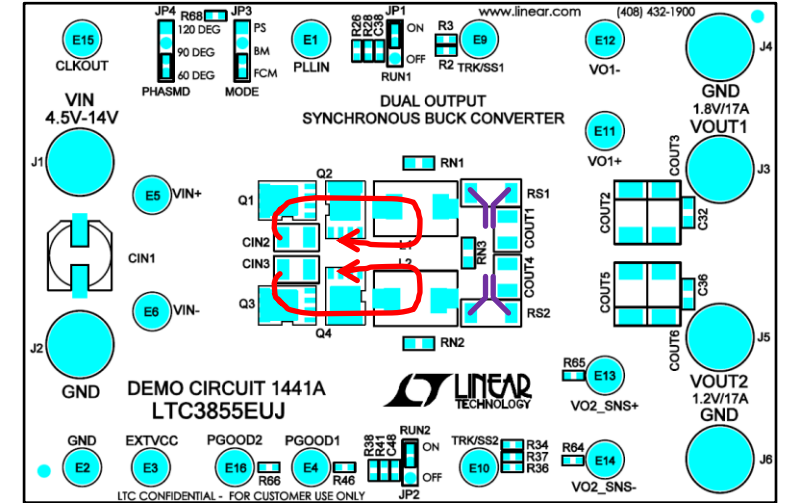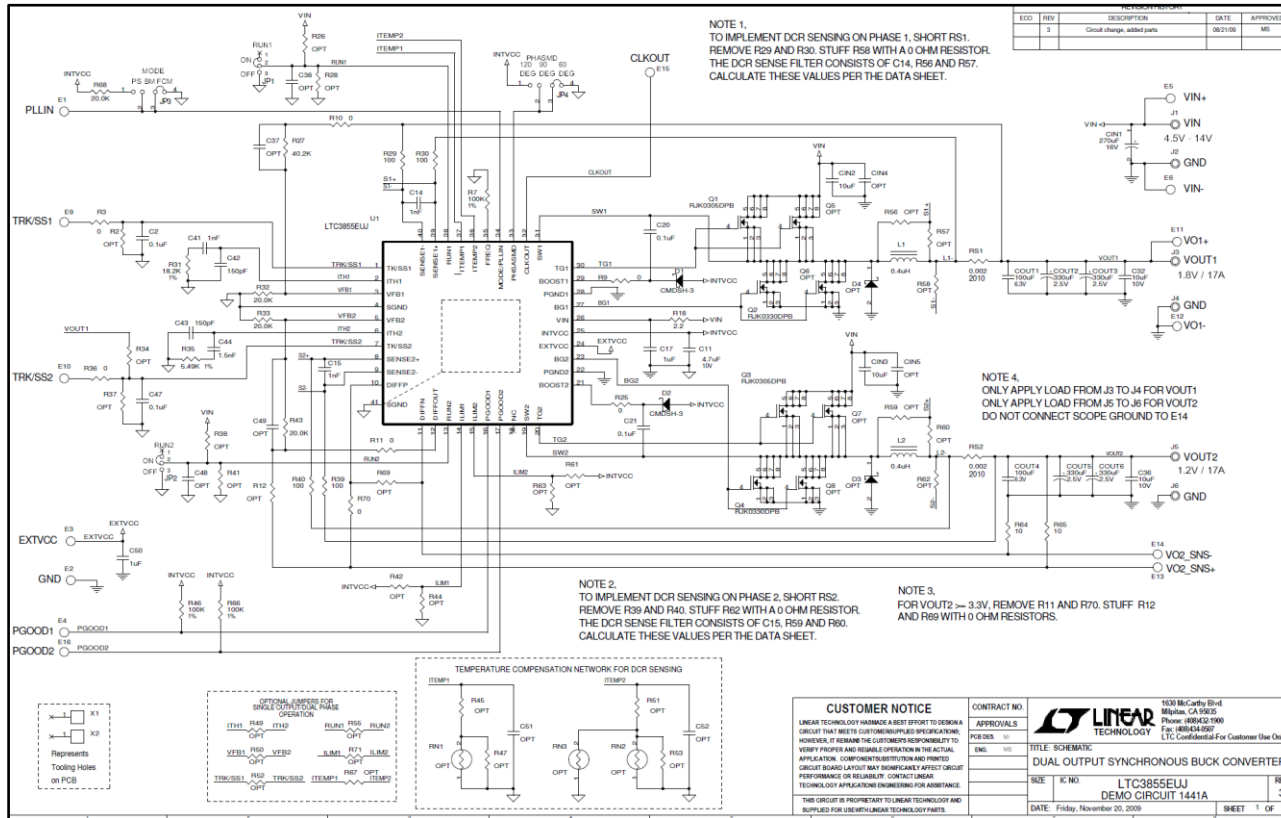


uModule Circuit Operation Sequence

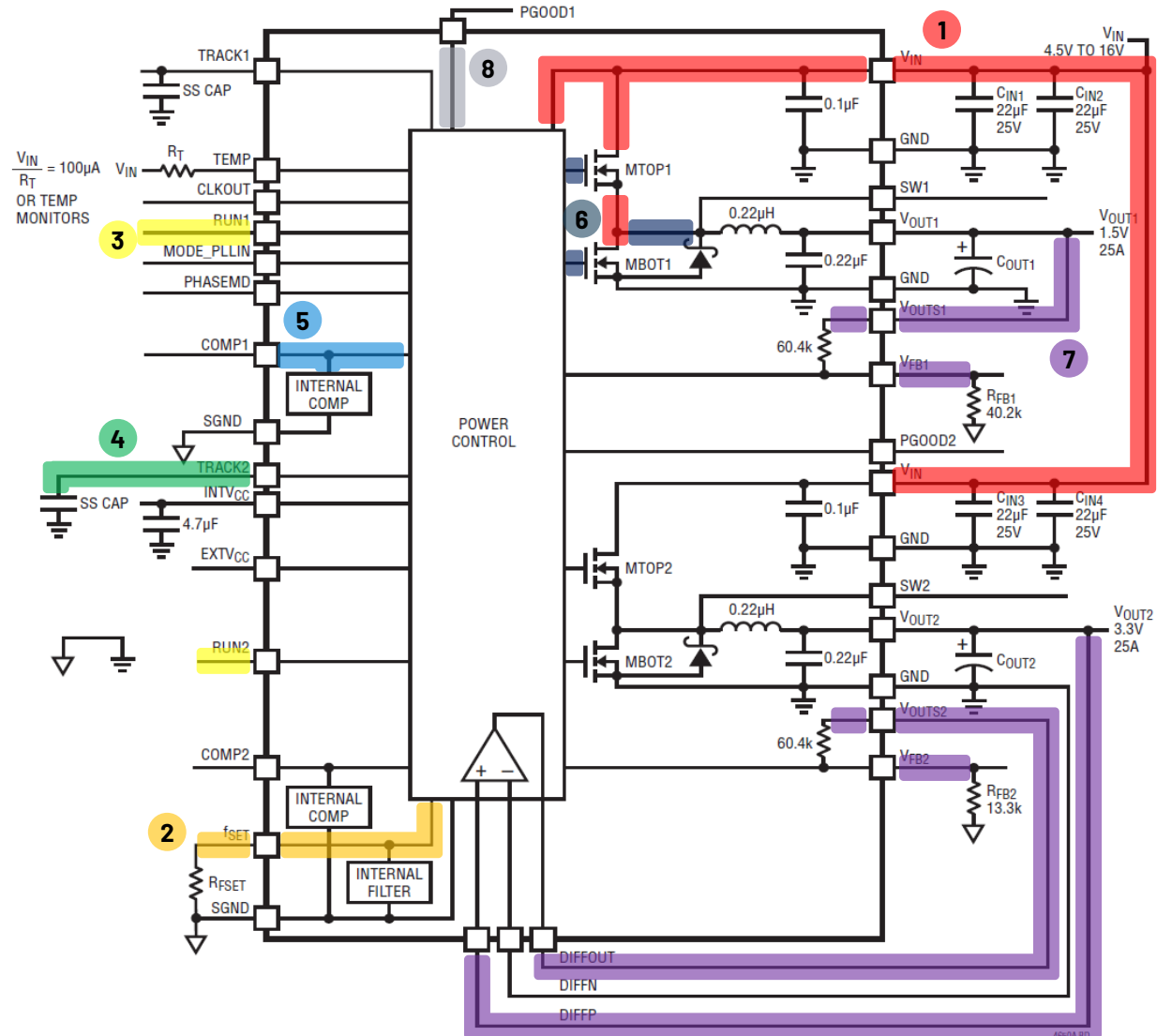

uModule Circuit Design

- Switching Frequency

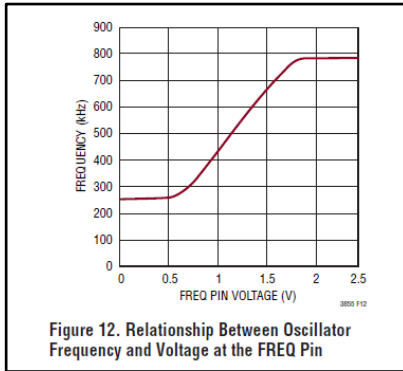

- Soft Start

$$t_{SS} = 0.6 \cdot \frac{C_{SS}}{1.3\mu A}$$

- Output Voltage

$$V_{OUT} = 0.6V \cdot \frac{60.4k + R_{FB}}{R_{FB}}$$

Table 1. V_{FB} Resistor Table vs Various Output Voltages

V_{OUT}	0.6V	1.0V	1.2V	1.5V	1.8V	2.5V	3.3V	5V
R_{FB}	Open	90.9k	60.4k	40.2k	30.2k	19.1k	13.3k	8.25k

- Input & Output Capacitor

Input Capacitors

The LTM4650A module should be connected to a low AC-impedance DC source. For the regulator input, two 22 μ F input ceramic capacitors per channel are used for RMS ripple current. A 47 μ F to 100 μ F surface mount aluminum electrolytic bulk capacitor can be used for more input bulk capacitance. This bulk input capacitor is only needed if the input source impedance is compromised by long inductive leads, traces or not enough source capacitance. If low impedance power planes are used, then this bulk capacitor is not needed.


For a buck converter, the switching duty-cycle can be estimated as:

$$D = \frac{V_{OUT}}{V_{IN}}$$

Without considering the inductor current ripple, for each output, the RMS current of the input capacitor can be estimated as:

$$I_{CIN(RMS)} = \frac{I_{OUT(MAX)}}{\eta\%} \cdot \sqrt{D \cdot (1-D)}$$

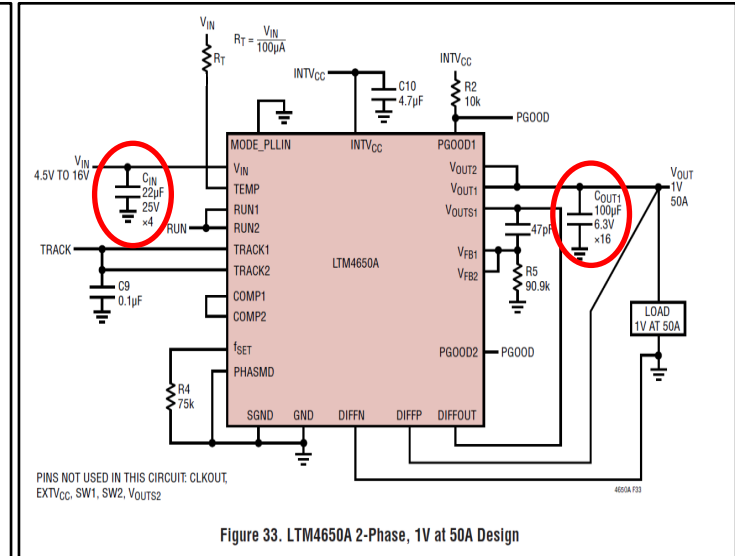In the above equation, $\eta\%$ is the estimated efficiency of the power module. The bulk capacitor can be a switcherated electrolytic aluminum capacitor, Polymer capacitor.






Output Capacitors

The LTM4650A is designed for low output voltage ripple noise and good transient response. The bulk output capacitors defined as C_{OUT} are chosen with low enough effective series resistance (ESR) to meet the output voltage ripple and transient requirements. C_{OUT} can be a low ESR tantalum capacitor, the low ESR polymer capacitor or ceramic capacitor. The typical output capacitance range for each output is from 300 μ F to 800 μ F per output channel. Additional output filtering may be required by the system designer, if further reduction of output ripples or dynamic transient spikes is required. Table 6 shows a matrix of different output voltages and output capacitors to minimize the voltage droop and overshoot during a 25% load step. The table optimizes total equivalent ESR and total bulk capacitance to optimize the transient performance. Stability criteria are considered in the Table 6




uModule Circuit Design Simulation Result

  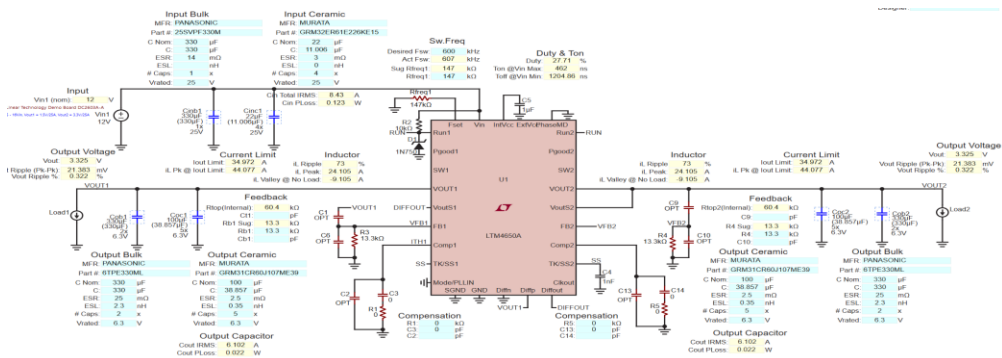- LTpowerCAD.exe Configuration
 - 12Vin
 - 600kHz
 - 3.3Vout @15A/ch




- Target Compensation Network
 - Bandwidth $\leq \frac{1}{5} \sim \frac{1}{10} f_{sw} (= 600kHz)$
 - Phase Margin $\geq 45^\circ$
 - Gain @ $\frac{f_{sw}}{2} \leq -8dB$
 - Gain @ $-180^\circ \geq 10dB$


uModule Artwork Design

  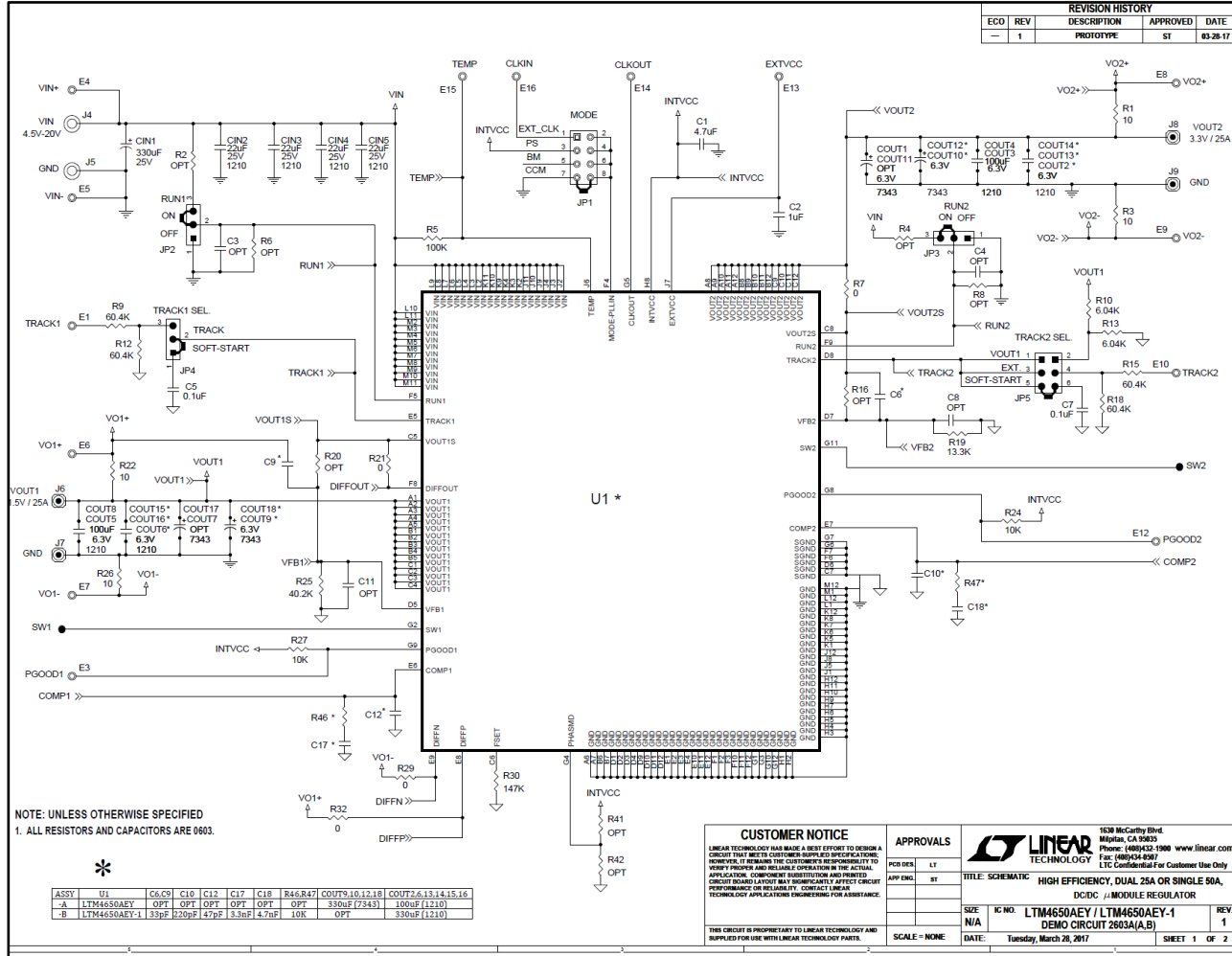


uModule Package Cross Section

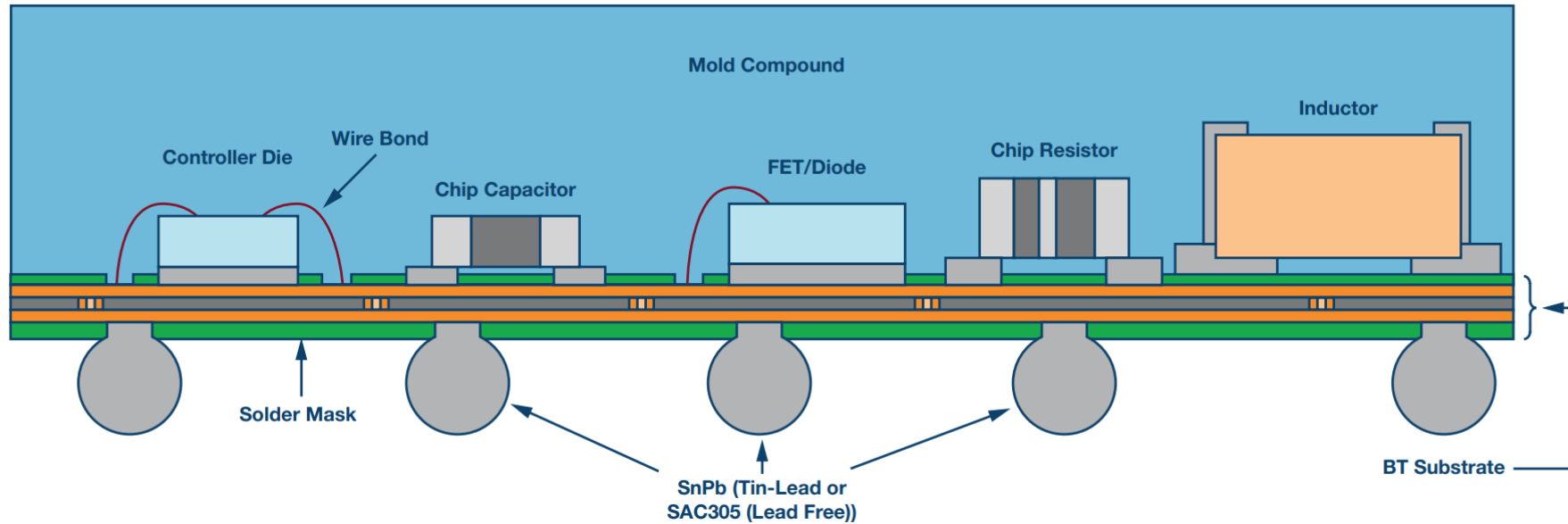


uModule Package Evolution

 


Gen 1: 2006
Standard Mold
10A in 15mm x 15mm

 


Gen 2: 2012
Integrated Heat Sink
26A in 15mm x 15mm

 

Gen 3: 2016
Component on Package
40A in 16mm x 16mm

 

Gen 4: 2018
Component on Package
125A in 15mm x 22mm

 





Gen 5: 2022
Open Frame
150A in 22mm x 24mm
200A in 22mm x 24mm

Silent Switcher Technology

SS1 Ultralow EMI 방출 → 노이즈 위험성 감소
 높은 스위칭 주파수에서도 높은 효율

SS2 Silent Switcher 구조에 필요한 바이패스 커패시터 내장
 PCB 레이아웃 민감도 최소화

    SS3 Ultralow LF 노이즈(0.1Hz to 100kHz)
 초고속 과도 응답
 전체 시스템 성능 향상



Silent Switcher^{®1}


Silent Switcher^{®2}

Silent Switcher^{®3}

μModule with Silent Switcher


- Silent Switcher의 저주파(10Hz ~ 100kHz) 노이즈 성능 향상
- 고전류 환경에서 LDO Post Filter 방식은 더 이상 실용적이지 않음
- 6.25mm × 6.25mm CoP uModule 플랫폼 활용

Silent Switcher

 


LT864xS
Silent Switcher 2

Low Noise
Current Reference
Error Amplifier

 

LT3045
Ultralow Noise LDO

Tiny CoP μModule





 


LTM4702/4703/4707
6.25mm × 6.25mm BGA



LTM4702: 18Vin, 8A Silent Switcher μ Module Regulator

FEATURES



- Complete Solution in $<1\text{cm}^2$ (Single-Sided PCB) or 0.5cm^2 (Dual-Sided PCB)
- Low Noise Silent Switcher[®]3 Architecture
- Ultralow EMI Emissions on Any PCB
- Ultralow RMS Noise (10Hz to 100kHz): $4\mu\text{V}_{\text{RMS}}$
- Ultralow Spot Noise: $4\text{nV}/\sqrt{\text{Hz}}$ at 10kHz
- Input Voltage Range: 2.7V to 18V
- Output Voltage Range: 0V to 6V
- 8A Maximum Continuous Output Current
- Fast Minimum Switch On-Time: 15ns
- Precision Current Reference: $100\mu\text{A} \pm 0.8\%$ Over Temperature
- Fast Start-Up Capability
- Wide Frequency Range: 300kHz to 4MHz
- Multiphase Parallel with Current Sharing
- Programmable Power Good
- Wide Temperature Range: -55°C to 150°C
- $6.25\text{mm} \times 6.25\text{mm} \times 5.02\text{mm}$ BGA Package

     

Lowest Noise LDO – Recent Technology Innovations

  


  LTM8080: Dual-500mA LDO with Switcher & Shield




TYPICAL APPLICATION

Dual 3.3V/500mA from 6V to 40V Input

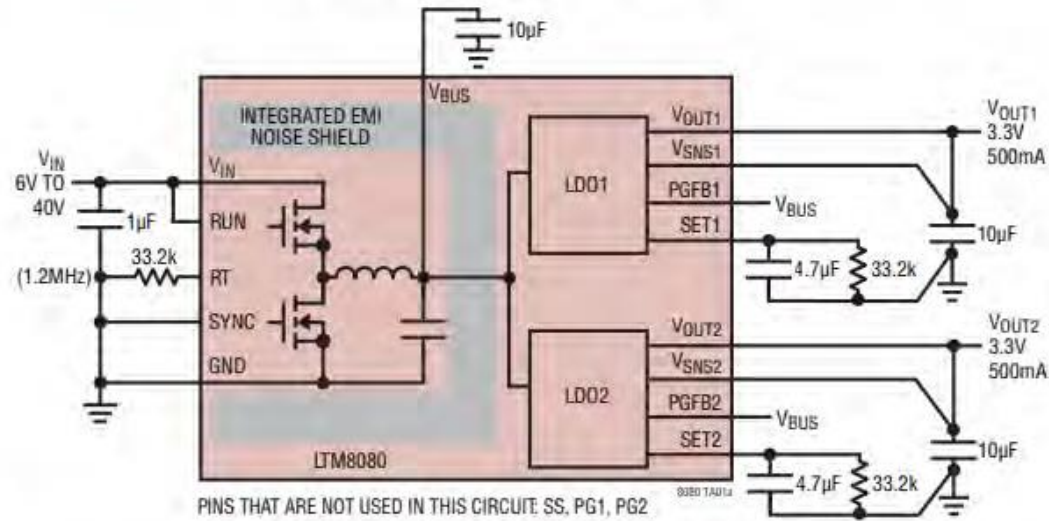


Noise Spectral Density

 


Rev. A

LTM8080: Noise Reduction with Magnetic Shield (Simulation)

LTM8080E01 w/o Magnetic Shield

 

LTM8080E01 w/ Magnetic Shield

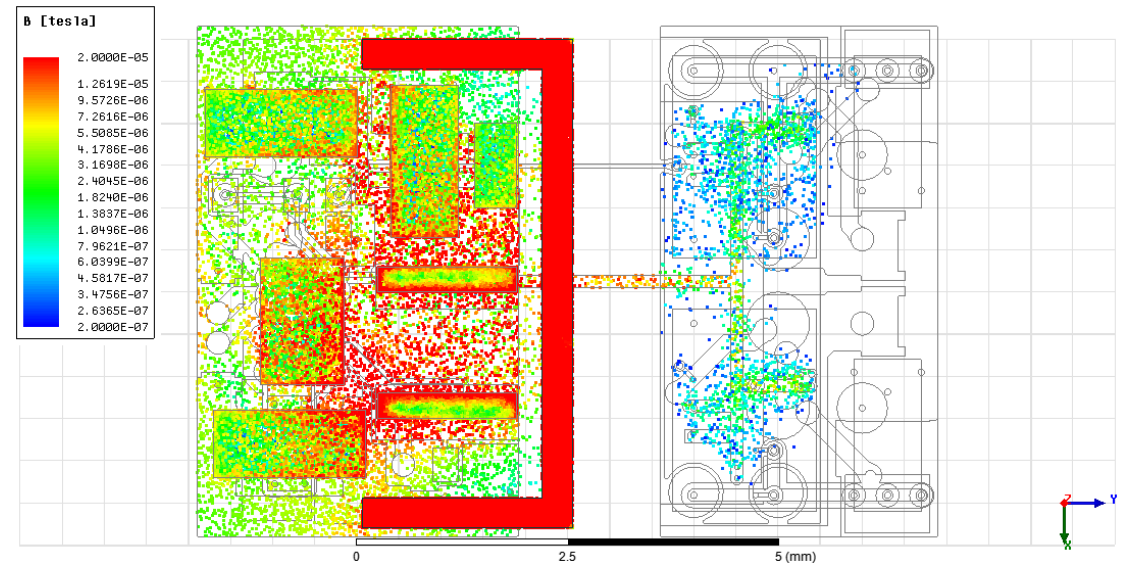


- Maxwell FEA (Finite Element Analysis) simulation 결과
 - Magnetic Shield가 Switcher → LDO로 유입되는 자기장 노이즈를 크게 저감 시킴

LTM8060F: μ Module EMI Shield Advantages



Package Level EMI Shield Advantages vs. Board Level EMI Shield

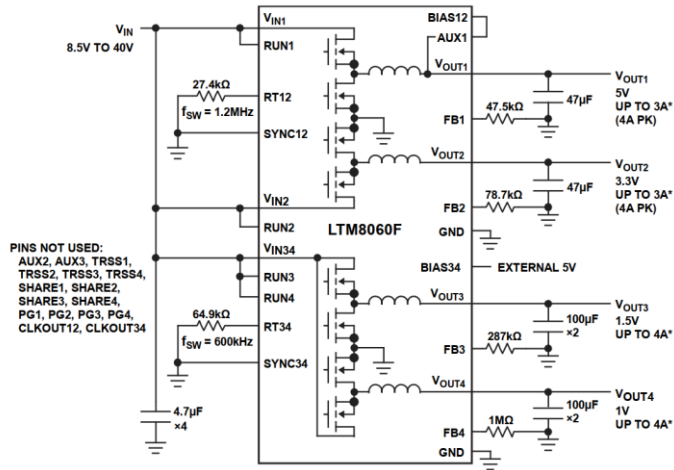- 패키지 레벨의 EMI Shield는 보드 레벨 Shield 대비 소형/낮은 높이/경량/저렴함
- 생산 시 Clip&Cage 장착 공정이 불필요하게 되어 제조 단계 감소




Package Level Conformal Shielding

Structure

  


Substrate's L2, L3 are GND planes

Board Level Metal Lid Shielding

 


Applications: Transmit + TRX Module
 Shielding: Stamped Metal Shield
 Board real estate: $\sim 301\text{mm}^2$
 Total Height: $\sim 1.8\text{mm}$
 Material cost: $\sim \$0.2\text{USD}$


Package Level Conformal Shielding

 


 
Applications: Transmit + TRX Module
 Shielding: Conformal Shielding
 Board real estate: $\sim 175\text{mm}^2$
 Total Height: $\sim 1.2\text{mm}$
 Material cost: $\sim \$0.07\text{USD}$



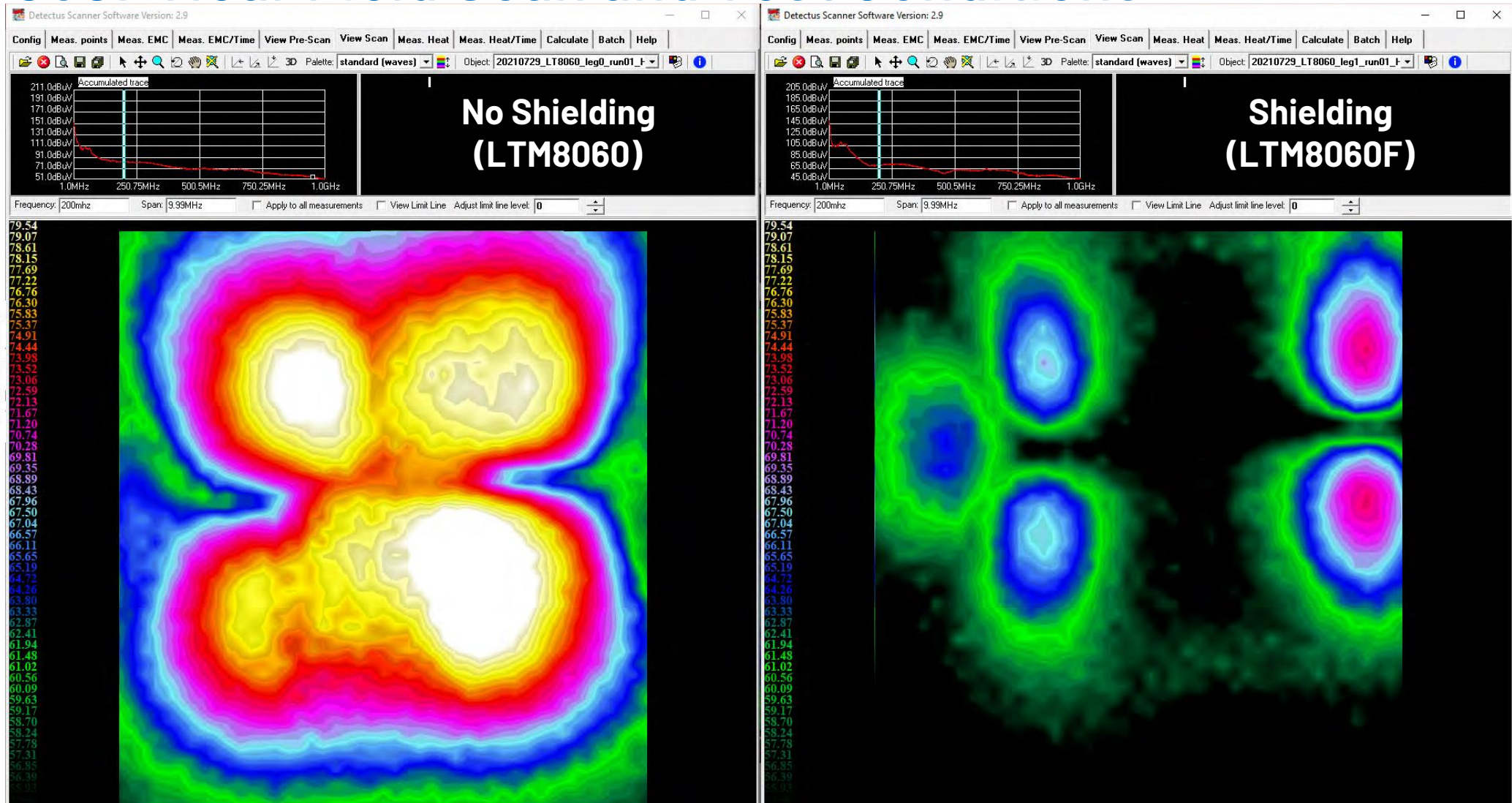LTM8060F Near Field Scan and Test Conditions




LTM8060F Near Field E Field & H Field

  



- LTM8060F는 1MHz ~ 1GHz 구간의 Near-field Electric Field 노이즈를 완전 제거
- LTM8060F는 1MHz ~ 1GHz 구간의 Near-field Magnetic Field 노이즈를 대폭 저감

LTM8060F Radiated EMI


 


- LTM8060 대비 LTM8060F는 방사 EMI가 크게 감소하였으며, 특히 100MHz ~ 500MHz 대역에서 큰 개선 효과 확인

  
LTM8060F Scope Probing Noise, 100% Reduction




LTM8060F Efficiency, Loss, Thermal

  

LTM8060 No Shielding

 

LTM8060F Shielding

 

- LTM8060F는 LTM8060과 같은 효율, 전력 손실, 발열 특성을 지님



Thermal					
Vin	Vout	Iout	Vbias	Fsw	Runtime
14V	5V	12A	None	1.2MHz	~30mins

LTM8060F vs. LTM8060 Major Differences




Features	LTM8060F	LTM8060
Size	16mm × 11.9mm	16mm × 11.9mm
Height	2.9mm	3.3mm
Package	LGA(pre-soldered PSGA micro bump)	BGA
Electric Field Near Field Noise	0	Normal
Magnetic Field Near Field Noise	10dB Lower	Normal
External EMI Shield	No Need	Might Need
Efficiency, Thermal, Power Loss	Same as LTM8060	Normal

  
Ultra thin: 1.18mm & 1.4mm μ Module for Optical Module






LTM4691 Dual 2A

 

LTM4663 1.5A TEC

 

 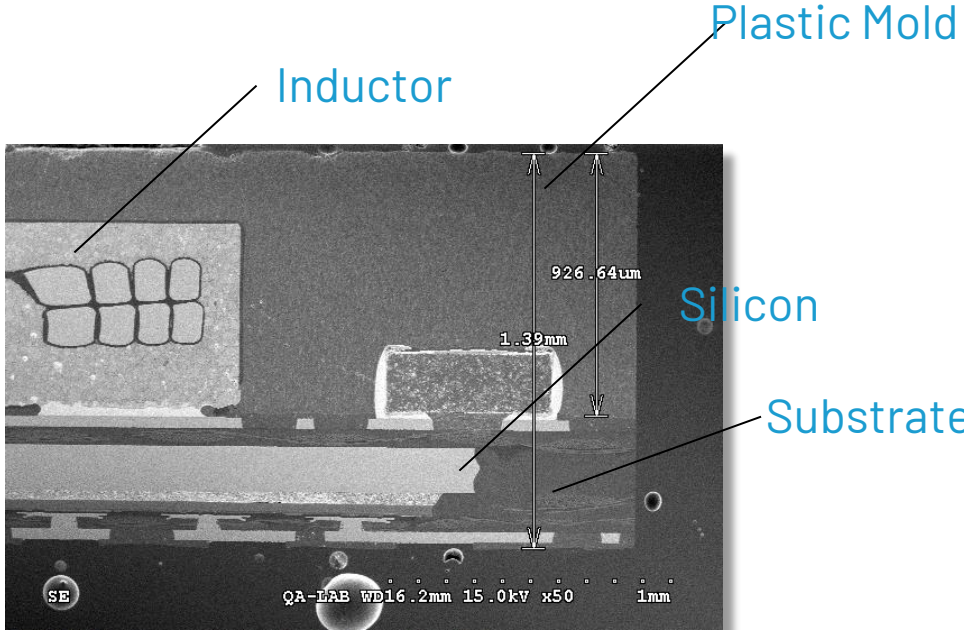 Thinner, Smaller: Embedded Si + Inductor on Top + Overmolded



Ultra thin Future: 1.2mm tall



Data Sheet LTM4723

Low V_{IN} , Ultrathin Dual 4A or Single 8A Step-Down DC-to-DC μ Module Regulator

FEATURES

- ▶ Input voltage range: 2.25V to 5.5V
- ▶ Programmable 0.5V to 3.6V output
- ▶ Dual 4A or single 8A output current
- ▶ $\pm 1.5\%$ total output voltage regulation
- ▶ Current mode control, fast transient
- ▶ External CLK synchronization 1MHz to 3MHz
- ▶ 180° out-of-phase operation
- ▶ Output voltage tracking and soft start
- ▶ Burst selectable pulse-skipping/Burst Mode/forced continuous mode at light load
- ▶ Output voltage tracking

GENERAL DESCRIPTION

The *LTM4723* is a complete dual 4A output switching mode step-down dc-to-dc power supply in a tiny 4.25mm × 4.25mm × 1.35mm LGA package. Included in the package are the switching controller, power FETs, inductors, and **1.20mm** tall components. Operating over an input voltage range of 2.25V to 5.5V, the *LTM4723* supports two outputs with a programmable output voltage range from 0.5V to 3.6V set by external resistors. Two outputs can be paralleled for a single 8A load. Only a few ceramic input and output capacitors are needed.

TYPICAL APPLICATION



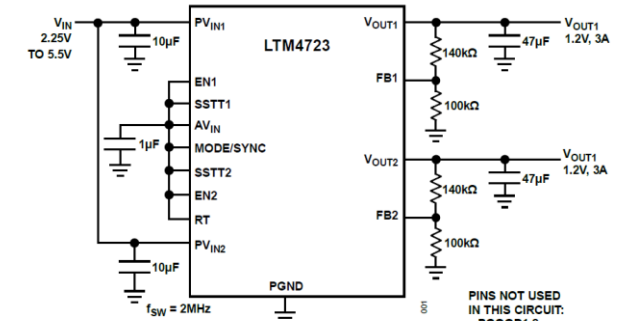


Figure 1. *LTM4723* Dual 4A Step-Down μ Module[®] Regulator

A Typical 48V System

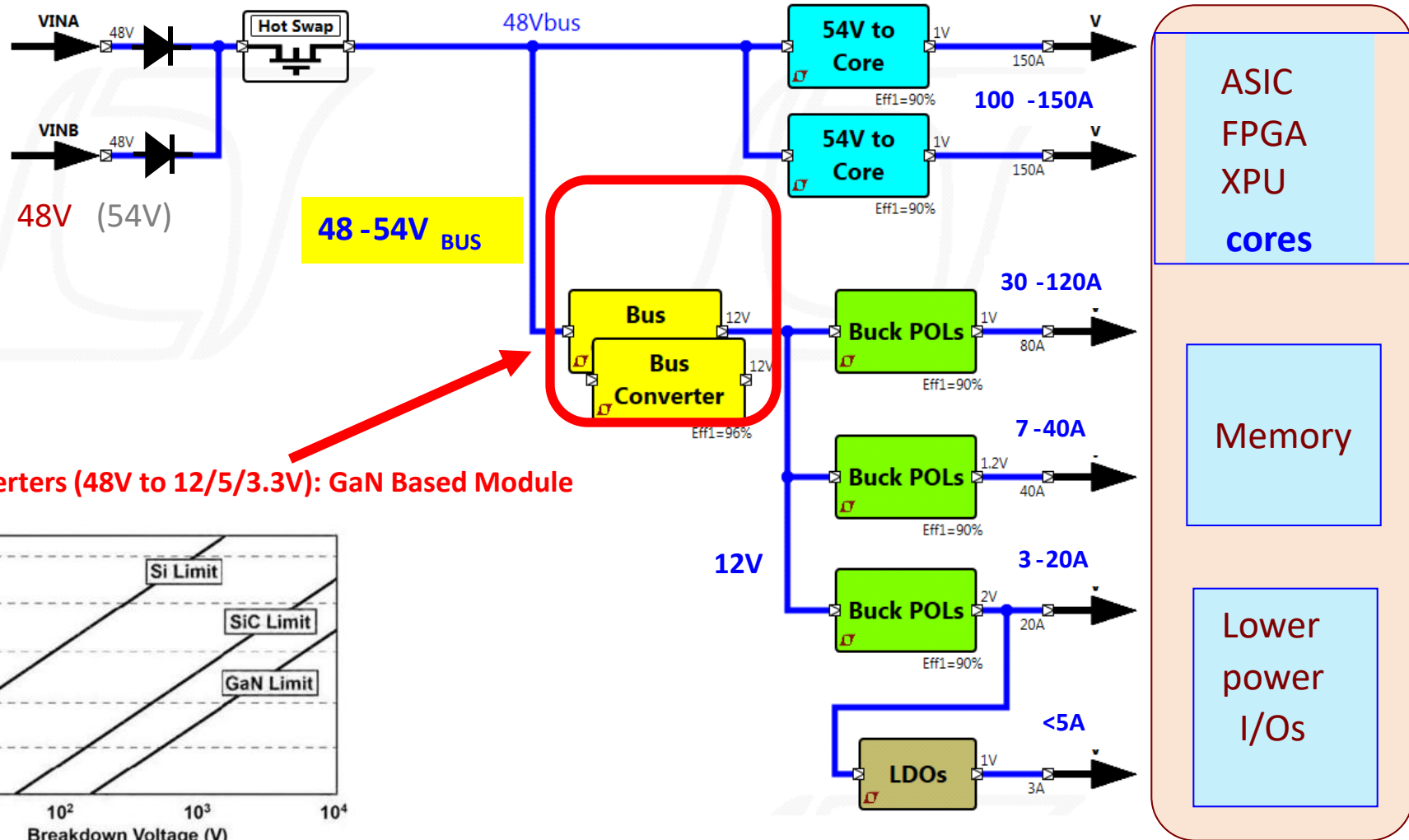


 Bus Converters (48V to 12V/5V/3.3V): GaN Based Module




GaN Solution Power Density

 LTC3892 (Si MOSFETs) demo board
(48VIN, 12Vout, 15A, 150kHz)






- High switching loss
- Low switching frequency
- **Bulky inductor!**

 LTC7891 (GaN FETs) demo board
(48VIN, 12Vout, 20A, 400kHz)



- Lower switching loss
- Higher switching frequency
- **Much smaller inductor!**

   Design Challenges/Concerns with Discrete GaN



- **Assembly: Die on FR4 PCB:**
 - 기계적 신뢰성 문제 발생 가능
 - Underfill 공정 필요
 - 전류 밀도 및 열 스트레스 증가


- **PCB layout requirements:**
 - 높은 스위칭 주파수로 인한 까다로운 레이아웃 요구 조건
 - PCB 기생 임피던스에 매우 민감하게 반응
 - Hot Loop 면적을 최소화 해야 하는 숙제

- **Circuit design:**
 - 전압, 전류, 열 특성에 따른 디바이스 Derating
 - Dead Time 및 Driver 구동 최적화 필요

GaN FETs vs. Si MOSFETs in Hard Switching Buck


- **Lower switching loss**

GaN turn on/off faster

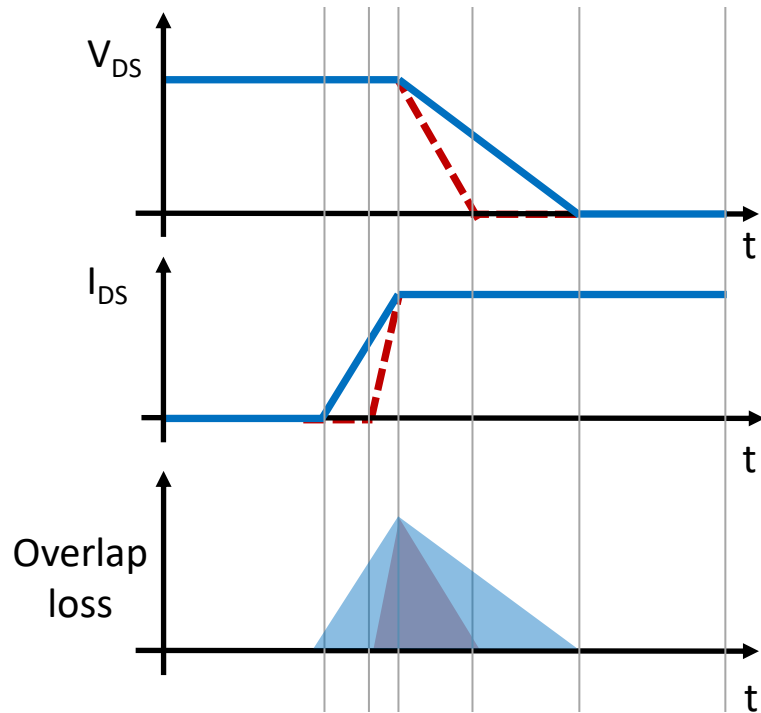

- **Higher risk of switching ringing**


 
동일한 Hot Loop ESL 조건에서도 GaN 솔루션은 더 큰 Switching Ringing이 나타남



➤ **Hard Switching GaN 기반 컨버터는 레이아웃을 특히 주의 깊게 설계해야 함**




Layout Optimization: Minimize ESL in Hot Loop

  - Decoupling Capacitor를 GaN FET 바로 근처에 배치할 것.
- 전류 루프 면적을 최소화할 것.
- 충분한 개수의 Via를 사용할 것.
- Ansys Q3D를 사용해 루프 ESL을 검증할 것.






Layout Optimization: Gate Driver Loop Design

  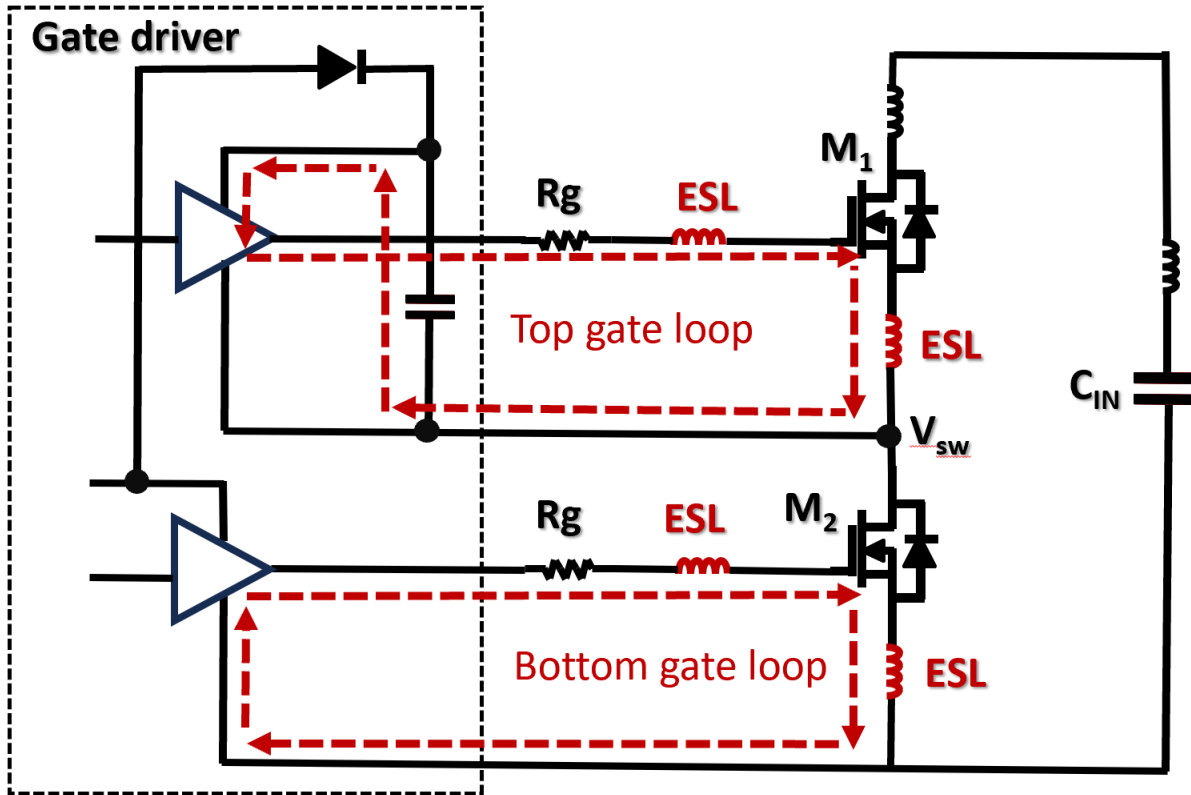- Gate Driver 루프 면적을 최소화할 것.
- Gate Driver 경로를 파워 경로와 분리할 것.
- Ansys Q3D를 사용해 Gate Drive 루프 ESL을 검증할 것.





Layout Optimization: Minimize Substrate Power Loss

   - 높은 전류 경로에 큰 ESR이 존재하면 기판(Substrate)에서 상당한 전력 손실이 발생할 수 있음.
- Ansys SIWave를 활용해 고전류 집중 구간을 찾고, 기판에서 발생하는 전력 손실을 분석할 것.



  80V/20A GaN-Based μ Module Regulator (LTM4730)



FEATURES


- Input Voltage Range: 30V to 80V
- Wide Output Voltage Range: 5V to 36V
- Tightly regulated and adjustable Vout
- 97% Efficiency (48VIN, 12VOUT, 20A)
- Scalable: Parallel for higher power
- Current mode control for easy current sharing
- 13mm x 13mm x 11.7mm BGA Package

APPLICATIONS



- Telecom, Datacenter, Industrial, and ATE
- High-reliability applications
- Broad markets

STATUS



- Sample: 02/2026
- Production: 10/2026

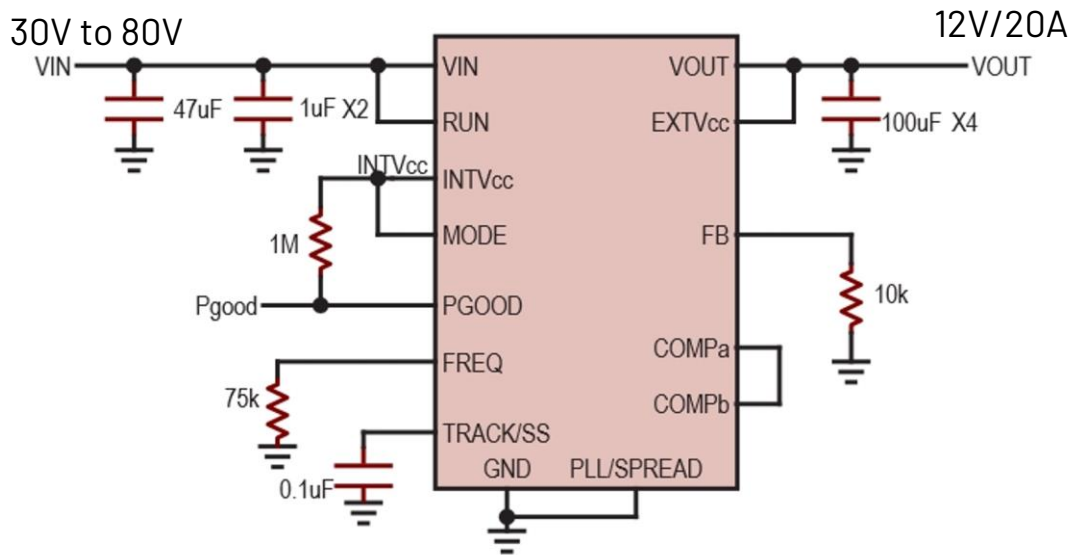


 
 
Package Thermal Verification via Icepak Simulation




Case temperature

  

GaN FETs temperature

   



Substrate temperature

 

BGA ball temperature




Clean Switching Node Waveform

  - Test under 48Vin, 12Vout@20A, fsw 400kHz




LTM4730 Gets High Power Density

   
- LTM4730 has **x10** power density than Si solution
- LTM4730 has **x3.8** density than discrete GaN solution




LTM4730 Gets High Power Efficiency

 

A Typical 48V System

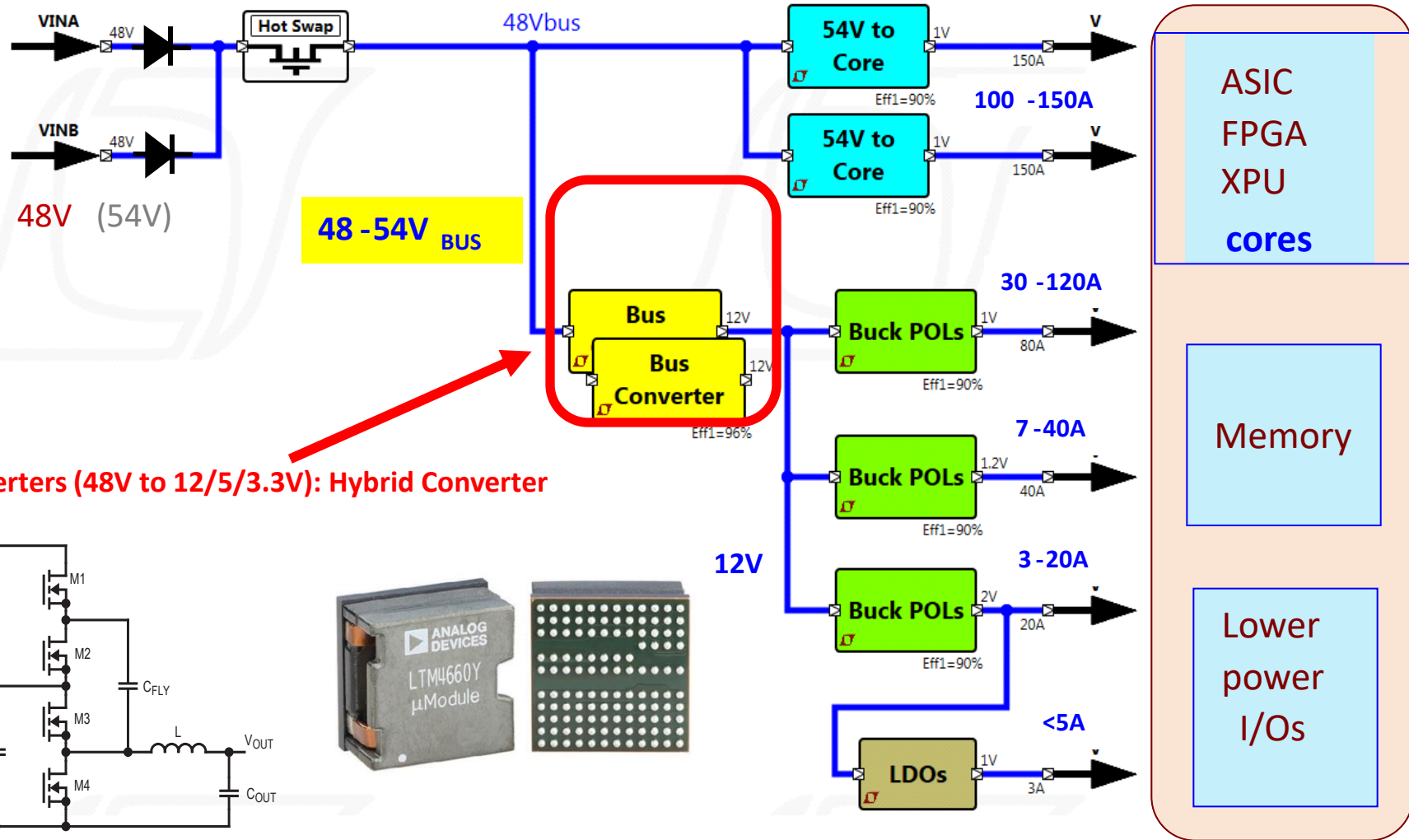


 Bus Converters (48V to 12/5/3.3V): Hybrid Converter





LTM4660 Hybrid Converter


Switched Capacitor

 


Synchronous Buck

  

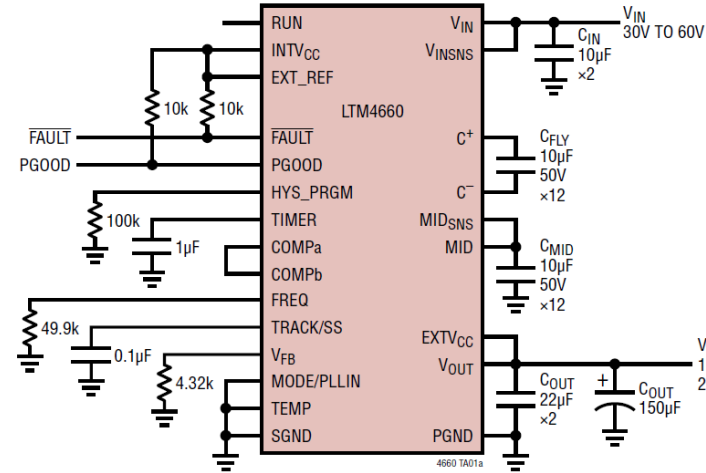
12V, 25A DC/DC μ Module Nonisolated Bus Converter



 Efficiency vs Load Current
 $V_{OUT} = 12V$





 
Radiated EMI Performance (CISPR22 Radiated Emission Test with Class B 3m Limits)



$V_{IN} = 54V$
 $V_{OUT} = 12V$
 $P_{OUT} = 300W$, $f_{SW} = 350kHz$
 DC2879A, MEASURED IN A 3m CHAMBER, PEAK DETECT METHOD


What is PMBus

 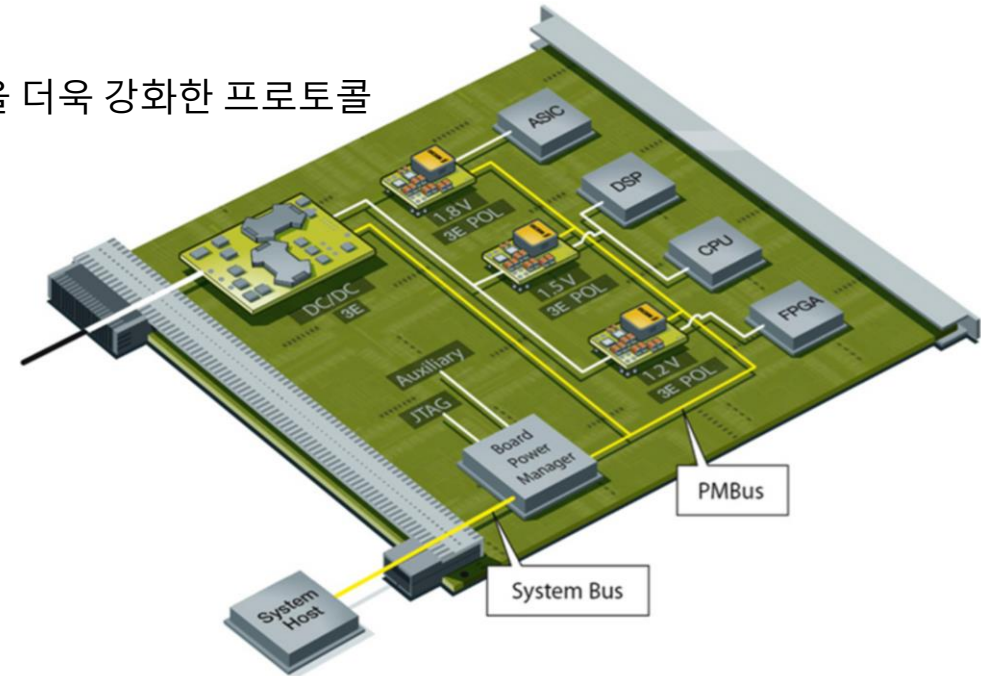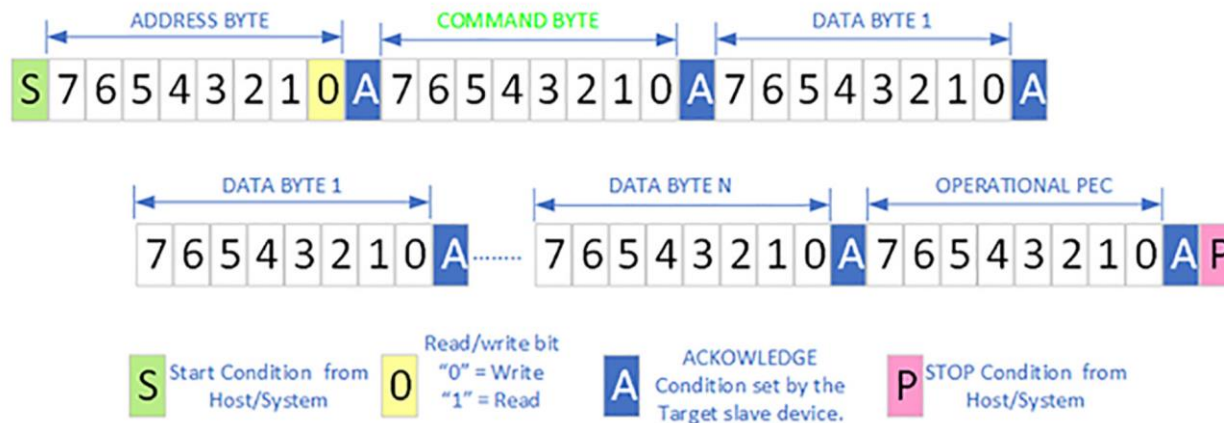- PMBus는 전원 관리(Power Management)를 위한 I2C 기반 통신 표준
- PMBus는 SMBUS(System Management BUS)를 확장한 형태로, 전원 관리에 필요한 기능을 더욱 강화한 프로토콜
- PMBus 통신은 2개의 신호선을 사용
 - SDA(Serial Data)
 - SCL(Serial Clock)
- PMBus는 최대 1MHz의 Interface 속도를 지원합니다.
- PMBus Data Packet 구조
 - 7bit address + 1bit Read/Write bit
 - 이후 8bit command Byte(명령 코드 포함)
 - 그 뒤 하나 이상의 8bit Data Byte 전송



PMBus: Less Power Usage and Better Power Control

 - PMBus는 설계를 단순화하고, 소프트웨어 부담을 줄이며, 실시간 진단 및 데이터 수집 기능을 제공하여 데이터 수집과 전력 사용 효율(PUE, power utilization effectiveness)을 개선하는데 도움이 됨
- PMBus는 다음과 같은 기능을 제공




Sequence

Turn on managed power supplies in an order and with timing defined by the user.



Monitor Telemetry

 Readback voltage, current, power, temperature, status.




Trim (Servo) and Margin

Servo loop digitally adjusts output voltage to a user-defined target or setpoint to tight DC accuracy. Margin-test system by adjusting output voltage.



Manage Faults

 Programmable fault responses protect system, shut down in orderly fashion, restart automatically if fault is removed.



Create Fault Log

Black-box recorder, capture events leading up to fault, stored in NVM.




New PMBus P0L Family Preview


Key Benefits

- PMBus
- P90(90nm) IC
- High Efficiency (~90%)
- Compact Size (6.25x6.25mm)
- LTM4739, LTM4740 is Common Footprint

TYPICAL APPLICATION

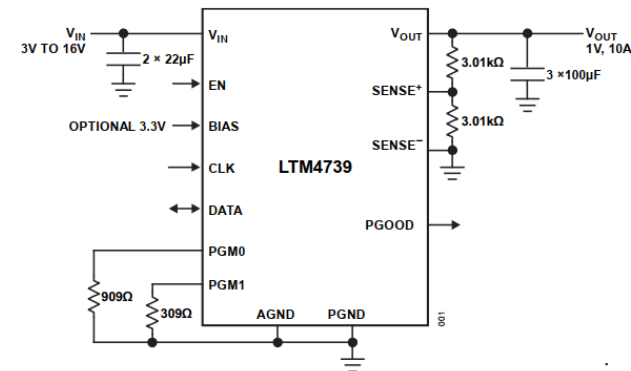


Development

 

LTM4739
10A

90% Eff 12V to 1V/10A


Development

 

LTM4740
15A

87% Eff 12V to 1V/15A


Development

 

LTM4741
25A

86.5% Eff 12V to 1V/25A

Development

 

LTM4742
Dual 20A
Single 40A

86.5% Eff 12V to 1V/40A

uModule vs uSLIC

μModule

LTMxxxxx



Integration


Size

Range


0.2A ~ 1000+ A

μSLIC


MAXMxxxxx

 

0.1A ~ 2A

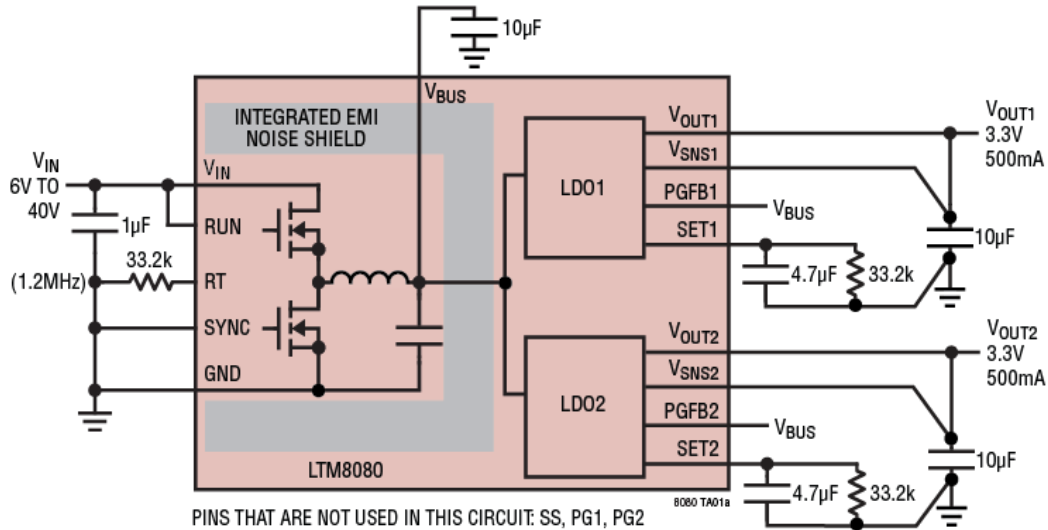

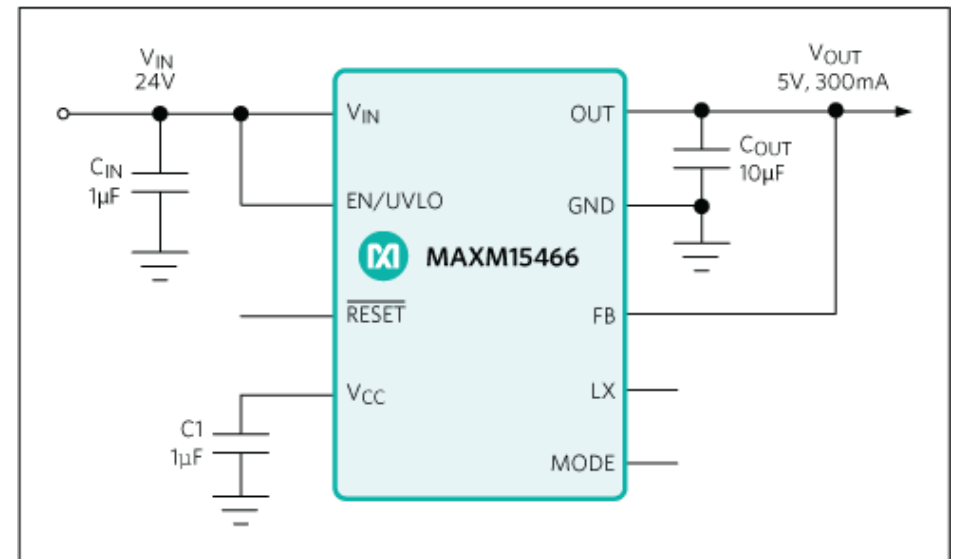
PINS THAT ARE NOT USED IN THIS CIRCUIT: SS, PG1, PG2



Comparison of Power Solution Size: 36Vin/3.3Vout/2A

Total solution area: 209.03 mm²

Power density: 31.57 W/mm²

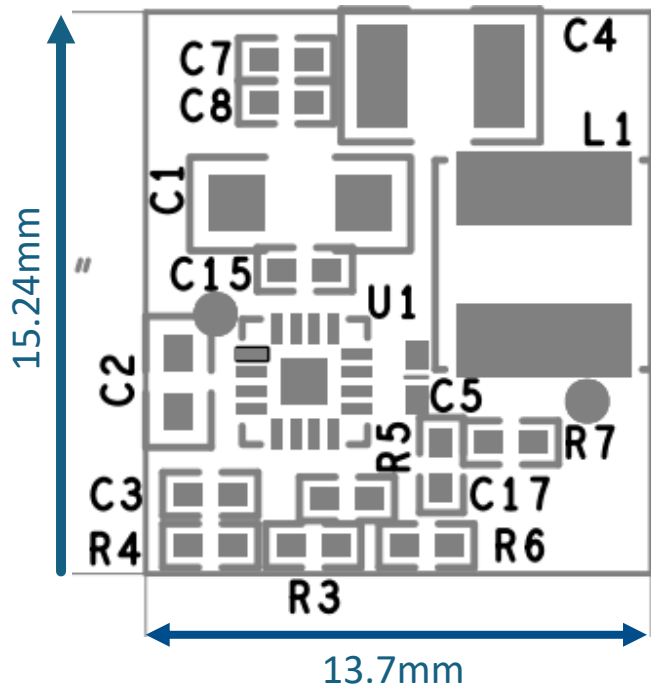

31.83%

total solution
area reduction




46.72%

increase in
power density

Total solution area: 142.5 mm²

Power density: 46.32 W/mm²

 

Monolithic power IC solution:

MAX17662

uSLIC™ power solution:

MAXM17633

What is a uSLIC Module?

- uSLIC : Micro System Level Integrated Circuit
 - 전력 IC와 인덕터를 하나의 패키지 안에 통합한 모듈

Benefits of uSLIC Modules:



Small Solution size



High Efficiency



Quicker Time To Market




High Power Density



Rugged



Reduced Eng'g Effort

 

uSLIC Packaging Technology

Multiple Layer Substrate

Better routability

Inductor Stacking





Smaller footprint

Pick and Place

Manufacturability


Pins on Periphery

Easier Board Layout

    



Common Design Challenges

 - 전자기기 소형화로 인해 설계 공간이 매우 제한적일 경우
 - Power Module을 사용하면 솔루션 크기를 크게 줄일 수 있음
- 높은 주변 온도 또는 공기 흐름이 없는 열적으로 어려운 환경
 - 고효율 Fully Synchronous Power Module을 사용하면 온도 상승을 최소화할 수 있음
- 배터리로 동작하는 장비로써 동작 시간을 최대화해야 하는 경우
 - 높은 효율은 배터리 사용 시간을 더욱 길게 확보하는 데 도움이 됨
- 긴 케이블, 품질이 나쁜 전원 등으로 인해 예측 불가능한 Voltage Transient가 발생할 수 있는 환경
 - 넓은 입력 전압 범위를 지원하는 Power Module은 추가적인 보호 기능과 안정적인 동작을 제공함




uSLIC Usages : Optical Proximity Sensor

PCB Size = 6.5 mm x 30 mm

  

uSLIC™ Module

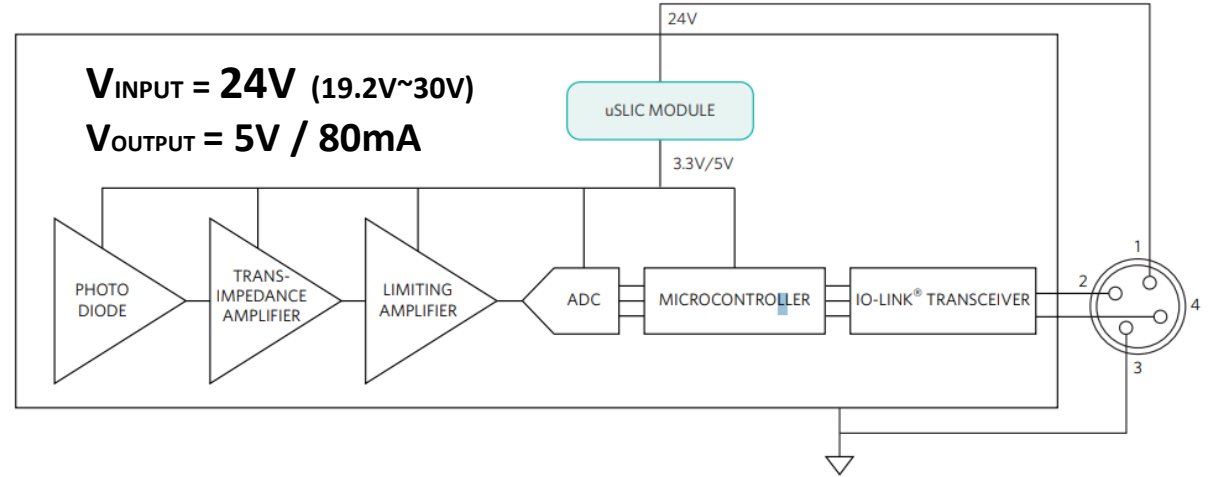

4X more efficient than the LDO

Device	Efficiency	Input Power	Power Dissipation
MAXM17532	83%	482mW	82mW
LDO	21%	1920mW	1520mW


Ratio: 395% 25% 1/19

uSLIC Usages : Motor Encoder



$V_{INPUT} = 24V$ (19.2V~30V)


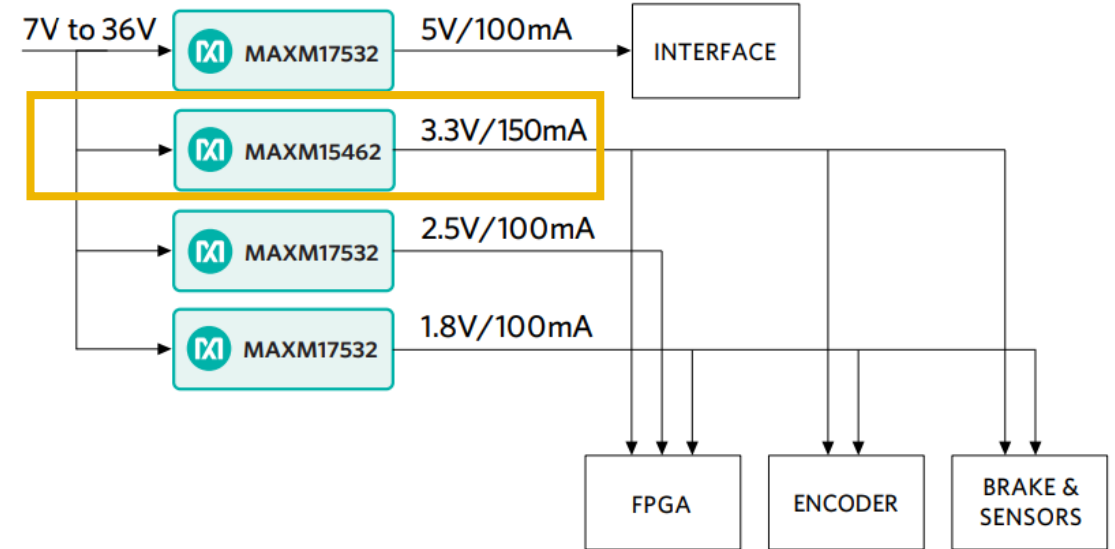
Motor inductive ringing adds an extra guard band requirement to the **7VDC to 36VDC** operating range for the power converter.



Device	Efficiency	Input Power	Power Dissipation
MAXM15462	85%	583mW	88mW
LDO	54%	917mW	422mW

Ratio: 158% 64% 1/4.8

uSLIC Usages : ATCA Housekeeping

 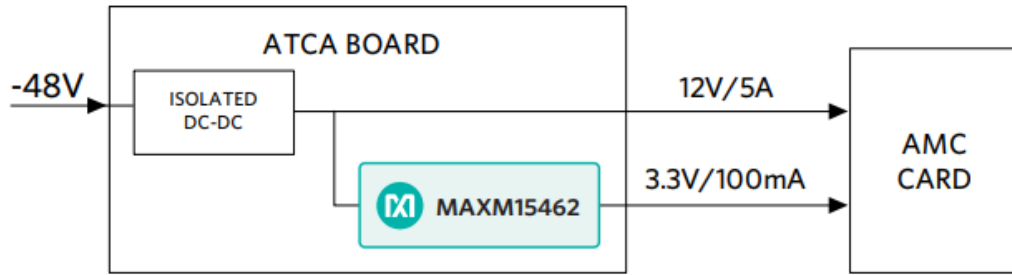


A **MAXM15462 42V/300mA uSLIC power module** would serve this +3.3V requirement very well while taking **very little space**, saving room for other circuitries.

- Easy to Use
- High Efficiency
- Flexible Design
- Robust Operation
- Rugged

uSLIC Usages : Harsh Industrial Environment




Typical 300 mA Buck

 


29.3mm² net area

MAXM15064
60V,300mA uSLIC


 


21mm² net area

28%
smaller

 


  High efficiency ensuring minimal heat output



Low Conducted and Radiated EMI

uModule & uSLIC Conclusion

 

AHEAD OF WHAT'S POSSIBLE

analog.com

